

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com

## **HIGH-ACCURACY DIGITAL LC METER**

- ★ Inductance from 10nH to 70mH
- ★ Capacitance from 0.1pF to 800nF
- ★ Automatic range selection
- ★ Accuracy  $\pm 1\%$  of reading,  
 $\pm 0.1\text{pF}$  or  $\pm 10\text{nH}$




## **SHIFT INDICATOR/REV LIMITER FOR CARS**

Helps you drive with the best economy or acceleration
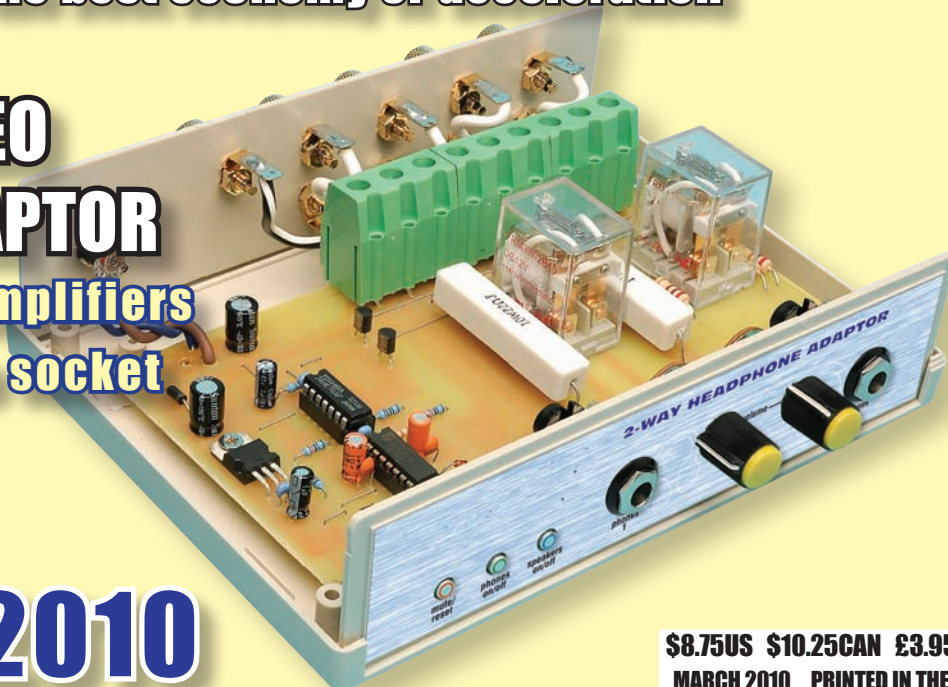
## **TWO-WAY STEREO HEADPHONE ADAPTOR**

A versatile unit for amplifiers without a headphone socket



*Plus*

## **TEACH-IN 2010**

Ladder Logic Programming For The PIC Micro

Part 5 – Advanced Programming and Interfacing Techniques

\$8.75US \$10.25CAN £3.95UK

MARCH 2010 PRINTED IN THE UK



# New Year VAT Busters

"for a limited time only..."

...we're keeping our prices at pre-VAT-increase levels"

# PEAK

electronic design ltd

## The New Atlas ESR Plus, Model ESR70

**£88.99  
inc VAT**



**NEW MODEL**

This new model of the famous **Atlas ESR** offers all the great features of the ESR60 but with extended measurement range and audible alerts.

**This is the Atlas ESR Plus!**

- Capacitance from 1uF to 22,000uF.
- ESR from 0.01 ohms to 40 ohms.
- Great for ESR and low resistance measurements (short tracing etc).
- Automatic controlled discharge function.
- Audible Alerts (for good ESR, poor ESR, open circuit and more).
- Gold plated croc clips.
- User Guide and Battery included.

## Atlas DCA - Model DCA55

The famous Peak Atlas, now with fitted premium probes. Just connect any way round to identify the type of semiconductor, pinout and lots of parameters too. Complete with battery, user guide and probes.

**£55 inc VAT**



Darlington's  
MOSFETs  
Diodes  
Transistors  
LEDs  
and more...

Look! New Probes.

## Atlas Star Pack (LCR/DCA)

**Extra VAT Busting Saver!!  
This pack saves you £25**

Includes the Atlas LCR Passive Component Analyser (model LCR40), Atlas DCA Semiconductor Analyser (model DCA55), premium padded carry case and user guides.

Complete with extra spare battery. You're ready to go!

**£125 inc VAT**



## Atlas SCR - Model SCR100

Connect Triacs or Thyristors any way round. Auto part identification and pinout display. Categories gate from 100uA to 100mA. Load conditions regulated at 12V, 100mA, even for a dying battery. Measures gate voltage drop. Long life alkaline battery supplied. Supplied with premium probes.



**Reduced Price!  
was £97**

**£79 inc VAT**

## Atlas LCR - Model LCR40

Passive component analyser. Automatically identify and measure inductors, capacitors and resistors. Auto frequency selection. Removable probes.



**£79 inc VAT**

## Atlas ESR - Model ESR60

**Special Offer!**

Measure capacitance and ESR! Capacitance from 1uF to 22,000uF ESR from 0.01 ohms to 20 ohms Battery included + Gold plated croc clips



**£75 inc VAT**

**was £87**

Peak Electronic Design Ltd, West Road House, West Road, Buxton, Derbyshire, SK17 6HF.

tel. 01298 70012 www.peakelec.co.uk sales@peakelec.co.uk Please add £2.75 p&p per order. Prices include UK VAT. See website for overseas prices.

Special Offer prices for limited period or while stocks last.

# www.stewart-of-reading.co.uk

CHECK OUT OUR WEBSITE, 1,000's of items currently in stock



**HP53131A UNIVERSAL COUNTER  
WITH OPT 001 (oven)**  
Unused Boxed 3GHZ **£850**  
Unused Boxed 225MHZ **£595**  
Used 225MHZ **£495**



**HP33120A FUNCTION GENERATOR**  
100 MicroHZ - 15MHZ  
Unused Boxed **£595**



**ANRITSU MS2601A SPECTRUM  
ANALYSER**  
10KHZ - 2.2 GHZ 50ohm **£750**

AGILENT E4402B Spectrum Analyser  
100HZ - 3GHZ with Option 1DN  
Tracking Gen; 1 DR Narrow Res;  
A4H GPIB, UKB **£5800**  
HP 8591E Spectrum Analyser  
9KHZ - 1.8GHZ with Tracking Gen  
No Moudlings, No Handle **£1500**  
HP 35670A FFT Dynamic Signal  
Analyser 2 Channel. Unused in  
original box **£1250**  
AGILENT 83752B Synthesised  
Sweeper0.01-20GHZ **£2500**  
HP83731B Synthesised 1-20GHZ  
with Opts IEI Attenuator, IE5 High  
Performance Mod Gen, IE5 High  
Stab TB **£7000**  
HP83711B Synthesised 1-20GHZ  
with Opt IEI Attenuator **£4500**  
AGILENT/HP E4431B Signal  
Generator 250KHZ-2GHZ Digital  
Modulation **£5000**  
MARCONI 2024 Signal Generator  
9KHZ-2.4GHZ Opt 04/11 HPIB **£2750**  
MARCONI/IFR 2030 Signal  
Generator 10KHZ-1.35 GHZ **£1250**  
MARCONI 2032 Signal Generator  
10KHZ-5.4GHZ **£995**  
MARCONI 2022E Synthesised  
AM/FM Signal Generator **£-**  
10KHZ-1.01GHZ Special price **£325**  
HP3580A Spectrum Analyser 5HZ-50KHZ  
Unused **£500**  
HP8566A Spectrum Analyser 100HZ-22GHZ  
**£1950**

HP8568A Spectrum Analyser  
100HZ-1500MHZ **£1250**  
AVCOM PSA-37D Spectrum  
Analyser 1MHZ-4.2GHZ **£-**  
IFR 1200S Service Communication  
Monitor **£2000**  
HP6624A Power Supply 0-20V  
0-2A Twice, 0-7V 0-5A; 0-50V  
0.8A Special price **£350**  
AVO/MEGGAR FT6/12 AC/DC  
breakdown tester **£-**

MARCONI/IFR/AEROFLEX 2025  
Signal Gen 9KHZ-2.51GHZ  
Opt 04 High Stab Opt 11  
High Power etc As New **£2500**  
SOLARTRON 1250 Frequency  
Response Analyser 10uHZ-20MHZ **£-**  
HP3324A Synthesised Function  
Generator 21MHZ **£500**  
TEKTRONIX AM503B with  
A6302 Probe and TM502A **£750**  
HP41800A Active Probe 5HZ-500MHZ **£750**

## EXTRA SPECIAL OFFER



## MARCONI 2945 RADIO COMMUNICATIONS TEST SET with....

**Opt 01** - 600 ohm Matching Unit - **Opt 03** - High Stability OCXO -  
**Opt 06** - Memory Card Drive with Real Time Clock - **Opt 08** - SSB Demodulator -  
**Opt 21** Demodulation Filters - **Opt 22** POCSAG Decode  
Complete with Carrying Bag **Only £2,500**

## Used Equipment - GUARANTEED Most Manuals Supplied

Prices plus carriage and VAT

Please check availability before ordering  
or **CALLING IN.**

## STEWART of READING

17A King Street, Mortimer,  
Near Reading RG7 3RS

T: (0118) 933 1111 • F: (0118) 933 2375  
9am - 5pm Monday - Friday



ISSN 0262 3617

- PROJECTS • THEORY •
- NEWS • COMMENT •
- POPULAR FEATURES •



VOL. 39. No 3

March 2010

# **EPE** EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

[www.epemag.com](http://www.epemag.com)

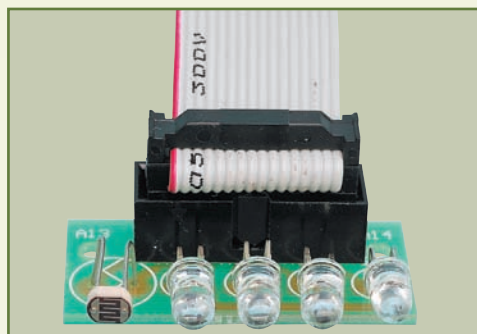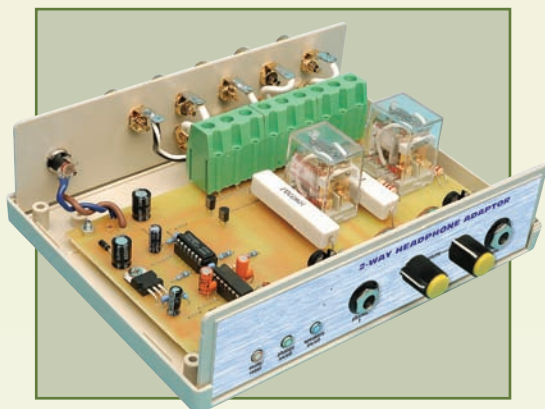

© Wimborne Publishing Ltd 2010. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our April 2010 issue will be published on Thursday 11 March 2010, see page 80 for details.

Everyday Practical Electronics, March 2010

## Projects and Circuits

- HIGH-ACCURACY DIGITAL LC METER** by Jim Rowe **10**  
A handy piece of test gear to build yourself
- 2-WAY STEREO HEADPHONE ADAPTOR** by Mauro Grassi **20**  
Provides two outputs with individual volume controls
- SHIFT INDICATOR AND REV LIMITER FOR CARS** by John Clarke **30**  
Drive with optimum performance or economy
- INGENUITY UNLIMITED** **72**  
Spectra-Lite II – a colourful display

## Series and Features

- TECHNO TALK** by Mark Nelson **18**  
Hybrid heaters and Nanostuff
- RECYCLE IT!** by Julian Edgar **42**  
Using the convex lenses from fancy car headlights
- TEACH-IN 2010 LADDER LOGIC PROGRAMMING FOR THE PIC MICRO** by Walter Ditch **46**  
Part 5: Advanced Programming and Interfacing Techniques
- CIRCUIT SURGERY** by Ian Bell **56**  
Why Do They Do That?
- PIC N' MIX** by Mike Hibbett **60**  
Easing Software Development
- PRACTICALLY SPEAKING** by Robert Penfold **64**  
Component handling and anti-static precautions
- MAX'S COOL BEANS** by Max The Magnificent **73**  
Book it!
- NET WORK** by Alan Winstanley **74**  
Off-site back-up; Smartphone

## Regulars and Services

- EDITORIAL** **7**
- NEWS** – Barry Fox highlights technology's leading edge **8**  
Plus everyday news from the world of electronics
- SUBSCRIBE TO EPE** and save money **19**
- ELECTRONIC MANUALS** **29**  
The Modern Electronics Manual and Electronics Service Manual on CD-ROM
- WIN A MICROCHIP mTouch AR1000 DEVELOPMENT KIT!** **Inside Front Cover**  
An *EPE* exclusive *FREE* entry competition
- PIC PROJECTS CD-ROM** **62**  
A plethora of handPICed projects
- PIC RESOURCES CD-ROM** **63**  
*EPE* PIC Tutorial V2, plus PIC Toolkit Mk3 and a selection of PIC-related articles
- CD-ROMS FOR ELECTRONICS** **66**  
A wide range of CD-ROMs for hobbyists, students and engineers
- READOUT** Matt Pulzer addresses general points arising **69**
- BACK ISSUES** Did you miss these? **70**
- DIRECT BOOK SERVICE** **75**  
A wide range of technical books available by mail order, plus more CD-ROMs
- EPE PCB SERVICE** **78**  
PCBs for *EPE* projects
- ADVERTISERS INDEX** **80**

**Readers' Services • Editorial and Advertisement Departments**

**7**

**01279**

**Credit Card  
Sales**

**467799**

## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95  
18Vdc Power supply (PSU120) £19.95  
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

### NEW! USB & Serial Port PIC Programmer



USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149KT - £49.95

Assembled Order Code: AS3149 - £59.95

### NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows XP Software. ZIF Socket and USB lead not incl.

Assembled Order Code: AS3128 - £49.95

Assembled with ZIF socket Order Code: AS3128ZIF - £64.95



### 'PICALL' ISP PIC Programmer



Will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC15C family) PIC microcontrollers. Free Windows software. Blank chip auto detect for super fast bulk programming. Optional ZIF socket. Assembled Order Code: AS3117 - £29.95  
Assembled with ZIF socket Order Code: AS3117ZIF - £44.95

### ATMEL 89xxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - £27.95

Assembled Order Code: AS3123 - £37.95

### Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1 rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port. Kit Order Code: 3081KT - £16.95  
Assembled Order Code: AS3081 - £24.95



### PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied. Kit Order Code: K8076KT - £39.95



### PIC Programmer & Experimenter Board

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included. Kit Order Code: K8048KT - £39.95

Assembled Order Code: VM111 - £59.95



## Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU445 £7.95

### USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055KT - £38.95

Assembled Order Code: VM110 - £64.95



### Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available. Kit Order Code: 3180KT - £49.95

Assembled Order Code: AS3180 - £59.95



### Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - £19.95

Assembled Order Code: AS3145 - £26.95  
Additional DS1820 Sensors - £3.95 each



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

### 4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £74.95

Assembled Order Code: AS3140 - £89.95




### 8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.

Kit Order Code: 3108KT - £64.95

Assembled Order Code: AS3108 - £79.95

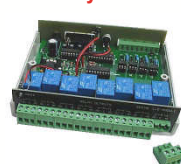

### Infrared RC 12-Channel Relay Board

Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £59.95

Assembled Order Code: AS3142 - £69.95



### Audio DTMF Decoder and Display

Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a 16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU445). Main PCB: 55x95mm. Kit Order Code: 3153KT - £34.95

Assembled Order Code: AS3153 - £44.95



### Telephone Call Logger

Stores over 2,500 x 11 digit DTMF numbers with time and date. Records all buttons pressed during a call. No need for any connection to computer during operation but logged data can be downloaded into a PC via a serial port and saved to disk. Includes a plastic case 130x100x30mm. Supply: 9-12V DC (Order Code PSU445).

Kit Order Code: 3164KT - £54.95

Assembled Order Code: AS3164 - £69.95





## Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

### 4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£69.95**  
Assembled Order Code: AS3190 - **£84.95**




### 40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC. Stand-alone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24 Vdc operation. Just change one resistor for different recording duration/sound quality. sampling frequency 4-12 kHz. Kit Order Code: 3188KT - **£28.95**  
Assembled Order Code: AS3188 - **£36.95**  
120 second version also available


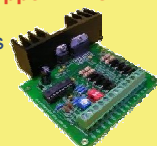
### Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications. Kit Order Code: 3187KT - **£39.95**  
Assembled Order Code: AS3187 - **£49.95**



### Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors. Kit Order Code: K8036KT - **£32.95**  
Assembled Order Code: VM106 - **£49.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

## Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

### DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£17.95**  
Assembled Order Code: AS3067 - **£24.95**

### Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£15.95**  
Assembled Order Code: AS3179 - **£22.95**



### Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£23.95**  
Assembled Order Code: AS3158 - **£33.95**




### Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£22.95**  
Assembled Order Code: AS3166v2 - **£32.95**


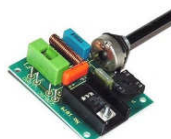
### AC Motor Speed Controller (700W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 700 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors. Kit Order Code: 1074KT - **£14.95**  
Assembled Order Code: AS1074 - **£23.95**



See [www.quasarelectronics.com](http://www.quasarelectronics.com) for lots more motor controllers



**QUASAR**  
electronics  
The Electronic Kit Specialists Since 1993

**Credit Card Sales**  
**0871 717 7168**

## Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

### 500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+. Order Code EPL500 - **£179.95**  
**Also available: 30-in-1 £19.95, 50-in-1 £29.95, 75-in-1 £39.95 £130-in-1 £44.95 & 300-in-1 £69.95 (see website for details)**



## Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

### Two-Channel USB Pc Oscilloscope

This digital storage oscilloscope uses the power of your PC to visualize electrical signals. Its high sensitive display resolution, down to 0.15mV, combined with a high bandwidth and a sampling frequency of up to 1GHz are giving this unit all the power you need. Order Code: PCSU1000 - **£399.95**



### Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use. Order Code: HPS10 - **£129.95** ~~£169.95~~



See website for more super deals!



[www.quasarelectronics.com](http://www.quasarelectronics.com)

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



# EVERYDAY PRACTICAL ELECTRONICS FEATURED KITS

March 2010

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested down under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

**Jaycar**  
Electronics

## 4 CHANNEL VERSATILE MIXER KIT

**KC-5448 £28.75 plus postage & packing**

This is an improved version of our popular guitar mixer kit and has a number of enhancements that make it even more versatile. The input sensitivity of each of the four channels is adjustable from a few millivolts to over 1 volt, so you plug in a range of input signals from a microphone to a line level signal from a CD player etc. A headphone amplifier circuit is also included for monitoring purposes. A three stage EQ is also included, making this a very versatile mixer that will operate from 12 volts. Kit includes case, PCB with overlay and all electronic components.

As published in EPE April 2009



## AV SIGNAL BOOSTER KIT

**KC-5350 £31.95 plus postage & packing**

You may experience some signal loss when using long AV cables. This kit will boost your composite, S-Video and stereo audio signals, preserving them for the highest quality transmission to your home theatre, projector or large screen TV. Kit includes case, PCB, silk-screened punched panels and all electronic components with clear English instructions. Requires 9VAC wall adaptor.

As published in EPE March 2006



## HIGH CURRENT MOTOR SPEED CONTROLLER KIT

**KC-5465 £26.25 plus postage & packing**

Controls a 12 or 24VDC motor at up to 40A continuous and features automatic soft-start, fast switch-off and a 4-digit display to show settings. Speed regulation is maintained even under heavy loads and the system includes an overload warning buzzer and a low battery alarm. Kit contains PCBs and specified electronic components.

Featured in EPE Jan 2010




## STUDIO 350 - HIGH POWER AMPLIFIER

**KC-5372 £50.75 plus postage & packing**

Delivers a whopping 350WRMS @ 4 ohms, or 200WRMS @ 8 ohms. It is super quiet, with a signal to noise ratio of 125dB(A) at full power. Harmonic distortion is just 0.002%, and frequency response is almost flat (less than -1dB) between 15Hz and 60kHz! Kit supplied in short form with PCB and electronic components. 500VA toroidal to suit MT-2146 £35.00

As published in  
EPE Oct/Nov 2006

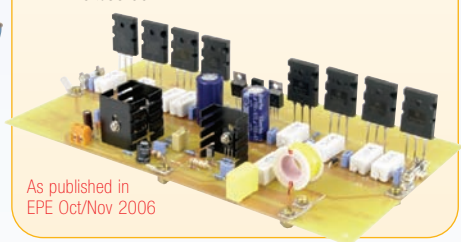

## STEREO HEADPHONE DISTRIBUTION AMPLIFIER KIT

**KC-5417 £10.25 plus postage & packing**

Drives one or two stereo headphones from any line level (1 volt peak to peak) input. The circuit features a facility to drive headphones with impedances from about 8-600Ω. Comes with PCB and all electronic components.

Featured in EPE November 2009

Also recommended: Box HB-6012 £2.00  
Power Supply Kit KC-5418 £6.00



## SMART CARD READER / PROGRAMMER

**KC-5361 £16.00 plus postage & packing**

Program both the microcontroller and EEPROM in the popular gold, silver and emerald wafer cards that conform to ISO-7816 standards. Powered by 9-12VDC wall adaptor or a 9V battery. Instructions outline software requirements that are freely available on the Internet. Kit supplied with PCB, wafer card socket and all electronic components.

As published in EPE May 2007



## EMERGENCY 12V LIGHTING CONTROLLER

**KC-5456 £20.50 plus postage & packing**

Automatically supplies power for 12V emergency lighting during a blackout. The system is powered with a 7.5Ah SLA battery which is maintained via an external smart charger. Includes manual override and over-discharge protection for the battery. Kit supplied with all electronic components, screen printed PCB, front panel and case. Charger and SLA battery available separately.

Featured in EPE  
November 2009




## RADAR SPEED GUN KIT MKII

**KC-5441 £29.00 plus postage & packing**

If you're into any kind of racing like cars, bikes boats or even the horses, this kit is for you. The electronics are mounted in the supplied Jiffy box and the radar gun assembly can be made simply with two coffee tins fitted end to end. The circuit needs 12 VDC at only 130mA so you can use a small SLA or rechargeable battery pack. Kit includes PCB and all specified components. This upgraded version is now even more stable and accurate than the popular original.

As published in EPE January 2009

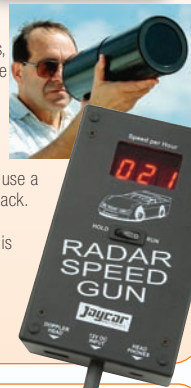

## COURTESY INTERIOR LIGHT DELAY KIT

**KC-5392 £6.00 plus postage & packing**

Enables your car to have the same interior light delay feature you find in many modern cars, allowing you time to buckle up and settle in before the light softly fades and finally goes out after a set time. Upgraded to a much simpler universal wiring setup, this kit contains PCB with overlay and electronic components.

As published in EPE  
February 2007




## THE 'FLEXITIMER'

**KA-1732 £6.00 plus postage & packing**

Switches a number of different output devices on and off at accurately timed intervals, ranging from a few seconds to a whole day. This kit includes PCB and all components. Requires 12-15VDC - recommended mains plugpack MP-3282 £4.25

As published in EPE September 2007

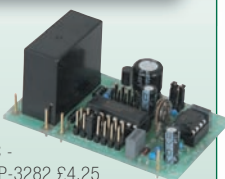

- Secure on-line ordering
- ALL prices in Pounds Sterling
- Minimum order ONLY £10

ORDER YOUR  
FREE CATALOGUE  
TODAY!



**Jaycar**  
Electronics

0800 032 7241

www.jaycarelectronics.co.uk



# POWER KITS FOR ELECTRONIC ENTHUSIASTS

## VOLTAGE MODIFIER KIT

**KC-5490 £23.25 plus postage & packing**

This kit intercepts and alters the signal from engine sensors that supply a voltage signal to the engine control unit (ECU). Restore correct air/fuel ratios after engine modifications, prevent engine boost cuts; or alter sensor signals for improved drivability. Requires hand controller for programming, RS232 cable and a suitable input signal. Kit includes PCB, case and electronic components.



**NEW TO EPE**

Recommended with this kit:  
Hand Controller Cat. KC-5386 £19.75  
RS232 Cable Cat. WC-7502 £4.00



## MARINE ENGINE SPEED EQUALISER KIT

**KC-5488 £11.75 plus postage & packing**

Avoid unnecessary noise and vibration in twin-engine boats. For optimum performance, both motors should run at exactly the same RPM. You can tune the engine speeds using the tachometer for each engine, however tachometers have an error of up to 5%. The Engine Speed Equaliser Kit takes the tachometer signals from each motor and displays the output on a meter that is centred when both motors are running at the same RPM. When there's a mismatch, the meter shows which motor is running faster and by how much. You simply adjust the throttles to suit. Short form kit only, requires moving coil panel meter (Cat. QP-5010 £5.25).

- 12VDC
- PCB and specified components



**NEW TO EPE**

## UHF REMOTE CONTROLLED MAINS SWITCH KIT

**KC-5462 £29.00 plus postage & packing**

Commercial remote control mains switches are generally limited to a range of 20m. This UHF system will operate up to 200m and is perfect for remote power control systems etc. Including a handheld controller, this kit is supplied with cases, screen printed PCBs, RF modules and electronic components. Requires replacement UK socket, see EPE January 2010 for details.

Featured in EPE Jan 2010



## FAST NI-MH BATTERY CHARGER KIT

**KC-5453 £12.50 plus postage & packing**

Ideal for RC enthusiasts who burn through a lot of batteries. Capable of handling up to 15 of the same type of Ni-MH or Ni-Cd cells. Build it to suit any size cells or cell capacity and set your own fast or trickle charge rate. Features overcharge protection and temperature sensing. Kit includes solder mask & overlay PCB, programmed micro and specified electronic components. Case, heatsink and battery holder not included.

Featured in EPE August 2009



## IMPROVED LOW VOLTAGE ADAPTOR

**KC-5463 £5.25 plus postage & packing**

A handy regulator to run a variety of devices such as CD or MP3 players from your car cigarette lighter sockets or even powered speakers from the power supply inside your PC. It will supply 3V, 5V, 6V, 9V, 12V or 15V and (when used with an appropriate input voltage and heatsink) deliver up to four amps at the selected output voltage. Kit includes screen printed PCB and all specified components. Heatsink not included.



## BATTERY ZAPPER MKIII

**KC-5479 £23.25 plus postage & packing**

Prolongs the life of your lead acid batteries. Like the original 2005 project, this circuit produces short high level bursts of energy to reverse the sulphation effect. The battery condition checker is no longer included and the circuit has been updated and revamped to provide more reliable, long-term operation. It still includes test points for a DMM and binding posts for a battery charger. Not recommended for use with gel batteries.

- PCB with solder mask and overlay components
- Screen printed machined case
- 6, 12 & 24VDC



## VOLTAGE MONITOR KIT

**KC-5424 £6.75 plus postage & packing**

Monitors either the battery voltage, airflow meter or oxygen sensor in your car. This versatile 12VDC kit features a 10 LED bar graph that indicates the measured voltage in 9-16V, 0-5V or 0-1V ranges. Features fast response time, high input impedance and auto dimming for night time driving. Kit includes PCB with overlay and all electronic components.


Featured in EPE November 2007



## VOLTAGE REGULATOR KIT

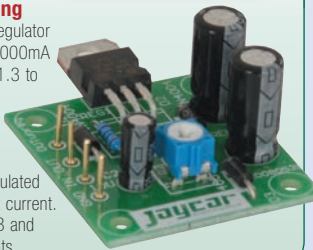**KC-5446 £5.00 plus postage & packing**

This handy voltage regulator can provide up to 1,000mA at any voltage from 1.3 to 22VDC. Ideal for experimental projects or as a mini bench power supply. Heatsink may be regulated depending on output current. Kit supplied with PCB and electronic components.



## SLA BATTERY HEALTH CHECKER

**KC-5482 £23.25 plus postage & packing**

Checks the health of your SLA batteries prior to charging or zapping with a simple LED condition indication of fair, poor, good etc. An ideal companion to our Battery Zapper MKIII.

- Overlay PCB and electronic components
- Silk-screened front panel and machined case included



## POST & PACKING CHARGES

| Order Value    | Cost |
|----------------|------|
| £10 - £49.99   | £5   |
| £50 - £99.99   | £10  |
| £100 - £199.99 | £20  |
| £200 - £499.99 | £30  |
| £500+          | £40  |

Max weight 12lb (5kg).  
Heavier parcels POA.  
Minimum order £10.

Note: Products are despatched from Australia, so local customs duty & taxes may apply.  
Prices valid until 31/03/2010

## HOW TO ORDER

- **ORDER ON-LINE:** [www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)
- **PHONE:** 0800 032 7241\*
- **FAX:** +61 2 8832 3118\*
- **EMAIL:** [techstore@jaycarelectronics.co.uk](mailto:techstore@jaycarelectronics.co.uk)
- **POST:** P.O. Box 107, Rydalmere NSW 2116 Australia
- **ALL PRICING IN POUNDS STERLING**
- **MINIMUM ORDER ONLY £10**

\*Australian Eastern Standard Time (Monday - Friday 09.00 to 17.30 GMT + 10 hours only)  
Expect 10-14 days for air parcel delivery

## FREE CATALOGUE

**Checkout Jaycar's extensive range**

**We have kits & electronic projects for use in:**

- Audio & Video
- Car & Automotive
- Computer
- Power
- Learning & Educational
- General Electronics Projects
- Gifts, Gadgets & Just for fun!
- Lighting
- Test & Meters

For your **FREE** catalogue log on to:  
[www.jaycarelectronics.co.uk/catalogue](http://www.jaycarelectronics.co.uk/catalogue)  
or check out the range at:  
[www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)



0800 032 7241

[www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)

**Jaycar**  
Electronics



|                    |          |       |         |       |            |        |
|--------------------|----------|-------|---------|-------|------------|--------|
| <b>4000 Series</b> | 74HC157  | £0.22 | 74LS367 | £0.21 | OP290GP    | £4.28  |
| 4000B              | 74HC158  | £0.23 | 74LS368 | £0.23 | OP297GP    | £4.64  |
| 4001B              | 74HC161  | £0.27 | 74LS373 | £0.43 | OP400GP    | £11.84 |
| 4002B              | 74HC162  | £0.45 | 74LS374 | £0.38 | OP495GP    | £8.69  |
| 4006B              | 74HC163  | £0.26 | 74LS378 | £0.62 | RC4136     | £1.00  |
| 4009UB             | 74HC164  | £0.20 | 74LS390 | £0.34 | SG3524N    | £0.82  |
| 4010B              | 74HC165  | £0.26 | 74LS393 | £0.33 | SG3543     | £0.88  |
| 4011B              | 74HC173  | £0.38 | 74LS395 | £0.26 | SSM2141P   | £3.21  |
| 4012B              | 74HC174  | £0.27 |         |       | SSM2142P   | £6.16  |
| 4013B              | 74HC175  | £0.35 |         |       | SSM2143P   | £3.78  |
| 4014B              | 74HC193  | £0.39 |         |       | TBA120S    | £1.04  |
| 4015B              | 74HC195  | £0.32 |         |       | TBA800     | £0.75  |
| 4016B              | 74HC240  | £0.37 |         |       | TBA820M    | £0.53  |
| 4017B              | 74HC241  | £0.32 |         |       | TDA1170S   | £4.80  |
| 4018B              | 74HC244  | £0.40 |         |       | TDA2004    | £2.24  |
| 4019B              | 74HC245  | £0.48 |         |       | TDA2003V   | £1.25  |
| 4020B              | 74HC251  | £0.30 |         |       | TDA2030AV  | £1.24  |
| 4021B              | 74HC253  | £0.25 |         |       | TDA2050V   | £2.51  |
| 4022B              | 74HC257  | £0.25 |         |       | TDA2611A   | £1.88  |
| 4023B              | 74HC259  | £0.29 |         |       | TDA2822A   | £0.79  |
| 4024B              | 74HC273  | £0.32 |         |       | TDA2653A   | £2.99  |
| 4025B              | 74HC299  | £0.61 |         |       | TDA648JN   | £2.57  |
| 4026B              | 74HC365  | £0.28 |         |       | TDA654JN   | £5.51  |
| 4027B              | 74HC367  | £0.38 |         |       | TD7112JN   | £1.97  |
| 4028B              | 74HC368  | £0.29 |         |       | TD7121JN   | £2.51  |
| 4029B              | 74HC373  | £0.35 |         |       | TD736JN    | £5.80  |
| 4030B              | 74HC374  | £0.34 |         |       | TD797JN    | £7.25  |
| 4035B              | 74HC390  | £0.37 |         |       | TD8111N    | £6.00  |
| 4040B              | 74HC393  | £0.36 |         |       | TD812AN    | £6.32  |
| 4041B              | 74HC393  | £0.36 |         |       | TD820AN    | £6.41  |
| 4042B              | 74HC393  | £0.36 |         |       | TD822AN    | £6.27  |
| 4043B              | 74HC393  | £0.36 |         |       | TD829JN    | £6.41  |
| 4046B              | 74HC395  | £0.27 |         |       | TD830AN    | £5.44  |
| 4047B              | 74HC397  | £0.22 |         |       | TD847JN    | £5.95  |
| 4048B              | 74HC398  | £0.46 |         |       | TD9696KN   | £7.73  |
| 4049B              | 74HC4002 | £0.46 |         |       | AD12020A   | £5.06  |
| 4049UB             | 74HC4017 | £0.24 |         |       | ADM222AA   | £3.55  |
| 4050B              | 74HC4020 | £0.36 |         |       | ADM232AA   | £3.55  |
| 4051B              | 74HC4040 | £0.29 |         |       | ADM485JN   | £2.97  |
| 4052B              | 74HC4049 | £0.31 |         |       | ADM666AN   | £2.72  |
| 4053B              | 74HC4051 | £0.50 |         |       | ADM690AN   | £5.13  |
| 4054B              | 74HC4052 | £0.34 |         |       | ADM691AN   | £5.48  |
| 4055B              | 74HC4053 | £0.22 |         |       | ADM695AN   | £6.48  |
| 4060B              | 74HC4060 | £0.23 |         |       | ADM699AN   | £5.58  |
| 4063B              | 74HC4075 | £0.32 |         |       | CA3130E    | £0.87  |
| 4066B              | 74HC4078 | £0.32 |         |       | CA3140E    | £0.63  |
| 4068B              | 74HC4511 | £0.64 |         |       | CA3240E    | £0.91  |
| 4069UB             | 74HC4514 | £0.84 |         |       | DG211CJ    | £1.25  |
| 4070B              | 74HC4538 | £0.41 |         |       | DG411DJ    | £2.00  |
| 4071B              | 74HC4543 | £0.90 |         |       | ICL7106CPL | £2.22  |
| 4072B              |          |       |         |       | ICL7107CPL | £2.71  |
| 4073B              |          |       |         |       | ICL7109CPL | £5.76  |

|                    |               |       |            |
|--------------------|---------------|-------|------------|
| <b>74HC Series</b> | 74LS138       | £0.33 | LP139YN    |
| 74HC00             | 74LS145       | £0.56 | LT1013CN8  |
| 74HC01             | £0.16 74LS148 | £0.64 | M34-1      |
| 74HC02             | £0.17 74LS151 | £0.29 | M34-2      |
| 74HC03             | £0.21 74LS156 | £0.36 | MAX202CPI  |
| 74HC04             | £0.21 74LS161 | £0.36 | MAX202CPI  |
| 74HC08             | £0.17 74LS158 | £0.27 | MAX220CPI  |
| 74HC10             | £0.21 74LS160 | £0.48 | MAX222CPI  |
| 74HC11             | £0.21 74LS161 | £0.32 | MAX232CPI  |
| 74HC14             | £0.18 74LS162 | £0.44 | MAX483CP   |
| 74HC20             | £0.28 74LS163 | £0.32 | MAX485CP   |
| 74HC27             | £0.16 74LS164 | £0.43 | MAX631AC   |
| 74HC30             | £0.22 74LS173 | £0.24 | MAX635A5C  |
| 74HC32             | £0.14 74LS175 | £0.30 | MAX1232CPI |
| 74HC42             | £0.36 74LS191 | £0.27 | MC1458N    |
| 74HC73             | £0.40 74LS192 | £0.60 | MC1488     |
| 74HC74             | £0.15 74LS193 | £0.50 | MC1489     |
| 74HC75             | £0.31 74LS195 | £0.24 | MC4558P    |
| 74HC85             | £0.23 74LS240 | £0.32 | MK484      |
| 74HC86             | £0.21 74LS241 | £0.32 | NE521N     |
| 74HC107            | £0.40 74LS243 | £0.30 | NE555N     |
| 74HC123            | £0.33 74LS244 | £0.41 | NE556N     |
| 74HC125            | £0.26 74LS245 | £0.45 | NE5532N    |
| 74HC126            | £0.46 74LS247 | £0.40 | NE5534N    |
| 74HC132            | £0.26 74LS251 | £0.24 | NE556N     |
| 74HC133            | £0.34 74LS257 | £0.34 | OP27CN     |
| 74HC137            | £0.30 74LS258 | £0.24 | OP90GP     |
| 74HC138            | £0.26 74LS266 | £0.14 | OP97FP     |
| 74HC139            | £0.31 74LS273 | £0.32 | OP113GP    |
| 74HC151            | £0.33 74LS279 | £0.24 | OP176GP    |
| 74HC153            | £0.30 74LS283 | £0.47 | OP177GP    |
| 74HC154            | £0.94 74LS365 | £0.21 | OP200GP    |

|        |                     |        |                          |                   |       |
|--------|---------------------|--------|--------------------------|-------------------|-------|
| £0.21  | OP290GP             | £4.28  | <b>Diodes</b>            |                   |       |
| £0.21  | OP297GP             | £4.64  |                          | 1N914             | £0.03 |
| £0.43  | OP400GP             | £11.81 |                          | 1N4001            | £0.04 |
| £0.38  | OP495GP             | £8.69  |                          | 1N4002            | £0.04 |
| £0.62  | RC4136              | £1.00  |                          | 1N4003            | £0.03 |
| £0.34  | SG3524N             | £0.82  |                          | 1N4004            | £0.03 |
| £0.33  | SG3543              | £6.88  |                          | 1N4005            | £0.04 |
| £0.26  | SSM2141P            | £3.21  |                          | 1N4006            | £0.04 |
|        | SSM2142P            | £6.16  |                          | 1N4007            | £0.03 |
|        | SSM2143P            | £3.78  |                          | 1N4148            | £0.03 |
| £0.40  | TBA120S             | £1.04  |                          | 1N4149            | £0.03 |
|        | TBA800              | £0.75  |                          | 1N5400            | £0.03 |
|        | TBA820M             | £0.53  |                          | 1N5401            | £0.03 |
| £23.04 | TD41170S            | £4.80  |                          | 1N5402            | £0.03 |
| £2.48  | TD4200A             | £2.24  |                          | 1N5403            | £0.03 |
| £2.48  | TD42003V            | £1.25  |                          | 1N5404            | £0.03 |
| £13.92 | TD42003AV           | £2.24  |                          | 1N5405            | £0.03 |
| £9.88  | TD42050V            | £2.51  |                          | 6A05              | £0.21 |
| £16.20 | TD42611A            | £1.89  |                          | 6A1               | £0.30 |
| £5.93  | TD42623A            | £2.99  |                          | 6A2               | £0.21 |
| £2.57  | TED3718DP           | £5.03  |                          | 6A4               | £0.21 |
| £5.51  | TEA5115             | £3.03  |                          | 6A6               | £0.21 |
| £1.97  | TL061CP             | £0.21  |                          | 6A8               | £0.30 |
| £2.51  | TL062CP             | £0.21  |                          | 6A10              | £0.30 |
| £5.80  | TL064CN             | £0.29  |                          | BA157             | £0.13 |
| £7.25  | TL071CN             | £0.20  |                          | BAT41             | £0.07 |
| £6.00  | TL072CN             | £0.20  |                          | BAT42             | £0.07 |
| £6.32  | TL074CN             | £0.25  |                          | BAT46             | £0.13 |
| £3.41  | TL081CN             | £0.17  |                          | BAT85             | £0.03 |
| £4.27  | TL082CN             | £0.32  |                          | BAV21             | £0.03 |
| £6.41  | TL084CN             | £0.37  |                          | BAW62             | £0.03 |
| £5.95  | TL7705ACP           | £0.82  |                          | BAX16             | £0.03 |
| £5.95  | TL7705ACP           | £0.63  |                          | BY127             | £0.13 |
| £5.06  | TS272CN             | £0.57  |                          | BY133             | £0.13 |
| £5.55  | TS555CN             | £0.26  |                          | OA91              | £0.50 |
| £5.55  | TM01F1P             | £5.60  |                          | OA200             | £0.30 |
| £2.97  | UA741CN             | £0.18  |                          | UF4001            | £0.03 |
| £2.72  | ULN2003A            | £0.38  |                          | UF4002            | £0.03 |
| £5.13  | ULN2004A            | £0.44  |                          | UF4003            | £0.03 |
| £6.48  | ULN2803A            | £0.45  |                          | UF4005            | £0.13 |
| £6.48  | ULN2804A            | £0.41  |                          | UF4006            | £0.13 |
| £5.87  | <b>EPROM's</b>      |        |                          | UF4007            | £0.13 |
| £0.63  | 24LC08BP            | £0.73  |                          | Zeners 2.7 to 33V | £0.03 |
| £0.91  | 24LC16BP            | £0.69  |                          | 500mW             | £0.30 |
| £1.25  | 27256-200           | £3.99  |                          | 1.3W              | £0.13 |
| £2.00  | 27C64A-15F          | £3.99  | <b>Bridge Rectifiers</b> |                   |       |
| £2.72  | 27C66B-15F6C2       | £3.99  |                          | 1A 50V            | £0.30 |
| £2.72  | 27C1001-15          | £3.98  |                          | 1A 100V           | £0.30 |
| £5.76  | 27C2001-15          | £4.41  |                          | 1A 200V           | £0.30 |
| £1.00  | 27C4001-10F6E9      | £1.00  |                          | 1A 600V           | £0.40 |
| £0.84  | 93C46N              | £0.28  |                          | 1A 800V           | £0.40 |
| £0.80  |                     |        |                          | 1.5A 50V          | £0.13 |
| £1.04  |                     |        |                          | 1.5A 100V         | £0.13 |
| £2.26  |                     |        |                          | 1.5A 200V         | £0.13 |
| £1.21  |                     |        |                          | 1.5A 400V         | £0.20 |
| £4.20  |                     |        |                          | 1.5A 600V         | £0.20 |
| £5.12  |                     |        |                          | 1.5A 800V         | £0.20 |
| £3.80  | AD420AN             | £25.38 |                          | 2A 100V           | £0.30 |
| £2.81  | AD7528JN            | £11.42 |                          | 2A 200V           | £0.30 |
| £4.48  | AD7545AK            | £14.04 |                          | 2A 400V           | £0.30 |
| £0.41  | AD7828KN            | £20.33 |                          | 2A 800V           | £0.30 |
| £0.44  | DAC08001            | £1.36  |                          | 2A 1000V          | £0.40 |
| £0.40  | ICL7109CPL          | £7.75  |                          | 3A 200V           | £0.30 |
| £2.71  |                     |        |                          | 3A 400V           | £0.40 |
| £1.00  | <b>uControllers</b> |        |                          | 3A 600V           | £0.30 |
| £0.90  | AT89C2051           | £6.38  |                          | 3A 1000V          | £0.30 |
| £0.90  | <b>PIC Series</b>   |        |                          | 4A 100V           | £0.70 |
| £0.20  | 12C508A04P          | £0.78  |                          | 4A 200V           | £0.80 |
| £0.18  | 12C509A04P          | £0.83  |                          | 4A 400V           | £0.80 |
| £0.12  | 16C54C04P           | £1.49  |                          | 6A 100V           | £0.90 |
| £0.36  | 16C54BJW            | £7.60  |                          | 6A 200V           | £0.90 |
| £1.37  | 16C56A-04P          | £1.56  |                          | 6A 400V           | £0.50 |
| £0.15  | 1F684-04P           | £3.14  |                          | 6A 600V           | £0.60 |
| £0.90  | 1F684-10P           | £4.16  |                          | 6A 800V           | £0.60 |
| £0.61  | 1F6627-04P          | £1.95  |                          | 8A 100V           | £0.90 |
| £1.10  | 1F6627-20IP         | £2.10  |                          | 8A 200V           | £1.00 |
| £0.21  | 1F7628-20IP         | £2.40  |                          | 8A 400V           | £1.20 |
| £0.90  | 1F6867-04SP         | £5.10  |                          | 8A 600V           | £1.30 |
| £1.98  | 1F6877-20P          | £4.80  |                          | 8A 1000V          | £1.40 |
|        |                     |        |                          | 25A 100V          | £1.00 |
|        |                     |        |                          | 25A 200V          | £1.00 |
|        |                     |        |                          | 25A 400V          | £1.00 |
|        |                     |        |                          | 35A 100V          | £1.80 |
|        |                     |        |                          | 35A 200V          | £1.80 |
|        |                     |        |                          | 35A 600V          | £2.90 |
|        |                     |        |                          | 35A 1000V         | £2.90 |
|        |                     |        |                          |                   |       |
|        |                     |        |                          |                   |       |
|        |                     |        |                          |                   |       |
|        |                     |        |                          |                   |       |



**Editorial Offices:**  
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road,  
Ferndown, Dorset BH22 9AU  
Phone: (01202) 873872. Fax: (01202) 874562.  
**Email:** enquiries@epemag.wimborne.co.uk  
**Web Site:** www.epemag.com  
See notes on **Readers' Technical Enquiries** below – we regret  
technical enquiries cannot be answered over the telephone.  
**Advertisement Offices:**  
Everyday Practical Electronics Advertisements  
Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU  
Phone: 01202 873872 Fax: 01202 874562  
**Email:** stewart.earn@wimborne.co.uk

## What would you like to see in EPE?

If you are reading this, then the chances are good that you are a practical person; someone who likes to understand the technical world around them, and who especially wants to get involved with electronic technology at a hands-on level. We certainly provide that hands-on aspect with our projects, but we also work hard to provide you with an understanding of design and theory.

In other words, we ensure EPE is a well-rounded magazine. It would be easy just to publish projects and let you the reader 'simply' follow the instructions, which, with care and a few troubleshooting tips, is more than likely to result in a successful build. However, that would miss the point of EPE, which is about enjoying electronics at a deeper level, and the very best way to do that is to really understand what is going on in a circuit. If you do appreciate the thinking behind a circuit's design, then not only can you improve or customise it to your own requirements, but also start on the rewarding process of designing and building your own original projects.

From 'Circuit Surgery', 'Practically Speaking' and 'Pic n' Mix' to our longer 'Teach-In' series, we aim to cover the full spectrum of contemporary electronic design – and we aim to do that for both beginners and those of you who are more experienced. We have a pretty good idea of what you enjoy; however, there is always room for improvement. In a discipline as large as electronics, it would be extraordinary if there weren't dozens of aspects of this versatile technology that we have neglected and which you would like to see covered. I briefly mentioned Nixie tubes last year, and knowledgeable readers sent in letters, emails, hyperlinks and just recently a project. That was a splendid (but not untypical) response, and the point of this Editorial is to remind you that we welcome your ideas for content – not just projects, but also explanations of design techniques, from analogue electronics to PIC software debugging.

So, do write in and let us know what you would like to see in your magazine.

*Min*

### AVAILABILITY

Copies of EPE are available on subscription anywhere in the world (see opposite) and from all UK newsagents (distributed by SEYMOUR). EPE can also be purchased from retail magazine outlets around the world. An Internet online version can be purchased and downloaded for just \$18.99US (approx £13) per year, available from [www.epemag.com](http://www.epemag.com)

### SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £19.95, 12 months £37.90, two years £70.50; Overseas: 6 months £23.00 standard air service or £32.00 express airmail, 12 months £44.00 standard air service or £62.00 express airmail, 24 months £83.00 standard air service or £119.00 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$18.99US (approx £13) for one year available from [www.epemag.com](http://www.epemag.com).

Cheques or bank drafts (in £ sterling only) payable to Everyday Practical Electronics and sent to EPE Subs. Dept., Wimborne Publishing Ltd. Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872. Fax: 01202 874562. **Email:** subs@epemag.wimborne.co.uk. Also via the Web at: [www.epemag.com](http://www.epemag.com). Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

### BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue PVC, printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days, but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date, valid from date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK website. **Overseas customers** – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

## VOL. 39 No. 3 MARCH 2010

**Editor:** MATT PULZER

**Consulting Editor:** DAVID BARRINGTON

**Subscriptions:** MARILYN GOLDBERG

**General Manager:** FAY KEARN

**Editorial/Admin:** (01202) 873872

**Advertising and Business Manager:**

STEWART KEARN (01202) 873872

**On-line Editor:** ALAN WINSTANLEY

**EPE Online** (Internet version) Editors:

CLIVE (Max) MAXFIELD and ALVIN BROWN

**Publisher:** MIKE KENWARD

### READERS' TECHNICAL ENQUIRIES

**Email:** techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

### PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in EPE employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

### COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

### ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts. The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

### TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



# NEWS

A roundup of the latest Everyday  
News from the world of  
electronics



## LED TV projector technology By Barry Fox

**D**emonstrations of competing LED projectors highlight the compromises designers now face when using the new solid-state light-emitting technology instead of conventional UHP, or ultra high performance, mercury arc lamps.

The UHP system was developed by Philips in 1995 and generates very high light output from a small lamp. But life is limited to a few thousand hours at best, with many projectors coming with only a three month warranty on the lamp. Plus, mercury content makes disposal of dead lamps an eco challenge.

UHP lamps can take up to an hour after switch on to give true colour, and cannot be quickly switched on and off. LED lamps last around 70,000 hours, are mercury-free for easy disposal and can be switched on and off instantly. LEDs convert electricity to light more efficiently and achieve steady colour state in 10 seconds, with a wider range of colours. No mechanical iris is needed for near infinite contrast ratio, and because separate red, green and blue LEDs are used, there is no DLP colour wheel, so no risk of 'rainbow effect' – the colour strobing which viewers may see if they move their head rapidly while watching the projected picture.

But LEDs are expensive, light output is less than for UHP lamps, and extreme cooling is needed if the projector is to fill a large screen.

Runco's Holger Graeff, claims its new QuantumColor 1080p single-chip LED projector, the Q-750 (costing around £18,000), uses 70% less power than lamp-based projection. Power consumption varies up to 250W, with 140W for typical use.

"Lampless LED is the future of video projection" says Planar CEO Gerry Perkel.

"An LED lampless light source is clearly the next step in front projection" says Joel Silver, founder and president of the Imaging Science Foundation.

Runco recommends a screen width of 72 inches to 92 inches, with a maximum of 108 inches. Graeff told us: "LED is not perfect yet. LED technology is developing. It's a beginning. And if you are happy with 100 inches in a dark room you can be happy with LED. The colours are so bright you don't notice that the picture is not so bright."

Room lights were completely dimmed to show clips from Cars, US football coverage, Dark Knight and Elton John in concert on a 92inch screen – with good results.

### Different approach

SIM2, the Italian manufacturer, has adopted a different approach with the 1080p MICO 50 LED projector (£15,000). Whereas Runco uses conventional fan air cooling

for its LEDs, SIM2 uses liquid cooling to increase power consumption to 370W, while still claiming a lifetime 'well above 100,000 hours'.

Demonstrating the SIM2 LED projector on the large screen of the British Film Institute's screening room in London, specialist journalists at first thought UK Managing Director Alan Roser was joking when he explained why the single-chip HD projector was as big as a carry-on suitcase – "it needs water cool plumbing", he said.

But after an impressive demonstration of *Star Trek*, he took off the projector lid and showed he wasn't jesting. The three discrete LEDs (red, green and blue) generate so much heat that a liquid cooling system, which looks just like a miniature car radiator with pumps, pipes and fans, is needed.


### Footnote

At the Runco demonstration in a London bar a few days later, Holger Graeff declined our request to remove the top of the Runco projector; he attributed the large size of the unit – similar to the SIM2 projector – to the large optics. The air coming from the side vents was just pleasantly warm, with no evidence of high temperatures inside the box.
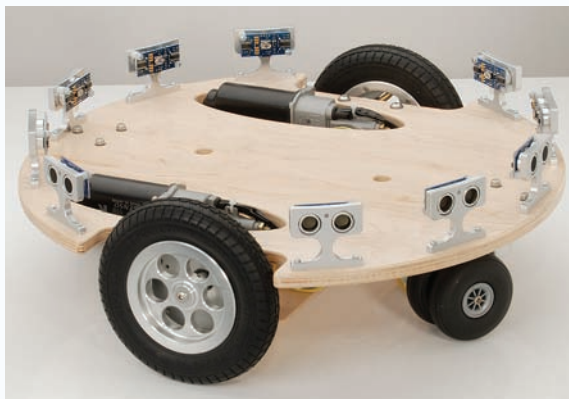
## Robot Base Kit

A Robot Base Kit has been introduced by Parallax. This is a plywood platform kit for the 12V Motor Mount and Wheel Kit (#27971) and the Caster Wheel Kit (#28971). This kit allows users to build a nearly complete robot and then add on their choice of processor and sensors (sold separately).

Also from Parallax is the Programming & Customizing the Multicore Propeller Microcontroller: Official Guide. The book begins with an introduction to the Propeller chip's architecture and Spin



programming language, debugging techniques, and sensor interfacing.

The remainder of the book introduces eight diverse and powerful applications, ending with a speech synthesis demonstration written by the Propeller chip's inventor, Chip Gracey. Numerous illustrations and example programs accompany each application. Example source code and other related resources are available for free download from <ftp://ftp.propeller-chip.com/PCMPProp>.

More information is available from [www.Parallax.com](http://www.Parallax.com)





## Touchscreen teaching

Much to Dulwich Village Infants' and Hobbs Hill Primary's delight, the ASUS Eee Top PCs proved to be a huge hit. Young pupils were more at ease with using the Eee Top PC's touchscreen than a traditional mouse, and this proved highly motivating.

"The Eee Tops were so popular that children were eager to get into class early to use them", says Sheila Kirrane, ICT coordinator at Dulwich Village Infants. "The

children seemed to be more confident when using them and not afraid to make mistakes, as they were able to rectify them without adult intervention."

Hobbs Hill's nursery also liked the Eee Top PC's unique approach. "I can see a lot of potential for having these computers in classes where mouse control is more difficult", says Miss King, Hobbs Hill's Assistant Nursery Manager. "Playing maths games or interacting with particular websites in this way would be a great advantage."

The Eee Top PC's touchscreen also offered one unexpected advantage, as Hobbs Hill year 6 pupil Laurie, age 6, points out: "Less arguing about the mouse when working in pairs!"

Although initially sceptical about netbooks, Hobbs Hill Primary soon saw the appeal of the ASUS Eee PCs. Graham King, ICT coordinator for Hobbs Hill Primary, explains: "The Eee PCs were easy to handle and were seen as potentially becoming a tool just like a calculator: I could see these being used on school journeys when we stay at a youth hostel."

The ease with which very young children could carry the lightweight Eee PCs also meant that they weren't confined to use in just one part of the classroom.

"The fact that they are so manageable and robust was a big plus, and they can

easily be used outside or transported to another part of the room", says Sheila Kirrane. "This encouraged real collaboration and plenty of 'on task' discussion."

Both schools were taken aback by the extremely positive reactions of their pupils to the ASUS computers and Dulwich Village was particularly smitten with the Eee Top PC.


"The Eee Top PCs gave greater independence to our learners and they became more familiar with touchscreen computers. The children's enthusiasm seemed to be reignited!" says Sheila Kirrane.

Ben, age 5, makes his appreciation of the ASUS Eee Top PC very clear: "I love this computer! It is easy to switch on and I don't need a teacher to help me."

It was a similar story at Hobbs Hill. Graham King says: "Perhaps the biggest impact was the enthusiasm with which the children responded to them. They saw them very much as something they could take ownership of."

You can follow ASUS on Twitter: <http://www.twitter.com/asusuk>

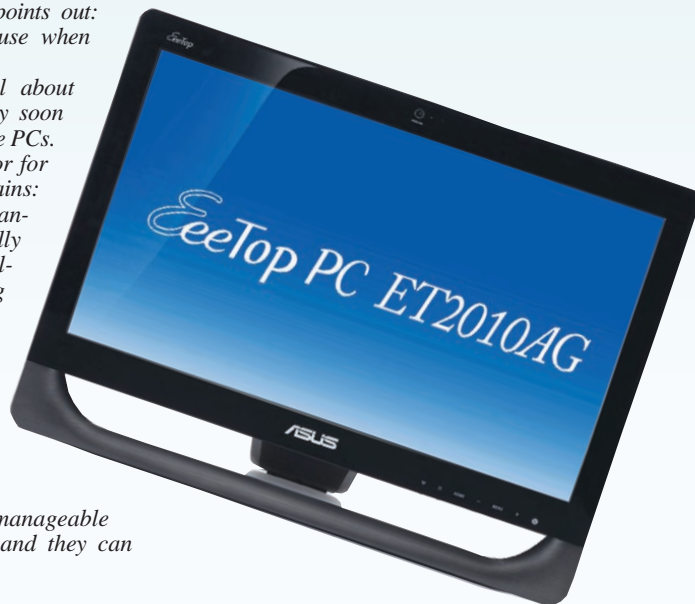Detailed stockist information can be found on the following link: [http://uk.asus.com/wheretobuy\\_new.aspx?slLanguage=en\\_GB&country=1339](http://uk.asus.com/wheretobuy_new.aspx?slLanguage=en_GB&country=1339)



**C**OMPUTER supplier ASUS wanted to explore the potential of the effective use and deployment of some of the Eee family of touchscreen computers within the infant and primary school environments. And whether or not this would have any impact on how younger children play and learn within the classroom.

The partner schools selected for the trial were Hobbs Hill Primary and Dulwich Village Church of England Infants School (DVIS). Hobbs Hill is the larger of the two, with 476 pupils from reception (age 4) to year 6 (age 11). DVIS has 270 pupils, from reception to year 2 (age 7).

Each school delivers its ICT (Information and Communication Technologies) curriculum via computers inside classrooms and dedicated computer suites. All teaching staff are involved in ICT teaching to some extent, and exploring new learning opportunities through ICT is seen as an important area. As Graham King, ICT coordinator for Hobbs Hill Primary, explains: "The challenge for us is to find more innovative ways of using ICT, rather than just create more impressive PowerPoint presentations."

ASUS Eee Top PCs were installed in Dulwich Village Infants' reception (ages four to five), year 1 (ages five to six) and year 2 (ages six to seven) classes. Eee PCs were also placed into one reception class. ASUS Eee PCs were provided for every pupil in one year 5 (ages 10 to 11) class at Hobbs Hill Primary, along with one Eee Top PC. A second Eee Top PC was also used in a Nursery class.

## USB flash drive kill pill

Kill Pill from Swedish company Cryptzone ([www.cryptzone.com](http://www.cryptzone.com)) makes it possible for a user or administrator to, at any time through the Internet, lock or wipe the contents on a lost or stolen USB flash drive wherever it is in the world.

Protecting USB flash drives has become a high priority for many companies. With the new version of Secured eUSB, Cryptzone can offer a new level of security which meets the current requirements for existing and upcoming

information security laws throughout the world.

Besides the Kill Pill feature, Secured eUSB contains a long list of new functionality and improvements in order to meet the growing demand for high security for businesses today. Among the new features are 'Synchronized Login' to Microsoft Active Directory and DCR – Data Content Reporting.

Each USB flash drive has built-in intelligence to report in real-time, when the flash drive was created, what files are on the flash

drive, where the files came from (path and computer), what was done with the files and, most importantly, what user accessed the drive and what did he/she do with the files. Additionally, the reports include an asset inventory listing of Active Directory members that indicates exactly the number of USB flash drives owned, brand/model of the drive, when it was created and much more.

The Secured eUSB solution can encrypt any brand/model of USB flash drive and even deal with flash drives that already contain data.



Here's a handy piece of test gear you can build for yourself – a Digital LC Meter for measuring inductance and capacitance over a wide range. It's based on an ingenious measurement technique, delivers surprising accuracy and is easy to build.

**M**ANY modern DMM's (digital multimeters) have capacitance measuring ranges, especially the up-market models. So it's not hard to measure the value of capacitors, as long as their value is more than about 50pF or so.

Below that level, DMMs are not very useful for capacitance measurements. Dedicated digital capacitance meters are available, of course, and they generally measure down to a few pF or so. But if you want to measure things like stray capacitance, they too are of limited use.

It's even worse when it comes to measuring inductors. Very few DMMs

have the ability to measure inductance, so in many cases you have to use either an old-type inductance bridge or a 'Q' meter. Both of these are basically analogue instruments, and don't offer either high resolution or particularly high accuracy.

### Micro solution

It's different for professionals, who for the last 20 years or so have been able to use digital LCR meters. These allow you to measure almost any passive component quickly and automatically, often measuring not just their primary parameter (like inductance or capacitance) but one or more secondary parameters

as well. However, many of these instruments carry a hefty price tag, keeping them well out of reach for many of us.


Fortunately, thanks to microcontroller technology, that situation has changed somewhat in the last few years, with much more affordable digital instruments now becoming available. These include both commercial and DIY instruments, along with the unit described here.

### Main features

As shown in the photographs, our new Digital LC Meter is very compact. It's easy to build, has an LCD readout and fits snugly inside a UB3-size utility box. It won't break the bank either – we estimate that you should be able to build it for less than £40.

Despite its modest cost, it offers automatic direct digital measurement over a wide range for both capacitance (C) and inductance (L) with 4-digit resolution. In fact, it measures capacitance from just 0.1pF up to 800nF and inductance from 10nH to 70mH.



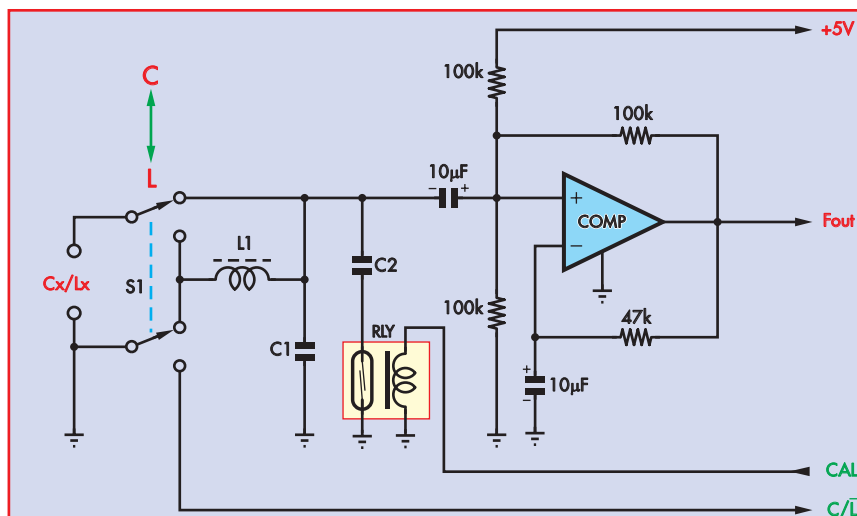

**Fig.1:** the circuit uses a wide-range test oscillator, the frequency of which varies when an unknown inductor (Lx) or capacitor (Cx) is connected. This oscillator is in turn monitored using a microcontroller which accurately calibrates the unit and measures the change in oscillator frequency. The microcontroller then calculates the unknown component's inductance or capacitance and displays the result on an LCD.

## HOW IT WORKS: THE EQUATIONS

### (A) In calibration mode

- (1) With just L1 and C1:  $F1 = \frac{1}{2\pi \cdot \sqrt{L1 \cdot C1}}$
- (2) With C2 added to C1:  $F2 = \frac{1}{2\pi \cdot \sqrt{L1 \cdot (C1 + C2)}}$
- (3) From (1) and (2), we can find C1:  

$$C1 = \frac{F2^2}{(F1^2 - F2^2)} \cdot C2$$
- (4) Also from (1) and (2), we can find L1:  

$$L1 = \frac{1}{4\pi^2 \cdot F1^2 \cdot C1}$$

### (B) In measurement mode

- (5) When Cx is connected:  $F3 = \frac{1}{2\pi \cdot \sqrt{L1 \cdot (C1 + Cx)}}$   
so  $Cx = C1 \cdot \left( \frac{F1^2}{F3^2} - 1 \right)$
- (6) Or when Lx is connected:  

$$F3 = \frac{1}{2\pi \cdot \sqrt{(L1 + Lx) \cdot C1}}$$
  
so  $Lx = L1 \cdot \left( \frac{F1^2}{F3^2} - 1 \right)$

**NOTE:** F2 & F3 should always be lower than F1

Measurement accuracy is also surprisingly good, at better than  $\pm 1\%$  of reading.

It operates from 9V to 12V DC, drawing an average current of less than 20mA. This means that it can be powered from either a 9V alkaline battery inside the case, or from an external plugpack supply.

## How it works

The meter's impressive performance depends on an ingenious measurement technique which was developed about 12 years ago by Neil Hecht, of Washington state in the US. It uses a wide-range test oscillator whose frequency is varied by connecting the unknown inductor or capacitor you're measuring. The resulting change in frequency is measured by a microcontroller, which then calculates the component's value and displays it directly on an LCD readout.

So there are basically only two key parts in the meter: (1) the test oscillator itself and (2) the microcontroller which measures its frequency (with and without the component being measured) and calculates the component's value.

To achieve reliable oscillation over a wide frequency range, the test oscillator is based on an analogue comparator with positive feedback around it – see Fig.1. This configuration has a natural inclination to oscillate because of the

very high gain between the comparator's input and output.

When power (+5V) is first applied, the comparator's non-inverting (+) input is held at half the supply voltage (+2.5V) by a bias divider formed by two 100kΩ resistors. However, the voltage at the inverting input is initially zero because the 10µF capacitor at this input needs time to charge via the 47kΩ feedback resistor. So, with its non-inverting input much more positive than its inverting input, the comparator initially switches its output high (ie, to +5V).

Once it does so, the 10µF capacitor on the inverting input begins charging via the 47kΩ resistor and so the voltage at this input rises exponentially. As soon as it rises slightly above the +2.5V level, the comparator's output suddenly switches low.

This low voltage is fed back to the comparator's non-inverting input via a 100kΩ feedback resistor. It is also coupled through the 10µF input

capacitor to a tuned circuit formed by inductor L1 and capacitor C1. This makes the tuned circuit 'ring' at its resonant frequency.

## Oscillation

As a result, the comparator and the tuned circuit now function as an oscillator at that resonant frequency. In effect, the comparator effectively functions as a 'negative resistance' across the tuned circuit, to cancel its losses and maintain oscillation.

Once this oscillation is established, a square wave of the same frequency appears at the comparator's output and it is this frequency (F<sub>out</sub>) that is measured by the microcontroller. In practice, before anything else is connected into the circuit, F<sub>out</sub> simply corresponds to the resonant frequency of L1, C1 and any stray capacitance that may be associated with them.

When power is first applied to the meter, the microcontroller measures

## Specifications

- **Inductance Range:** from about 10nH to over 70mH (4-digit resolution)
- **Capacitance Range:** from about 0.1pF to over 800nF (4-digit resolution)
- **Range Selection:** automatic (capacitors must be non-polarised types)
- **Sampling Rate:** approximately five measurements per second
- **Expected Accuracy:** better than  $\pm 1\%$  of reading,  $\pm 0.1\text{pF}$  or  $\pm 10\text{nH}$
- **Power Supply:** 9V to 12V DC at less than 20mA (non-backlit LCD module). Can be operated from an internal 9V battery or an external plugpack.

## Parts List – High-accuracy Digital LC Meter

|  |   |
|--|---|
| *1 PC board, code 745 (Main), size 125 × 58mm                        | 1 M3 nut (metal)  |
| *1 PC board, code 746 (Adpt.), size 36 × 16mm                        | 2 M2 × 6mm machine screws (for S1)                            |
| *1 PC board, code 747 (Bar), size 41 × 21mm                          | 4 M3 × 12mm nylon screws                                      |
| 1 UB3-size box, 130 × 68 × 44mm                                      | 8 M3 nylon nuts   |
| 1 16×2 LCD module (Jaycar QP-5515 or QP-5516 or similar – see panel) | 4 M3 nylon nuts with integral washers                         |
| 1 5V 10mA DIL reed relay (Jaycar SY-4030)                            | 1 9V battery-snap lead  |
| 1 100μH RF inductor (L1)   | 1 10kΩ horizontal trimpot (VR1)                               |
| 1 4.0MHz crystal, HC-49U   | <b>Semiconductors</b>   |
| 1 DPDT subminiature slider switch (S1)                               | 1 PIC16F628A microcontroller, pre-programmed – see text (IC1) |
| 1 SPST momentary contact pushbutton switch (S2)                      | 1 7805 +5V regulator (REG1)                                   |
| 1 SPDT mini toggle switch (S3)                                       | 1 1N4148 signal diode (D1)                                    |
| 1 18-pin DIL IC socket   | 1 1N4004 1A rect. diode (D2)                                  |
| 1 2.5mm PC-mount DC connector  | <b>Capacitors</b>   |
| 1 4×2 section of DIL header strip                                    | 1 22μF 16V radial elect.                                      |
| 1 7×2 section of DIL header strip                                    | 2 10μF 16V radial elect.                                      |
| 1 jumper shunt   | 1 10μF 16V tantalum   |
| 1 binding-post/banana socket, red                                    | 1 100nF monolithic  |
| 1 binding-post/banana socket, black                                  | 2 1nF MKT or polystyrene (1% if possible) (C1, C2)            |
| 2 PC terminal pins, 1mm dia  | 2 33pF NPO ceramic  |
| 4 M3 × 15mm tapped spacers   | <b>Resistors</b> (0.25W 1% metal film)                        |
| 4 M3 × 6mm csk head machine screws                                   | 3 100kΩ      2 4.7kΩ  |
| 5 M3 × 6mm pan head machine screws                                   | 1 68kΩ      4 1kΩ   |
|  | 1 47kΩ  |
|  | * Available as a set from the <i>EPE PCB Service</i>          |

this frequency (F1) and stores it in memory. It then energises reed relay RLY1, which switches capacitor C2 in parallel with C1 and thus alters the oscillator frequency (ie, it lowers it). The microcontroller then measures and stores this new frequency (F2).

Next, the microcontroller uses these two frequencies, plus the value of C2 to accurately calculate the values of both C1 and L1. If you're interested, the equations it uses to do this are shown in the top (Calibration Mode) section of the box titled 'How it works: the equations'.

Following these calculations, the microcontroller turns relay RLY1 off again to remove capacitor C2 from the circuit, allowing the oscillator frequency to return to F1. The unit is now ready to measure the unknown inductor or capacitor (Cx or Lx).

### Into the unknown

As shown in Fig.1, the unknown component is connected across the test terminals. It is then connected to the

oscillator's tuned circuit via switch S1.

When measuring an unknown capacitor, S1 is switched to position 'C' so that the capacitor is connected in parallel with C1. Alternatively, for an unknown inductor, S1 is switched to position 'L' so that the inductor is connected in series with L1.

In both cases, the added values of Cx or Lx again causes the oscillator frequency to change, to a new frequency (F3). As with F2, this will always be lower than F1. So, by measuring F3 as before, and monitoring the position of S1 (which is done via the C/L connection at IC1 pin 12), the microcontroller can calculate the value of the unknown component using one of the equations shown in the lower section of the equations box – ie, the section labelled 'In measurement mode'.

From these equations, you can see that the micro has some fairly solid 'number crunching' to do, both in the calibration mode when it calculates the values of L1 and C1, and then

in the measurement mode, when it calculates the value of Cx or Lx. Each of these values needs to be calculated to a high degree of resolution and accuracy. To achieve this, the micro's firmware needs to make use of some 24-bit floating point maths routines.

### Circuit details

How this ingenious yet simple measurement scheme is used to produce a practical LC meter can be seen from the full circuit diagram of the High-Accuracy Digital LC Meter, shown in Fig.2. It's even simpler than you might have expected, because there's no separate comparator to form the heart of the measurement oscillator. Instead, we're making use of a comparator that's built into the microcontroller (IC1) itself.

As shown, microcontroller IC1 is a PIC16F628A and it actually contains two analogue comparators which can be configured in a variety of ways. Here we are using comparator 1 (CMP1) as the measurement oscillator. Comparator 2 (CMP2) is used only to provide some additional 'squaring up' of the output from CMP1, and its output then drives the internal frequency counting circuitry.

The oscillator circuitry is essentially unchanged from that shown in Fig.1. Note that IC1 controls relay RLY1 (which switches calibrating capacitor C2 in and out of circuit) via its I/O port B's RB7 line (pin 13). Diode D1 prevents the micro's internal circuitry from being damaged by inductive spikes when RLY1 switches off.

In operation, IC1 senses which position switch S1 is in using RB6 (pin 12). This is pulled high internally when S1b is in the 'C' position, and low when S1b is in the 'L' position. Crystal X1 (4MHz) sets the clock frequency for IC1, while the associated 33pF capacitors provide the correct loading to ensure reliable starting of the clock oscillator.

The results of IC1's calculations are displayed on a standard 2×16 line LCD module. This is driven directly from the micro itself, via port pins RB0 to RB5. Trimpot VR1 allows the LCD contrast to be optimised.

### Firmware and link functions

The firmware in IC1 is designed to automatically perform the calibration function just after initial start-up. However, this can also be performed at any other time using switch S2.



Pressing this switch simply pulls the micro's MCLR pin (4) down, so that the micro is forced to reset and start up again, recalibrating the circuit in the process.

Links LK1 to LK4 are not installed for normal use, but are used for the initial setting up, testing and calibration. As shown, these links connect between RB3 to RB0 and ground respectively.

For example, if you fit LK1 and then press S2 to force a reset, the micro will activate RLY1 (to switch capacitor C2 into circuit) and measure oscillator frequency F2. This is then displayed on the LCD.

Similarly, if you fit LK2 and press S2, the micro simply measures the initial oscillator frequency (F1) and displays this on the LCD. This allows you to not only make sure that the oscillator is operating, but also you can check its frequency as well. We'll have more to say about this later.

Links LK3 and LK4 allow you to perform manual calibration 'tweaks' to the meter. This is useful if you have access to a capacitor whose value is very accurately known (because it has been measured using a full-scale LCR meter, for example).

With LK3 fitted, the capacitance reading decreases by a small amount each time it makes a new measurement (which is about five times per second). Conversely, if LK4 is fitted instead, the microcontroller increases the capacitance reading by a small increment each time it performs a new measurement.


Each time a change is made, the adjustment factor is stored in the micro's EEPROM, and this calibration value is then applied to future measurements. Note also that although the calibration is made using a 'standard' capacitor, it also affects the inductance measurement function.



In short, the idea is to fit the jumper to one link or the other (ie, to LK3 or LK4) until the reading is correct. The link is then removed.

As mentioned above, links LK1 to LK4 are all left out for normal operation. They're only used for troubleshooting and calibration.

## Power supply


Power for the circuit is derived from an external 9V to 12V DC source. This can come from either a plugpack supply or from an internal 9V battery. The switched DC power input socket

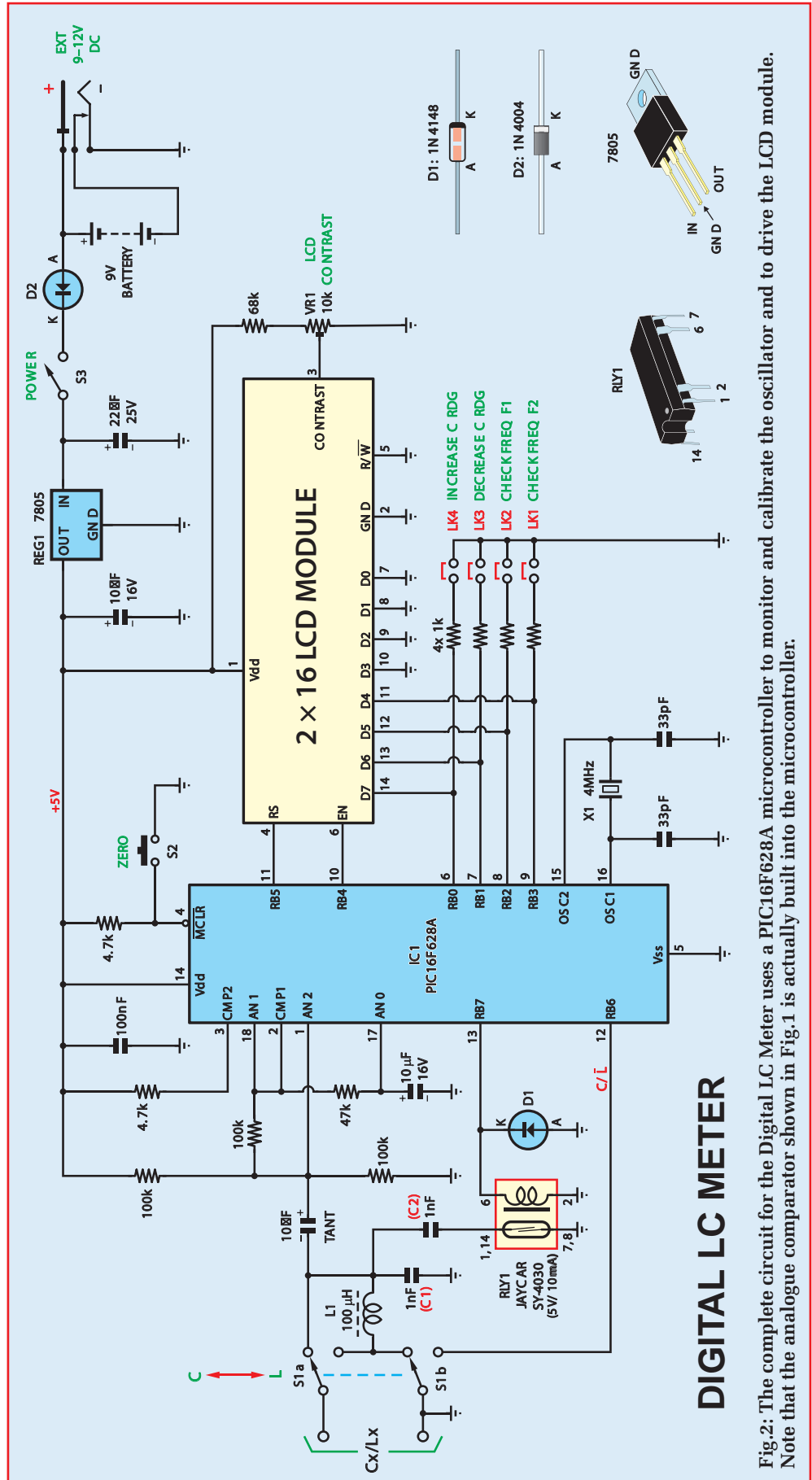

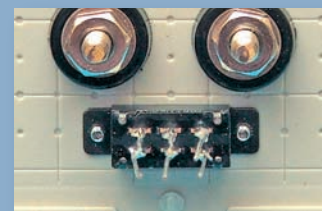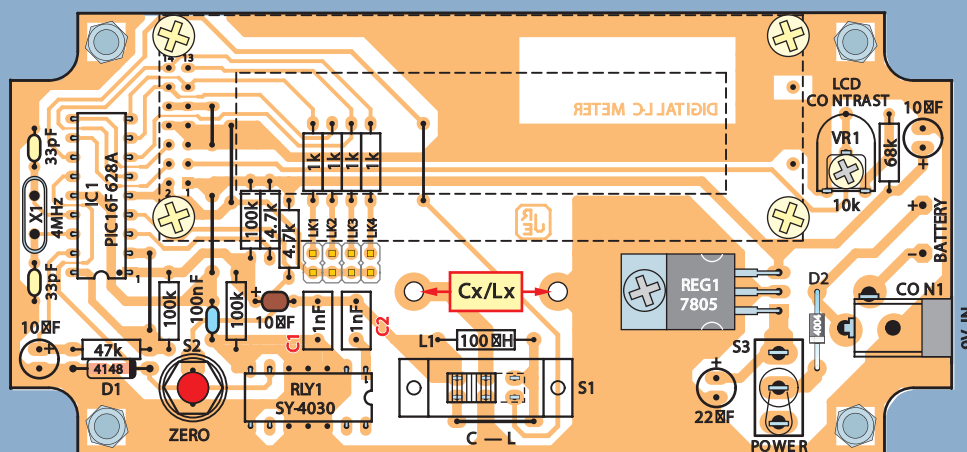

**Fig.3:** follow this layout diagram to build the Digital LC Meter, but don't solder in the switches or the test terminals until after these parts have been mounted on the front panel. The 2-way pin headers for links LK1-LK4 are installed on the copper side of the board – see text.

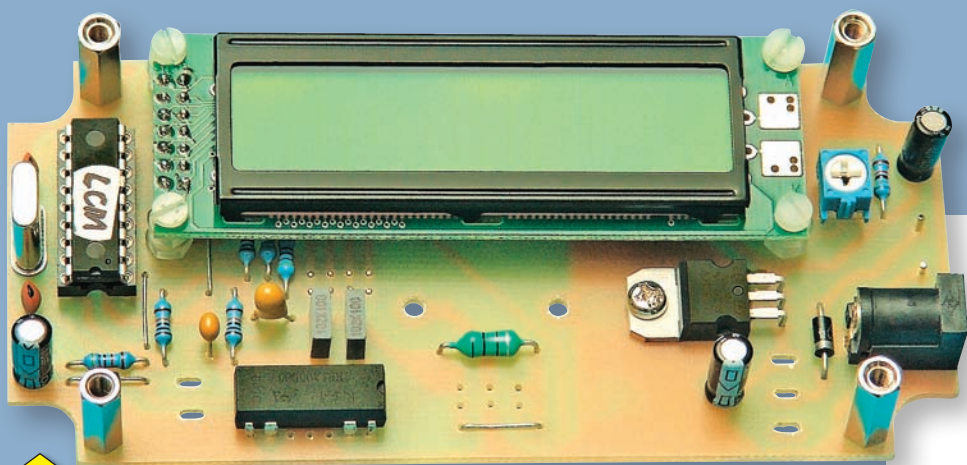Part of the back of the case lid before the PC board assembly is attached, showing the 'extension leads' soldered to slide switch S1's terminals.



The PC board assembly is attached to the case lid using M3 × 15mm spacers and M3 × 6mm countersink (csk) machine screws. Make sure that the assembly is secure before soldering the switch lugs and test terminals.

automatically disconnects the battery when the plugpack supply is connected.

The incoming DC rail is fed via reverse polarity protection diode D2 and power switch S3 to regulator REG1 – a standard 7805 device. The resulting +5V rail at REG1's output is then used to power IC1 and the LCD module.

## Software

The software files are available via the *EPE* Library site, accessed via **[www.epemag.com](http://www.epemag.com)**. Pre-programmed PICs are available from

Magenta Electronics – see their advert in this issue for contact details.

## Construction




 
 
Because it uses so few parts, the unit is very easy to build. All the parts, except for switches S1 to S3 and the Cx/Lx input terminals, are mounted on a PC board, code 745, measuring 125 × 58mm. This board is available from the *EPE PCB Service*.

The LCD module connects to a 7×2 DIL pin header at one end of the board, and is supported at either end using M3 nylon screws and nuts.

- Fig.3 shows the parts layout on the PC board. Here's the suggested order of fitting the components to the PC board:
- 1) Fit DC power connector CON1 and the two 1mm PC board terminal pins for the internal battery connections.
  - 2) Fit the six wire links, four of which go under where the LCD module is later fitted. Don't forget the link immediately below switch S1.
  - 3) Install the 4x2 DIL pin header used for links LK1 to LK4. **Note that this item must be mounted on the copper side of the board (not on the top),** so that a jumper can later be fitted to any of the links when the board assembly is attached to the box lid).

To install this header, just push the ends of the longer sides of the pins into the board holes by 1-2mm, then solder them carefully to the pads. That done, push the plastic strip down the pins so that it rests against the solder joints,

## Table 1: Resistor Colour Codes

|   | No. | Value | 4-Band Code (1%)           | 5-Band Code (1%)                |
|---|-----|-------|----------------------------|---------------------------------|
|  | 3   | 100kΩ | brown black yellow brown   | brown black black orange brown  |
|  | 1   | 68kΩ  | blue grey orange brown     | blue grey black red brown       |
|  | 1   | 47kΩ  | yellow violet orange brown | yellow violet black red brown   |
|  | 2   | 4.7kΩ | yellow violet red brown    | yellow violet black brown brown |
|  | 4   | 1kΩ   | brown black red brown      | brown black black brown brown   |



leaving the clean outer ends of all pins free to take a jumper shunt.

- 4) Fit a 7×2 DIL pin header for the LCD module connections. This header is fitted to the top of the PC board in the usual way.
- 5) Install the 11 resistors, seven of which go under the LCD module. Table 1 shows the resistor colour codes, but you should also check each resistor using a DMM before soldering in position on the board.
- 6) Install trimpot VR1, followed by inductor L1 and reed relay RLY1.
- 7) Fit the five non-polarised capacitors, followed by the 10μF tantalum, the two 10μF radial electrolytics and the 22μF radial electrolytic. Note that the tantalum capacitor and the electrolytics are polarised, so take care with their orientation.
- 8) Install DIL relay RLY1, the 18-pin socket for IC1 and the 4MHz crystal X1. Follow these parts with diodes D1 and D2 and regulator REG1.  
Note that the regulator's leads are bent downwards through 90° 6mm from the body, so that they pass through the holes in the board. Before soldering the leads, secure the metal tab to the PC board using an M3 × 6mm machine screw and nut.
- 9) Secure the LCD module to the PC board, using four M3 × 12mm cheesehead nylon screws and 12 nuts (three on each screw). Fig.4 shows the details.  
At each mounting point, two plain nuts act as spacers between the module and the PC board, while a third nut with an integral washer is fitted to secure the assembly under the PC board. Note that when you're fitting the module to the top of the board, it should be lowered carefully so that the holes at the lefthand end slip down over the pins of the 7×2 DIL strip fitted earlier.
- 10) Solder the 14 pin connections on the top of the LCD module using a fine-pointed iron.
- 11) Plug the programmed PIC16F628A (IC1) into its socket, then fit four M3 × 15mm tapped spacers to the PC board mounting points. Secure these spacers using M3 × 6mm pan-head screws.

That completes the board assembly. It can now be placed to one side while you work on the case.

## Preparing the case

As shown in the photographs, the PC board assembly is mounted on the lid of a standard UB3-size box.

If you're building the Digital LC Meter from a kit, the plastic case will probably be supplied with all holes drilled and with screen-printed lettering for the front panel. If so, it will be simply a matter of fitting the switches and binding 'test' posts to the lid.

Note that slide switch S1 is secured using two M2 × 6mm machine screws, while switches S2 and S3 are mounted using their own mounting nuts and lockwashers. The binding posts mount to the panel in the same way.

If you have to drill the case holes yourself, you can use a photocopy of the front panel artwork (Fig.5) as a drilling template. In addition, you will have to drill/ream a 10mm diameter hole in the righthand end of the box to give access to the DC connector (CON1). This hole should be positioned 22mm from the front edge of the case and 9mm down from the lid, so that it aligns correctly with CON1.

That done, a copy of the front panel artwork can be attached to the lid using an even smear of neutral-cure silicone sealant and the holes cut out using a sharp hobby knife.

Once all the panel hardware is in place, the next step is to fit the PC board. The first thing to note here is that the rear lugs of switches S2 and S3 will pass through their PC pads when the board is mounted on the lid, with just enough metal protruding to allow soldering.

This also applies to the binding post terminals. **However, slide switch S1's lugs are not long enough for this, so after the switch is mounted on the lid, a short length of tinned copper wire (eg, a resistor lead offcut) must be soldered to each lug to extend its length.**

By the way, when you're fitting these short extension wires, it's a good idea to make a small hook at the end of each wire and pass it through the lug's hole before squeezing it with needle-nose pliers. The idea here is to ensure that, once soldered, it's not going to fall out when the lower ends of the wires are later soldered to the board pads.

Once the extension wires have been fitted, you should be able to fit the PC board assembly on the lid so that all the switch and binding post leads pass through their matching board holes.

That done, you can fasten it all together using four M3 × 6mm countersink head screws, which pass through the front of the lid and into the spacers.

The assembly can now be completed by soldering the switch and binding post leads and by fitting the battery snap connector.

## Checkout and calibration

Your LC meter is now ready for testing and calibration. To do this, first connect a plugpack supply or a 9V alkaline battery to the unit, set slider switch S1 to the 'Capacitance' position and switch on using S3. As soon as power is applied, the message 'Calibrating' should appear on the LCD for a second or two, then the display should change to read 'C = NN.N pF', where NN.N is less than 10pF.

If this happens, then your meter is probably working correctly, so just leave it for a minute or two to let the test oscillator stabilise. During this time the capacitance reading may vary slightly by a few tenths of a picofarad as everything settles down – that's normal.


Now press 'Zero' button S2 for a second or two and release it. This forces the microcontroller to start up again and recalibrate, so you'll briefly see the 'Calibrating' message again and then 'C = 0.0pF'. This indicates that the microcontroller has balanced out the stray capacitance and reset its zero reference.

## Troubleshooting

If you don't get any messages displayed on the LCD, chances are that you've connected either the battery snap lead or the plugpack lead's connector with reversed polarity. Check the supply connections carefully. With power applied, you should be able to measure +5V on pin 14 of IC1 with respect to ground (0V).

Alternatively, if you get some messages on the LCD, but they're not as described, it's time to check that the meter's test oscillator is working properly. To do this, switch off, fit jumper shunt LK2 (ie, at the back of the board), then apply power and watch the LCD.

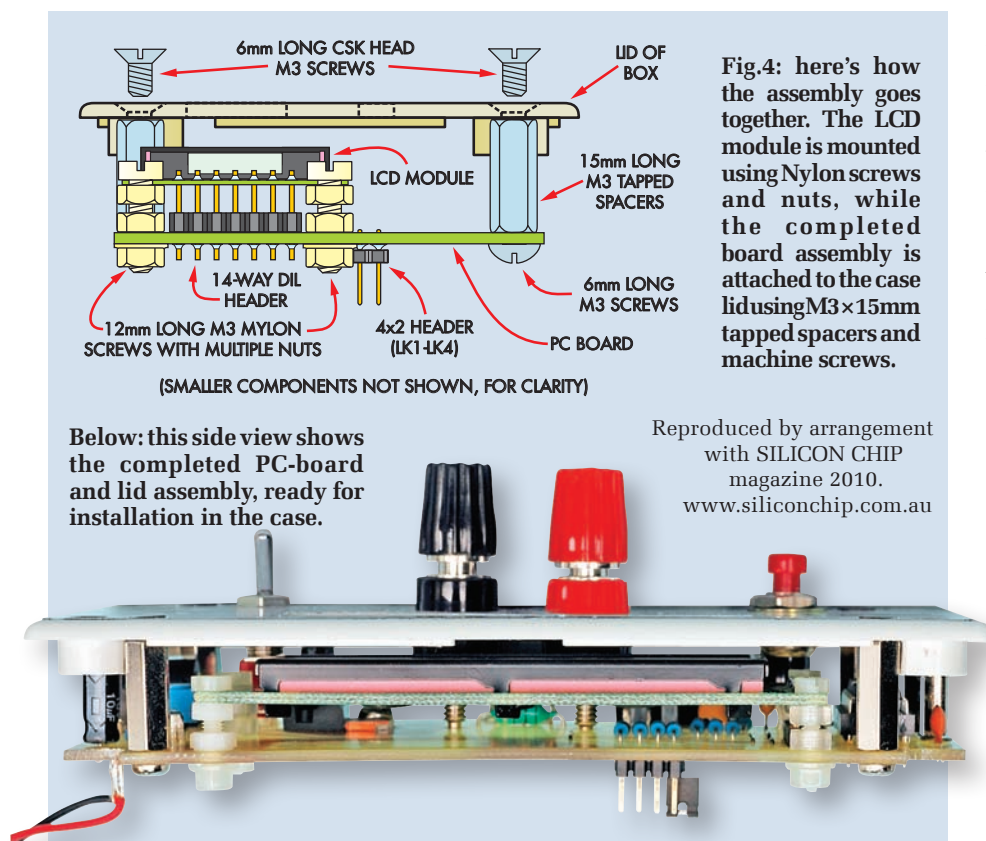After the 'Calibrating' message, the micro should display an eight-digit number which represents the oscillator frequency F1. This should be between about 00042000 and 00058000, if your components for L1 and C1 are within the usual tolerance.



Reproduced by arrangement  
with SILICON CHIP  
magazine 2010.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

If the figure you get for F1 is '00000000', your test oscillator isn't working and you will need to switch off and look for the cause. The possibilities include missed solder joints, a poor solder joint involving one of the oscillator components, or perhaps a tiny sliver of solder bridging adjacent copper tracks or pads.

If you do get a figure in the correct range, write the value down, then switch off and transfer the jumper shunt to the LK1 position. Re-apply power and check that the LCD now shows a different

eight-digit number after calibrating. This will be F2 – ie, the oscillator frequency when capacitor C2 is switched in parallel with C1.

Because the two capacitors are nominally the same value, F2 should be very close to 71% of F1. That's because doubling the capacitance reduces the frequency by a factor equal to the square root of two (ie,  $1/\sqrt{2} = 0.707$ ). If your reading for F2 is well away from 71% of F1, you may need to replace C2 with another capacitor whose value is closer to C1.

On the other hand, if F2 is exactly the same as F1, this suggests that relay RLY1 is not actually switching C2 in at all. This could be due to a poor solder joint on one of RLY1's pins or you may have wired it into the board the wrong way around.

Once you do get sensible readings for F1 and F2, your Digital LC Meter will be ready for calibration and/or use. If you don't have a capacitor of a known value to perform your own accurate calibration, you'll have to rely on the meter's own self-calibration (which relies largely on the accuracy of capacitor C2). In this case, just remove any jumpers from LK1 to LK4 and fit your meter assembly into its box, using self-tapping screws to hold everything together.

The battery sits in the bottom of the case. It is secured by wrapping it in foam, so that it is firmly wedged in place when the lid assembly is fitted to the case.

## Fine-tuning the calibration


If you happen to have a capacitor of known value (because you've been able to measure it with a high-accuracy LCR meter), you can easily use it to fine-tune the Digital LC Meter's calibration.

First, switch the unit on and let it go through its 'Calibrating' and 'C = NN.N pF' sequence. That done, wait a minute or two and press the Zero button (S2), ensuring that the LCD then shows the correctly zeroed message – ie, 'C = 0.0 pF'.

Next, connect your known-value capacitor to the test terminals and note the reading. It should be fairly close to the capacitor's value, but may be somewhat high or low.

If the reading is too low, install link LK4 on the back of the board and watch the LCD display. Every 200ms or so, the reading will increment as the PIC microcontroller adjusts the meter's scaling factor in response to the jumper. As soon as the reading reaches the correct figure, quickly remove the jumper to end the calibration adjustment.

Conversely, if the meter's reading for the known capacitor is too high, follow the same procedure, but with the jumper in the LK3 position. This will cause the micro to decrement the meter's scaling factor each time it makes a measurement, and as before, the idea is to remove LK3 as soon as the reading reaches the correct figure.

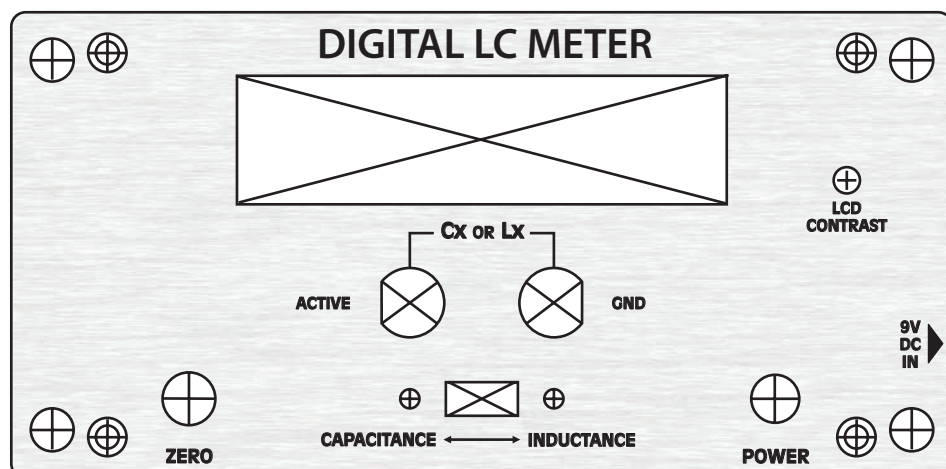

**Fig.5: this full-size front-panel artwork can be used as a drilling template for the front panel.**





**Fig.6:** this is what appears on the LCD screen after zeroing the unit in Capacitance mode.

If you are not fast enough in removing the jumper during either of these calibration procedures, the microcontroller will 'overshoot'. In that case, you simply need to use the opposite procedure to bring the reading back to the correct figure. In fact, you may need to adjust the calibration back and forth a few times until you're satisfied that it is correct.

As previously mentioned, the PIC microcontroller saves its scaling factor in its EEPROM after every measurement during these calibration procedures. That means that you only have to do the calibration once. Note also when you calibrate the meter in this way using a known-value capacitor, it's also automatically calibrated for inductance measurements.

## Using it

The Digital LC Meter is easy to use. Initially, you just switch it on, set S1 to Capacitance (NOT Inductance), wait a minute or two for it to stabilise and then zero it using pushbutton S2. It's then just a matter of connecting the unknown component to the test terminals, selecting 'Capacitance' or 'Inductance' using S1 and reading the component's value off the LCD.


Alternatively, you can zero the Digital LC Meter on the 'Inductance' range by fitting the shorting bar shown in Fig.7 (since this bar has virtually zero inductance). This shorting bar is initially connected between the test terminals, and switch S2 is then pressed to zero the reading. That done,

## Using A Backlit LCD

Either the Jaycar QP-5515 LCD module (no backlight) or the QP-5516 LCD module (with backlight) or similar can be used with this project.

If you intend running the unit from a plugpack or if battery use will only be for short periods, then the backlit version can be used. Alternatively, for general battery use, we recommend the non-backlit version – its current consumption is much lower and so the battery will last a lot longer.

## Adaptor board for very small capacitors

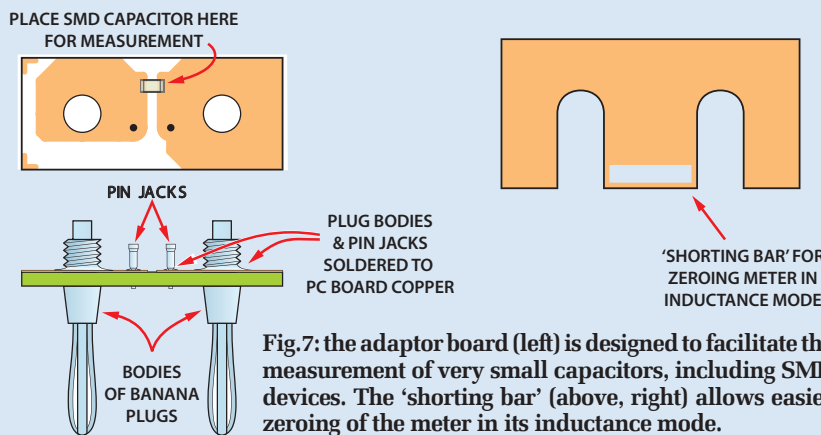

**Fig.7:** the adaptor board (left) is designed to facilitate the measurement of very small capacitors, including SMD devices. The 'shorting bar' (above, right) allows easier zeroing of the meter in its inductance mode.

**T**O help measure very small capacitors—including trimmers and SMD capacitors—we have designed a small adaptor board which can be plugged into the meter's binding post terminals. This adaptor board provides a pair of closely spaced pin jacks, along with copper pads separated by a 1mm gap.

The pin jacks make it easier to measure small leaded capacitors and very small trimmers, while the copper pads alongside are for measuring SMD capacitors.

The adaptor board is easily assembled. It mounts copper-side-up on two banana plugs, which are soldered to the copper around the two large holes.

That done, the two pin jacks (cut from a SIL or DIL socket strip) are soldered into the two smaller holes.

To use this adaptor board, you simply plug it into the top of the Digital LC Meter's binding posts and then press the Zero button (S2) to force the meter to cancel out the additional stray capacitance. You can then measure small leaded capacitors, trimmers or SMD capacitors simply by applying them to the top of the adaptor.

Finally, we have also designed a second small adaptor board which acts as a 'shorting bar'. It connects between the two normal binding posts of the Digital LC Meter, to allow zeroing of the meter in its **inductance** mode.

the shorting bar is removed and the unknown inductor connected across the test terminals.

Note, if you don't have S1 (Capacitance/Inductance) in the correct position, the micro will usually give

an 'Over Range' error message on the LCD. This will also occur if the component's value is outside the meter's measuring range – ie, above about 800nF for capacitors or 70mH for inductors.

**EPE**

## Acknowledgements

The Digital LC Meter described in this article is based on a 1998 design by Neil Hecht of 'Almost All Digital Electronics', in Auburn, Washington, US (see his website at [www.aade.com](http://www.aade.com)).

Mr Hecht's design used a PIC16C622 microcontroller, together with an LM311 comparator in the measuring oscillator. His firmware also made use of floating-point maths routines for PIC processors. These were written by Frank Testa, and made available on the website of PIC manufacturer Microchip Technology ([www.microchip.com](http://www.microchip.com)).

Since then, various people have produced modified versions of the design, including Australian radio amateur Phil Rice, VK3BHR of Bendigo, Victoria. Mr Rice and others have also modified the firmware and adapted it to use the PIC16F628 micro with its internal comparator. They also added the firmware calibration facility. Further information on Mr Rice's version can be found on the website of the Midland Amateur Radio Club ([www.marc.org.au](http://www.marc.org.au)).

In summary, a great deal of the credit for this latest version of the design must go to those earlier designers. The author acknowledges their work.

# Hybrid Heaters And Nanostuff

## TechnoTalk

Mark Nelson

**Few would deny that energy conservation and carbon reduction are key issues of the moment, even if most politicians display far too little commitment to, or understanding of, the issues. Our leaders may be doing too little, but we really can do something, even if our motivation is more on saving money than the planet – ‘every little helps’. Electronics research is playing a vital part too, as Mark Nelson now explains.**

**J**ust before Christmas, the politicians demonstrated their true level of commitment to combating climate change. The only people who took comfort from this weak-willed capitulation were those who deny the existence of climate change. But however disappointed, depressed (or bored stiff) you may be by the argument and counter-argument, your wallet must be interested in the energy conservation measures that will save you money as well as save the planet.

### Hybrid heater has star quality

The word hybrid has always caused me problems. The concept implies neither fish nor fowl, and smacks of the same kind of compromise as a seminar (why not go the whole hog and settle for an entire ‘nar’?). Nevertheless, General Electric (US) has struck a blow against energy wastage with its new-technology water heater, hybrid or not. This all-new design provides the same amount of domestic hot water as traditional heaters do, but saves users up to \$320 (£200) a year on their electricity bills. That’s a 62% reduction on monthly utility bills for years to come. Little wonder that this appliance has achieved Energy Star rating.

So how does it work? The tank portion of this electric water heater includes two electric heating elements, a pressure relief valve, an internal porcelain-lined tank and an anode rod. But what truly sets this product apart sits just above the tank. In a nutshell, this is a heat pump that draws warmth out of the surrounding air and transfers it into the tank.

A compressor and evaporator are integrated into the electric water heater unit and the evaporator draws in ambient heat from surrounding air using two variable speed fans. Condenser coils wrap the tank all the way to the bottom to transfer this heat into the tank and heat the water.

There’s a 3-D animation at [www.geappliances.com/heat-pump-hot-water-heater/electric-water-heater-features.htm](http://www.geappliances.com/heat-pump-hot-water-heater/electric-water-heater-features.htm), where you can also read about the easy-to-use control panel and back-lit LCD display that enable users to select the five different operational modes that optimise the way the heater works.

Right now, demand for these heaters is outrunning production, which is not surprising as the price at around £1,000 is no more than an equivalent ‘old-technology’ hybrid heater. With a payback like this I certainly want one of these, but like you, I shall have to watch out for similar products to appear over here in the not too distant future.

### Scavengers update

A few months back we covered energy scavenging from the trample of punters’ feet, the weight of cars driving over treadle plates in supermarket car parks and even microchips harvesting radio frequency energy. But there are other techniques, and there are now sensor modules on the market that harvest tiny but useful amounts of energy from their surroundings using light, temperature change and rotation, as well as vibration, linear motion and pressure. The energy is fully adequate to register detected values and transmit data wirelessly.

At the forefront in free energy acquisition is the company EnOcean ([www.enocean.com/en/energy-harvesting](http://www.enocean.com/en/energy-harvesting)), which offers solutions for powering electronic circuitry by a choice of either solar, thermal or mechanical means. Their white paper, *Energy For Free*, is a fascinating read, and you can download it for free from their website, along with application notes, data sheets and much more.

### Blue skies research

My eyes lit up recently when I saw a headline referring to microwave fridges and nano diving boards. It appeared to make sense, as you can have gas refrigerators as well as gas ovens. So, logically alongside microwave ovens why not microwave fridges as well, especially as these are an international first developed by our very own National Physical Laboratory?

‘Now read on’, as they say in the best serialised stories. And as I read on, I discovered that the application of these fridges is not in households, but in quantum physics labs. Disappointing, but at least they do save a lot of energy. In fact, NPL scientists are paving the way for highly accurate measurement of nano-scale matter, by being the first team in the world to develop a tiny microwave-powered room-temperature fridge.

This microwave refrigerator cools tiny devices, called micro or nano-scale mechanical resonators, to  $-170^{\circ}\text{C}$ . Cooling these devices, which look and behave like tiny diving boards, down to that level is vital to making accurate measurements.

Any material that is warmer than absolute zero ( $-273^{\circ}\text{C}$ ) will have atoms moving around inside it, and this makes it very difficult to measure certain parameters accurately. NPL has developed a technique that selectively cools down just the property of a sample that needs to be measured, saving an enormous amount of energy.

This technique will be of great use in nano-scale and quantum physics, as it allows scientists to detect tiny changes in physical factors such as mass, force and displacement by accurately measuring changes in the resonant frequency of the ‘diving board’. This means it can be used in applications where highly sensitive detection is needed, such as bio-analytical screening for viruses (by catching a virus on the diving board). In the longer term this technique could lead to development of even more sensitive ‘quantum’ diving boards that could be used to examine the really big questions of quantum physics, such as at what scale quantum effects break down?

### Nonsense

Maybe you find this research into microwave fridges just far-fetched nonsense, exactly as you might have thought back in 1946 reading new a book by Miles Henslow called *The Miracle of Wireless*.

*Radio welding’ used during the war; ... which is really a method of creating and localising a rapid, intense heat is in use today in the manufacture of plywood and plastics. Glues can be hardened and set within seconds instead of hours. Sausage and chops can be cooked in half a minute by the pressing of a switch.*

Cooking food by wireless – how utterly ridiculous! Yet I bet there’s a microwave oven in your kitchen, so perhaps future science has a value after all. Check out this too: another ludicrous prediction by Henslow, in the same book.

*Maybe it will sound a far-fetched idea today, but the time is surely approaching when everyone will be able to carry about with him a small radio telephone. Wartime development of apparatus to work on very short wavelengths has opened up many entrancing possibilities.*

*Hundred of thousands of ‘radio-telephone channels’ can be used over short distances without interference; and the installation of a network of automatic telephone exchanges might well be utilized for handling the calls from a multitude of pedestrian or automobile telephone subscribers, to sort them out and pass them by line – or by radio link – to main exchanges. Certainly it is but a matter of time before the railway traveller is able to pick up the phone and dial his office or his home.*

That matter of time was 40 years, but you should never underestimate the potential of blue skies research and invention!



# 2-Way Stereo Headphone Adaptor



By Mauro Grassi

**Do you have a stereo amplifier without a headphone socket, but want to listen to your music via headphones? If so, this versatile Stereo Headphone Adaptor will do the job. It connects between your amplifier and loudspeakers, has several operating modes and features two output sockets with individual volume controls.**

**I**F YOU built our 20W Class-A Stereo Amplifier Module described in the Oct '08 issue, you will be aware that it lacks a headphone socket. Similarly, many hifi valve amplifiers also lack a headphone socket, the assumption being that a true hifi enthusiast will want to listen via good-quality loudspeakers.

A headphone output was not included in the Class-A Stereo Amplifier because it would degrade its superb audio performance. Both the wiring paths and the general circuit layout are critical factors in the design, and any changes, however slight, can cause big changes in the signal-to-noise ratio and harmonic distortion figures of the amplifier.

## Headphone listening

If you do want to listen via headphones, a far better option is to build the simple Stereo Headphone Adaptor presented here. It connects directly to the amplifier's speaker terminals and switches the loudspeakers and stereo headphone sockets using two DPDT (double-pole, double-throw) relays, so there's no chance of it degrading the audio performance.

As mentioned in the introduction, you can connect up to two sets of stereo headphones. These can be switched on or off at the touch of a button, and the volume of each can be individually controlled. In addition, the loudspeakers can be switched on or off and there's also a mute switch, which turns everything off.

This means that you can operate the system in one of four modes:

- Loudspeakers only
- Headphones only
- Headphones and loudspeakers operating together
- Mute (all off). It's also possible to mute the system by individually turning the headphones and the speakers off.

Perhaps we should clarify the operation of the mute switch, as it doesn't function quite like a traditional mute switch. Pressing it once certainly mutes the headphones and/or loudspeakers, but pressing it a second time doesn't 'unmute' the system. Instead, you have to press either the 'phones' button or the 'headphone' button (or both) to restore the sound.


## DPDT relays

Because it uses two DPDT relays to do the switching, the Stereo Headphone Adaptor can be used with amplifiers with quite high power outputs. In fact, it's good for use with amplifiers with outputs up to about 100W RMS or more, *provided you're sensible with the Volume control setting on the amplifier.*

We've also designed the unit to not only work with solid-state amplifiers, but also with valve amplifiers as well. The latter must be taken into account separately because unlike solid-state amplifiers, operating a valve amplifier without a load (ie, a loudspeaker) can cause problems.

The reason why most valve amplifiers should not be operated without a load is that they can sometimes

**Fig.1: the Stereo Headphone Adaptor connects between your stereo amplifier and the loudspeakers. It can drive two pairs of headphones.**

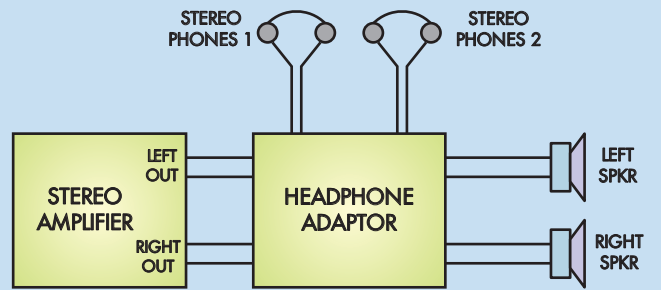

oscillate supersonically. Worse still, they can then produce very high AC voltages in the primary windings of the output transformers. These voltages can be so high that they can cause flashover across the valves sockets or even within the valves themselves. This will not only damage the valves, but other components as well.

As shown in the photos, the unit is housed in a low-profile instrument case with the volume controls, headphone sockets and pushbutton switches neatly laid out on the front panel. The miniature pushbutton switches incorporate integral LEDs, which indicate the settings – red for 'power on', green for 'phones on' and blue for 'speakers on'.


On the rear panel (see below) is a DC power socket and nine gold-plated binding-post terminals. Eight of these terminals are used to connect the amplifier input and loudspeaker output leads, while the ninth terminal connects to the amplifier's chassis and is the earth return for the headphone sockets.

## Default setting

The default mode setting was an important consideration in designing this circuit. We opted to have both the loudspeakers and the headphones on when the circuit is unpowered, and this is done using the normally-closed (NC) contacts of the relays. The advantage of this scheme is that the loudspeakers (and the headphone outlets for that matter) will operate normally when the unit is switched off (ie, zero power consumption).


This is also the default setting when power is first applied to the unit. After that, it's just a matter of using the pushbutton switches to toggle the loudspeakers and the headphones off and on.

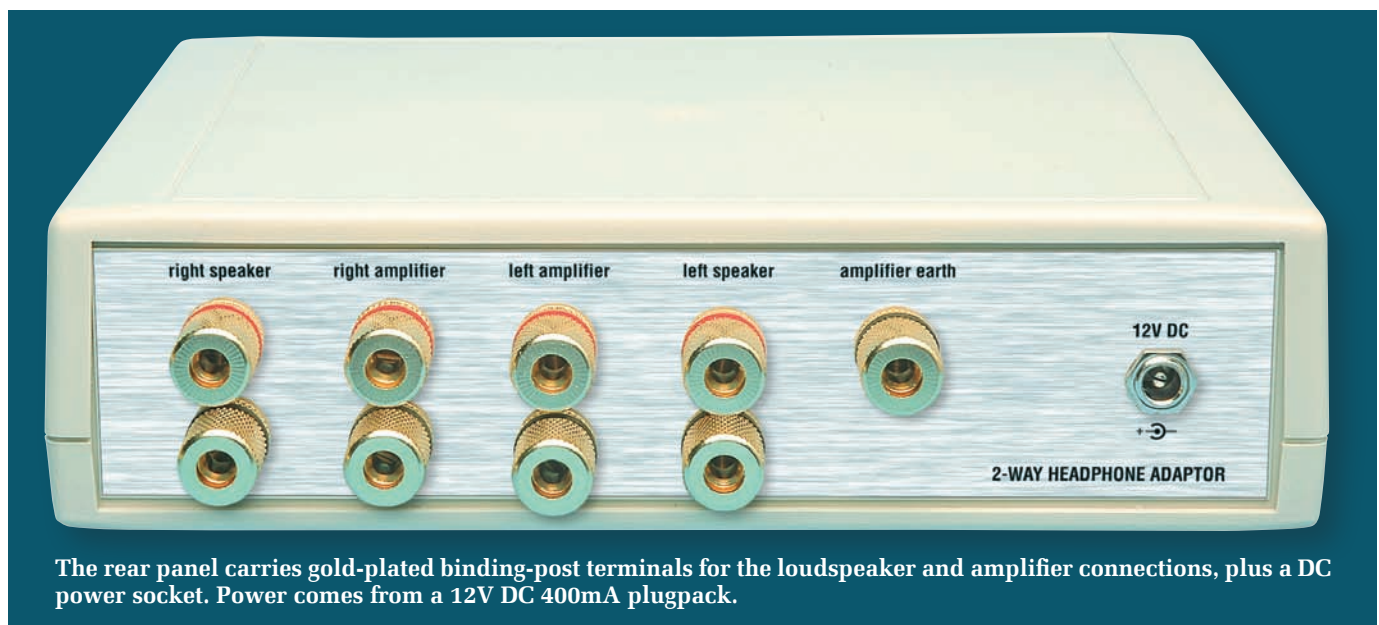The leftmost switch is the mute switch and, as mentioned, this turns both the loudspeakers and the headphones off (but not on again). This switch carries a red LED, which is permanently lit while power is applied – ie, this LED simply serves as a power on indicator.



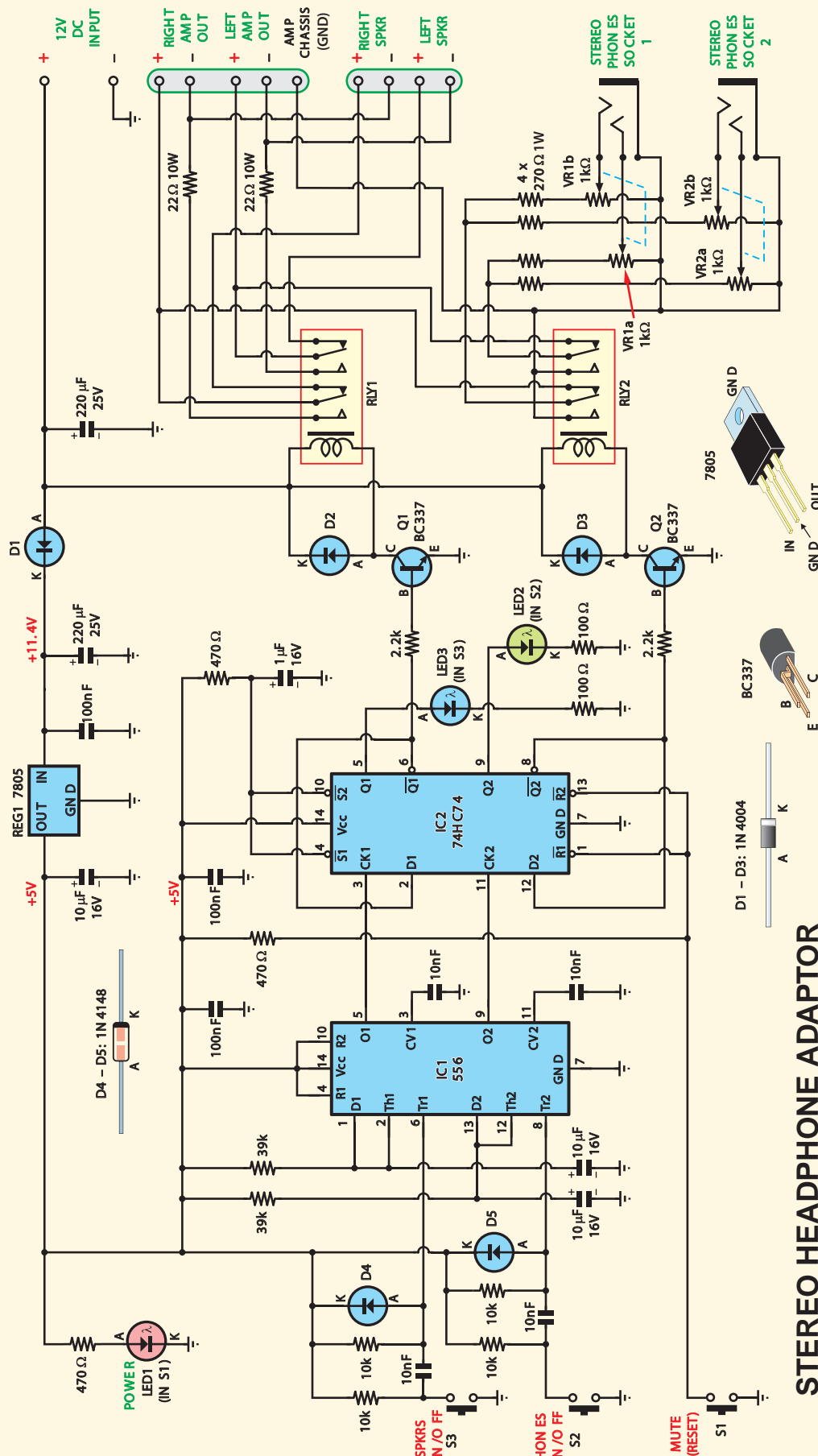The rear panel carries gold-plated binding-post terminals for the loudspeaker and amplifier connections, plus a DC power socket. Power comes from a 12V DC 400mA plugpack.





## STEREO HEADPHONE ADAPTOR

Fig.2: the circuit uses two DPDT (double-throw, double-break) relays to toggle the loudspeakers and/or stereo headphone outputs when switches S2 and S3 are pressed. IC1, a 556 dual timer, debounces these two switches and its outputs at pins 5 and 9 each clock one section of dual D-type flip-flop IC2 whenever a switch is pressed. IC2's Q outputs (pin 6 and 8) in turn drive transistors Q1 and Q2, which then control the relays.

The next switch controls the two headphone sockets, and its green LED lights when the headphones are on. Finally, the third switch controls the speakers and its blue LED lights when the speakers are on. These latter two switches toggle their respective outputs on or off each time they are pressed.

Note that when the loudspeaker switch is toggled to the off position, it places dummy 22Ω loads across the amplifier's left and right channel outputs – ie, these loads appear in place of the speakers. This is done to accommodate valve amplifiers, as these should be loaded at all times as explained earlier.

## Circuit details

Refer now to Fig.2 for the full circuit details. It's based on two ICs (IC1 and IC2), a couple of transistors (Q1 and Q2) and the aforementioned DPDT relays (RLY1 and RLY2).

IC2, a 74HC74 dual D-type flip-flop, forms the heart of the circuit. This is wired in toggle mode, with its D1 and D2 inputs directly connected to their corresponding  $\overline{Q1}$  and  $\overline{Q2}$  outputs. The two set inputs ( $\overline{S1}$  and  $\overline{S2}$ ) are connected to a power-on reset circuit consisting of a 470Ω resistor and a 1μF capacitor, while the two resets ( $\overline{R1}$  and  $\overline{R2}$ ) are connected to ground via the mute (reset) switch S1.

In operation, the D-type flip-flop toggles its outputs on the rising edges of the clock signal pulses. When that happens, the state of the D input (either a logic high or low) is transferred to the Q output and  $\overline{Q}$  toggles to the opposite state.

For example, let's assume that IC2's Q1 output (pin 5) is low. This means that  $\overline{Q1}$  (pin 6) and D1 (pin 2) will both be high. When the next clock pulse arrives, the high on D1 is transferred to Q1 and  $\overline{Q1}$  and D1 toggle low.

Similarly, on the next clock pulse, the low on D1 is transferred to the Q1 output, and  $\overline{Q1}$  and D1 then toggle high again.

When power is first applied, the two set inputs (pins 4 and 10) are pulled low via the 1μF capacitor. This sets IC2's Q outputs high and so  $\overline{Q1}$  and  $\overline{Q2}$  are both low, and transistors Q1 and Q2 are off.

As a result, the relays also remain off and the loudspeakers and headphone outputs are switched on via the NC (normally closed) contacts. In addition,

## Parts List – 2-Way Stereo Headphone Adaptor

1 PC board, code 748, available from the *EPE PCB Service*, size 172 × 104mm

1 ABS instrument case, size 190 × 140 × 50mm

1 12V 400mA DC plugpack

2 control knobs

2 12V DPDT relays with 10A 230V AC contacts (Jaycar SY-4065) (RLY1, RLY2)

2 6.35mm PC-mount stereo jack sockets

3 3-way heavy-duty PC-mount screw terminal blocks

1 PC-mount 2.5mm DC socket, or

1 panel-mount 2.5mm DC socket

4 self-adhesive rubber feet

2 M3 × 12mm machine screws

1 M3 × 6mm machine screw

3 M3 nuts

2 M3 × 6mm tapped spacers

4 panel-mount gold-plated binding posts, red

5 panel-mount gold-plated binding posts, black

1 1m-length of heavy-duty speaker cable

1 300mm-length tinned copper wire for links

2 BC337 NPN transistors (Q1, Q2)

1 7805 +5V regulator (REG1)

3 1N4004 rect. diodes (D1 to D3)

2 1N4148 signal diodes (D4, D5)

### Switches

1 SPST horizontal PC-mount tactile switch, with green LED (Jaycar SP-0616)

1 SPST horizontal PC-mount tactile switch, with red LED (Jaycar SP-0615)

1 SPST horizontal PC-mount tactile switch, with blue LED (Jaycar SP-0617)

### Capacitors

2 220μF 25V radial electrolytic

3 10μF 16V radial electrolytic

1 1μF 16V radial electrolytic

3 100nF monolithic

4 10nF ceramic

### Resistors (0.25W 1% metal film)

2 39kΩ      3 470Ω

4 10kΩ      4 270Ω 1W

2 2.2kΩ      2 100Ω

2 22Ω (10W wirewound)

2 1kΩ dual 16mm log pots (VR1, VR2)

Reproduced by arrangement with SILICON CHIP magazine 2010.  
www.siliconchip.com.au

### Semiconductors

1 NE556 dual timer IC (IC1)

1 74HC74 dual D-type flip-flop (IC2)

LED2 and LED3 both light (since the two Q outputs are high) to indicate that the speakers and the headphones are on.

## Dual timer

IC1 is a 556 dual timer and is basically two independent 555 timers in one package. Both sections are configured as one-shot monostables with pulse widths of just under 0.5s. They are used to debounce switches S2 (phones on/off) and S3 (speakers on/off), to provide clean clock pulses for the D inputs of IC2.

This debouncing circuitry is necessary because the metal contacts in the switches tend to 'bounce' as they close. As a result, we get a series of short pulses from the switches instead of just one pulse. If these pulses were fed directly to the clock (CK) inputs of IC2, there's no guarantee that the flip-flops would toggle, as the switches are just as likely to produce an even number of pulses as an odd number.


The monostables in IC1 eliminate this problem. As shown, switches S2 and S3 are connected to the trigger inputs (Tr1 and Tr2) of the monostables via 10nF capacitors. When a switch is pressed, its corresponding trigger input is briefly pulled low (via one of the 10nF capacitors) and this triggers the monostable.

As a result, the monostable's output (pin 5 or pin 9) goes high and applies a positive-going clock pulse to the relevant clock input of IC2. This causes the corresponding D-type flip-flop to toggle.

For example, let's assume that the circuit is powered up and is in the default state. If switch S3 is now pressed, pin 5 of IC1 goes high for about 0.5s and applies a clock pulse to pin 3 (CK1) of IC2. As a result, the relevant flip-flop toggles and sends its  $\overline{Q1}$  output high.

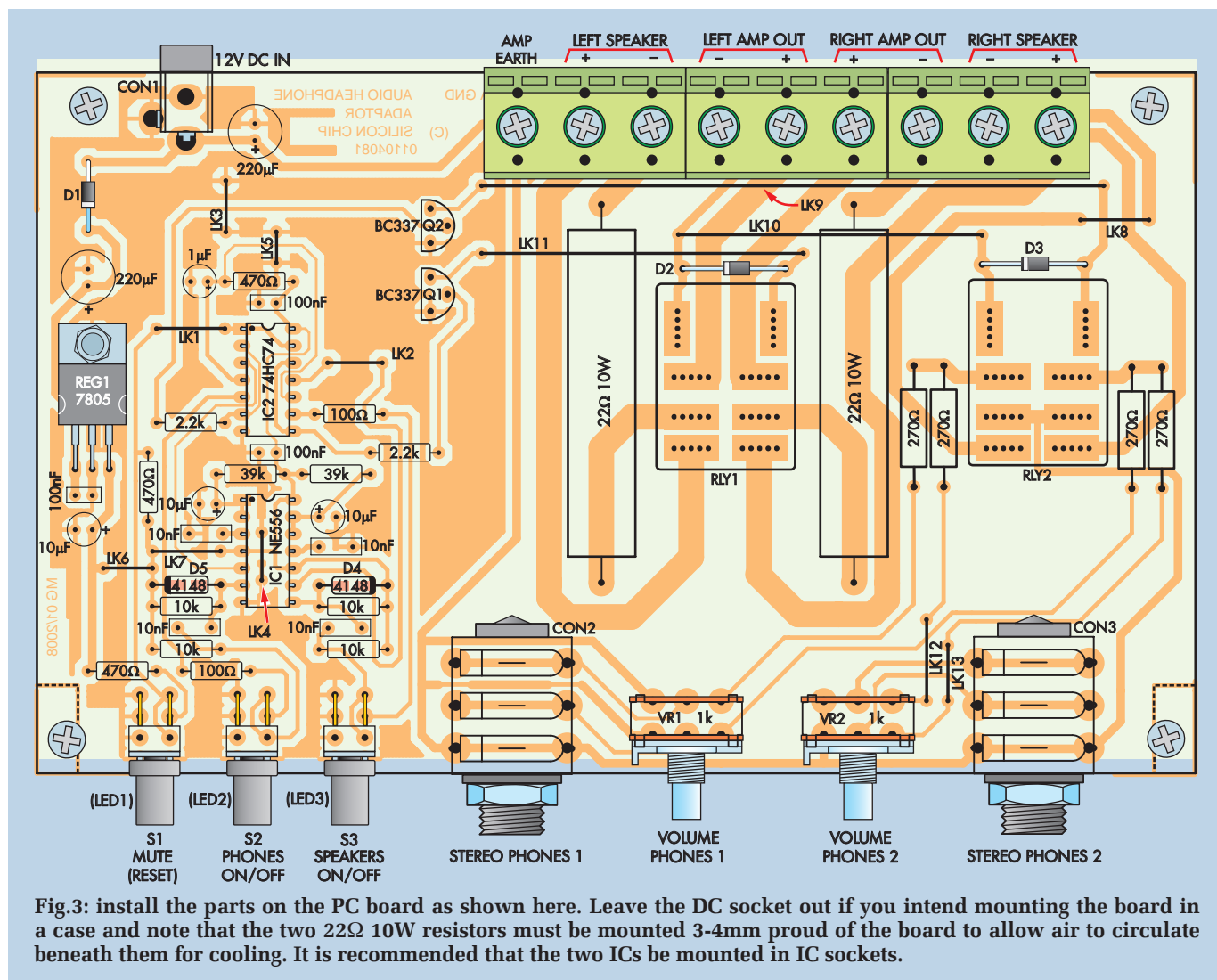This turns on transistor Q1 and relay RLY1, and so the NC (normally






closed) contacts open and disconnect the loudspeakers. At the same time, the relay's NO (normally open) contacts switch two 22Ω 10W resistors across the amplifier outputs to provide the dummy loads. In addition, LED 3 turns off since IC2's Q1 output is now low. Pressing switch S3 again retriggers the monostable and toggles the flip-flop to its opposite state, so that Q1 is low again. This turns off transistor Q1 and RLY1 and reconnects the loudspeakers via the relay's NC contacts. In addition, LED3 turns on (to indicate that the speakers are on) since IC2's Q1 output is now high. Switch S2 and its following circuitry work in exactly the same fashion to control transistor Q2 and relay RLY2. This relay, in turn, switches the signals from the left and right channel amplifier outputs to the two headphone sockets (via the volume controls).

Both the ring (right channel) and tip (left channel) terminals of the headphone sockets are driven via 270Ω 1W resistors and dual 1kΩ log potentiometers VR1 and VR2, the latter functioning as Volume controls. Even with the volume wound right up, the 270Ω resistors should provide sufficient attenuation to protect the headphones from damage. **Note, however, that you should increase these resistors to 680Ω or more if you have high-impedance (say 600Ω) headphones.** The sleeve (ie, earth) terminal of each headphone socket is connected to the amplifier chassis to provide the ground return. Diodes D4 and D5 are there to ensure that IC1's trigger inputs (pins 6 and 8) cannot go more than 0.6V above the +5V supply rail. What happens is that when a switch is pressed, the relevant 10nF capacitor quickly charges to +5V via

a 10kΩ resistor (ie, one side of the capacitor is pulled to ground and the other side goes to +5V). When the switch is subsequently released, the side that was at ground is immediately pulled to the +5V rail by another 10kΩ resistor, and so the other side of the capacitor would go to +10V if not for the diode – ie, we would get a brief 10V spike. Diodes D4 and D5 clip these voltage spikes to +5.6V and thus prevent damage to IC1. **Muting** Switch S1 is the mute (or Reset) switch and is connected directly to the reset inputs (pins 1 and 13) of both flip-flops in IC2. When this switch is pressed, the reset inputs are pulled to ground and the flip-flops are both set with their Q outputs low and their Q outputs high. As a result, transistors Q1 and Q2 and the relays are on, and so the

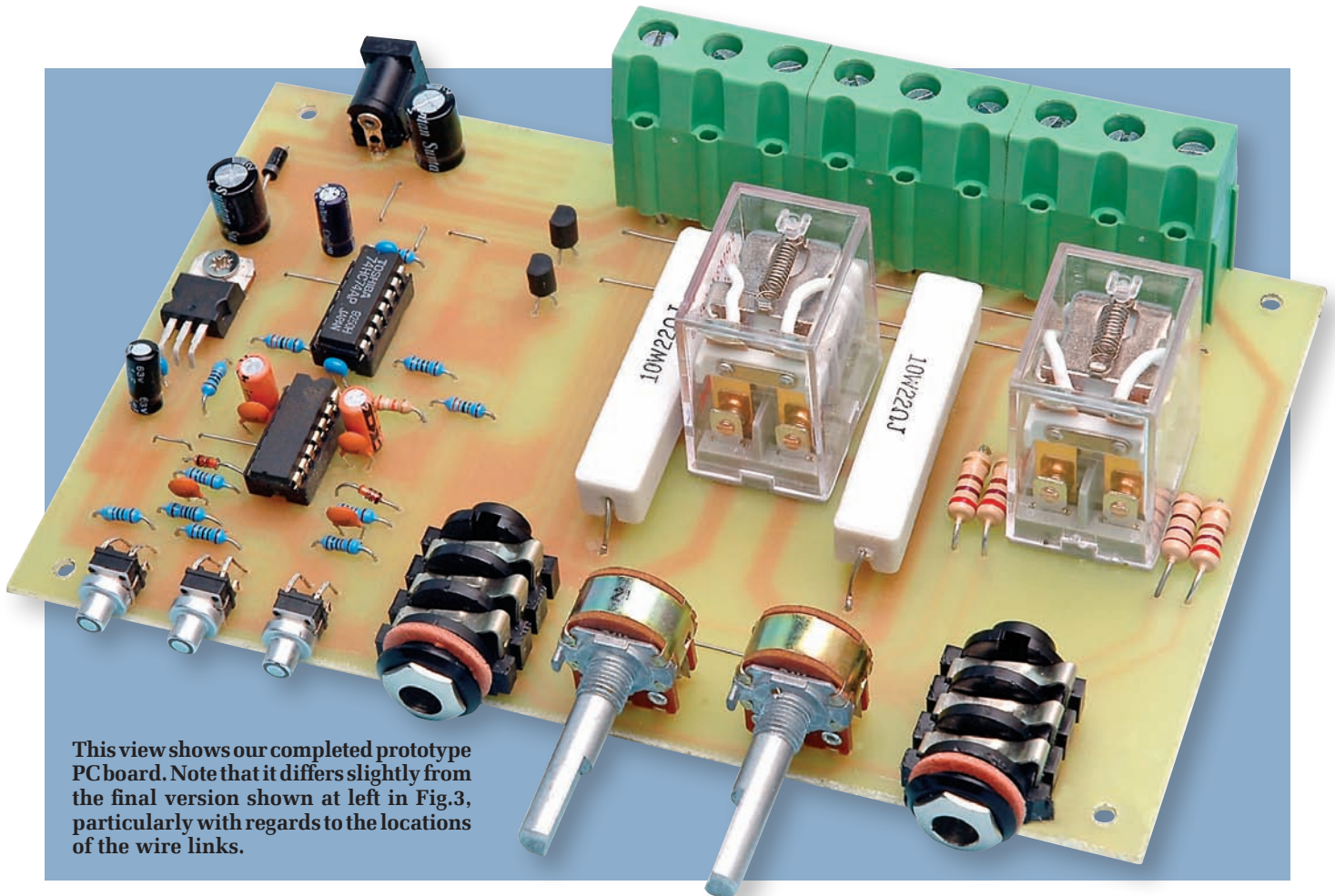

headphones and loudspeakers are off. They can then only be turned back on again by pressing switches S2 and S3.

Diodes D2 and D3 are used to quench the high back-EMF spikes that are generated when the relays switch off. This is necessary to protect the relay driver transistors from damage.

## Power supply

Power is derived from a 12V DC plugpack. This supply is filtered using a 220 $\mu$ F electrolytic capacitor, and is used to directly power the relay driver transistors and the relays.

The rest of the circuit is powered from a +5V rail, which is derived from

a 3-terminal voltage regulator, REG1. Diode D1 provides reverse polarity protection and its output is filtered using a second 220 $\mu$ F electrolytic capacitor before being applied to the input of the regulator. A 10 $\mu$ F capacitor decouples the regulator's output, with additional 100nF capacitors placed close to the supply pins of IC1 and IC2.

Finally, the power LED (inside S1) is powered via a 470 $\Omega$  current-limiting resistor. This LED is on whenever power is applied.

## Construction

Construction is fairly straightforward with all the parts mounted on a single PC board, code 748. This

board is available from the *EPE PCB Service*.

Our prototype was housed in a plastic case measuring 190 × 140 × 50mm. If you intend using this case, it will be necessary to cut out the front corner pieces from the PC board in order to clear the front case pillars.

Fig.3 shows the parts layout on the PC board. Before mounting any parts, check the board carefully for etching defects, then check the hole sizes for the headphone sockets, screw terminal blocks and relays by test fitting these parts into position. Enlarge any holes if necessary.


Begin the assembly by installing the 13 wire links in the positions

## Resistor Colour Codes

|   | No. | Value         | 4-Band Code (1%)          | 5-Band Code (1%)                |
|---|-----|---------------|---------------------------|---------------------------------|
| □ | 2   | 39k $\Omega$  | orange white orange brown | orange white black red brown    |
| □ | 4   | 10k $\Omega$  | brown black orange brown  | brown black black red brown     |
| □ | 2   | 2.2k $\Omega$ | red red red brown         | red red black brown brown       |
| □ | 3   | 470 $\Omega$  | yellow violet brown brown | yellow violet black black brown |
| □ | 4   | 270 $\Omega$  | red violet brown brown    | red violet black black brown    |
| □ | 2   | 100 $\Omega$  | brown black brown brown   | brown black black black brown   |
| □ | 2   | 22 $\Omega$   | NA                        | NA                              |



## Constructional Project

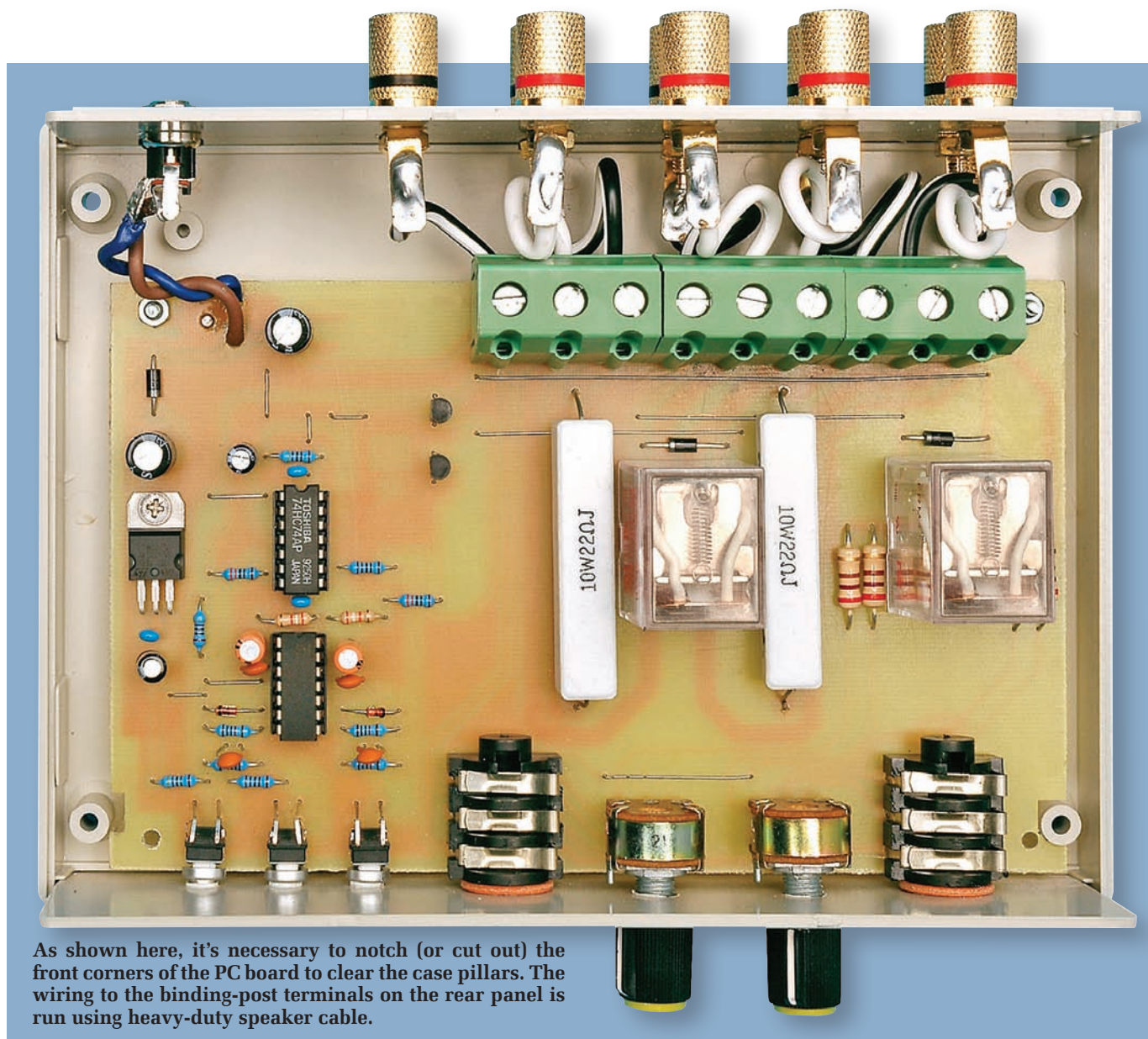

As shown here, it's necessary to notch (or cut out) the front corners of the PC board to clear the case pillars. The wiring to the binding-post terminals on the rear panel is run using heavy-duty speaker cable.

indicated. These links should all be run using tinned copper wire and must be straight.

To straighten the link wire, simply clamp one end in a vice and then stretch the wire slightly by pulling on the other end with a pair of pliers. Each link can then be cut to length and its end bent down at right angles before installing it on the PC board.

Note particularly that LK4 goes under IC1, while LK9 runs directly behind the screw terminal blocks.

That done, install the resistors and diodes D1 to D5, but leave the 22 $\Omega$  10W resistors out for the time being. Table 1 shows the resistor colour codes, but you should also check each one using a digital multimeter.

Take care with the orientation of the diodes and note that D1 to D3 are type 1N4004 while D4 and D5 are type

1N4148. Note also that D4 and D5 face in opposite directions.

The 7805 3-terminal voltage regulator is next on the list. As shown, it's installed with its metal tab flat against the PC board and its leads bent down through 90° to go through their respective holes.

To do this, first position the device on the board, then use a pair of needle-nose pliers to grip the leads at the appropriate point and bend the leads down by 90°. The device's metal tab can then be fastened to the board using an M3  $\times$  6mm screw, nut and lockwasher and the leads soldered.


Do not solder the leads before bolting down the metal tab. If you do this, you could crack the soldered joints as the tab is bolted down.

The capacitors are next on the list. Start with the monolithic and ceramic types, then install the six electrolytics.

Make sure that the latter are all installed with the correct polarity.

Next, install the two 22 $\Omega$  10W resistors. These should both be mounted 3 to 4mm proud of the PC board to allow air to circulate beneath them for cooling. A couple of thick pieces of cardboard can be used to achieve an even spacing.

Now for the ICs and transistors. Push the transistors down onto the board as far as they will comfortably go before soldering their leads and be sure to use the correct IC at each location. Make sure also that each IC is correctly oriented and be careful not to create unwanted solder bridges when soldering their pins. We strongly recommend you use IC sockets here if you do not wish to solder IC pins directly to the circuit board; prolonged heat on the pins can damage ICs.

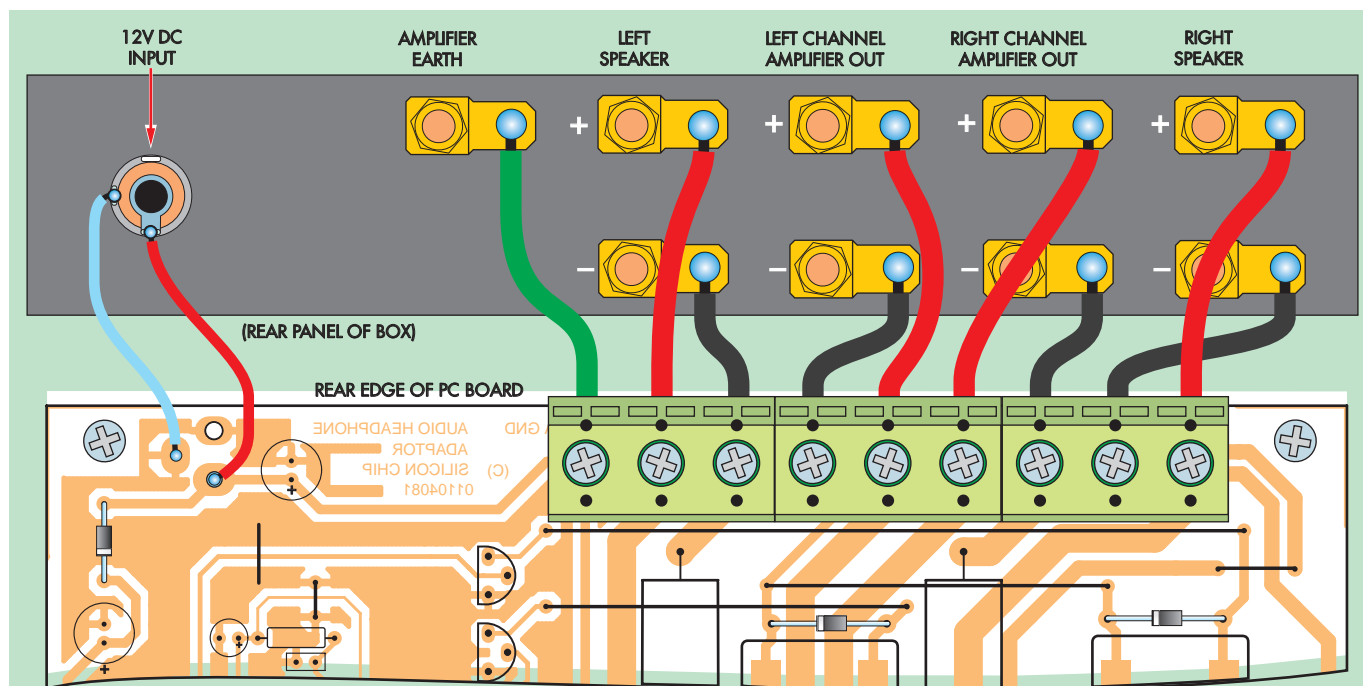

**Fig.4:** follow this diagram to complete the wiring between the PC board and the rear panel hardware. Note that the leads to the loudspeaker and amplifier terminals should be run using heavy-duty speaker cable.

Finally, the board assembly can be completed by mounting the larger hardware items. These include the two dual (stereo) log. potentiometers, the headphone sockets, the relays and the three 3-way screw terminals blocks. **Cut the pot shafts to about 15mm long before fitting them and make sure that each part is seated correctly against the PC board before soldering its leads/tags.**

The DC power socket should also be installed unless you are mounting the board in a case and intend using a panel-mount DC socket instead.

## Testing

Before applying power, go over the board and carefully check your work. In particular, check that the correct part has been used at each location, that all polarised parts are correctly oriented and that there are no missed solder joints or solder 'bridges'.

Once you are satisfied that all is correct, connect a 12V DC plugpack, switch on and check that all three LEDs in switches S1 to S3 light. Check also that the relays remain off at switch-on.

Now press the phones switch (S2) and check that relay RLY2 toggles. At the same time, the green LED in S2 should go out. Pressing this switch again should toggle RLY2 off again and turn the green LED back on.

Finally, check that RLY1 and the blue LED alternately toggle on and off each time the speakers switch (S3) is pressed.

If the module passes all these tests, then it is working correctly. If not, then you're in for a spot of troubleshooting. Here's what to look for if it doesn't work:

**1) Symptom:** no LEDs light when power is applied.

**Do this:** check the supply polarity. If that's correct, check the orientation of diode D1 and check for +5V at the output of regulator REG1.

**2) Symptom:** all LEDs initially light, but one relay refuses to toggle when its switch is pressed.

**Do this:** check that the corresponding Q output from IC2 toggles correctly (ie, between 0V and about +4.8V) each time the switch is pressed. If it does, then check the relevant transistor – its collector (C) should toggle high or low each time the switch is pressed.

If the transistor is switching correctly but the relay doesn't operate, check that the diode across the relay coil is correctly oriented.

**3) Symptom:** a Q output from IC2 does not toggle when the relevant switch is pressed.

**Do this:** check IC2 and IC3 for correct placement and orientation and check that their pins are all soldered

correctly. Check also that diodes D4 and D5 are the right way around (note: these two diodes face in opposite directions).

If you have a scope, check the relevant output (pin 5 or 9) from IC1 – you should see a 0.5s positive-going pulse each time the switch is pressed. Check that this pulse is being applied to the corresponding clock input of IC2.

If there are no pulses from IC1, check the parts associated with the switches at the trigger inputs to this IC. The IC itself may also be faulty (unlikely).

## Final assembly

Now for the final assembly. If you are building the unit from a kit, the case will probably be supplied pre-drilled with screen-printed front and rear panels. If not, then you will have to drill the panels yourself using the front and rear panel artworks (Fig.5 and Fig.6) as templates.

The best approach is to first centre-punch the hole locations, then drill each one using a small pilot drill before enlarging it to the correct size. The larger holes (ie, for the headphone sockets, the pots and the DC socket) should be initially drilled to about 5mm, then carefully enlarged to size using a tapered reamer.

That done, colour copies of the panel artworks can be attached to the



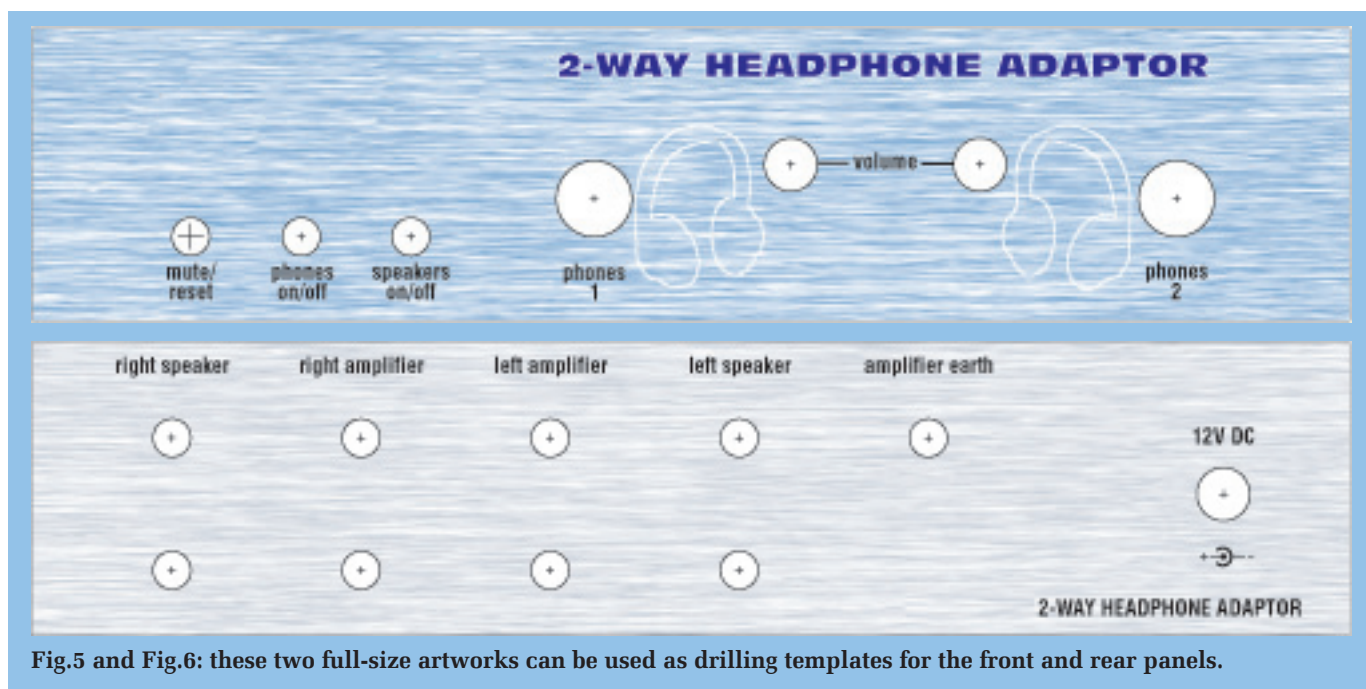


Fig.5 and Fig.6: these two full-size artworks can be used as drilling templates for the front and rear panels.

drilled panels using an even smear of silicone sealant and the holes cut out using a very sharp hobby knife.

Next, fit the front panel to the module and secure it by doing up the nuts for the two headphone sockets. Similarly, fit the panel-mount DC socket and the nine gold-plated binding-post terminals to the rear panel.

Now drop the PC board and front panel assembly into the case and mark out the locations in the base for the rear corner mounting holes. Remove the board and drill these two holes to

3mm, then mount two tapped 6mm spacers in these positions, securing them using M3 × 12mm machine screws which pass up through the bottom of the case.

That done, solder a couple of 50mm long medium-duty hook-up leads to the power supply pads on the PC board. The board assembly can then be secured in place and the wiring to the rear panel completed as shown in Fig.4.

Be sure to use extra heavy-duty speaker cable (eg, 32/0.20) for all connections between the speaker binding-

posts and the screw terminal blocks. The lead to the amplifier earth terminal can be run using medium-duty hook-up wire. You can then complete the assembly by fitting the knobs to the pot shafts and attaching the case lid.

## Trying it out

As already mentioned, this unit connects in series between the amplifier outputs and the loudspeakers, so disconnect the loudspeaker leads from the amplifier and connect them to the Stereo Headphone Adaptor instead.

The outputs from the amplifier then connect to the left and right channel input terminals on the adaptor.

Finally, connect a lead from the terminal marked 'amp earth' to the amplifier's chassis.

If your amplifier doesn't have a ground terminal, then it may be possible to attach a solder lug under one of the case screws. Alternatively, the earth lead can go to the 'negative' terminal of ONE of the amplifier output channels (but not to both, otherwise you'll get an earth loop and lots of hum). This can be done by connecting an insulated wire

link between the 'amp earth' terminal and the 'left amp -' terminal on the back of the Stereo Headphone Adaptor.

After that, it's just a matter of switching everything on, plugging in your headphones and trying it out. **EPE**



The completed 2-Way Stereo Headphone Adaptor, it can be used with both valve and solid-state amplifiers.

By JOHN CLARKE



# Shift Indicator and Rev Limiter For Cars

**If you drive your car for optimum performance, you will want this Shift Light Indicator to indicate just when to change gears. As a bonus, it incorporates a Rev Limiter which throttles back the fuel injectors.**

**I**F YOU'RE interested in driving your car for best acceleration or fuel economy, you will know that an engine's torque peaks at a lower RPM than the peak power. You will also know that when driving for maximum fuel economy, it is wise to keep engine revs reasonably low and to get into the highest gear as soon as possible.

But whether you are driving for best acceleration or economy, you don't want to be watching the tachometer to judge each gear change. That would distract your attention from the road. Having a Shift Light Indicator is the way to go. You will see LEDs light up without having to divert your eyes from the road.

Our Shift Light Indicator has three LEDs to indicate shift points, plus a fourth LED for the Rev Limiter. How you set the individual LED RPM values is up to you. For example, you could set the three LEDs to give a 'ready', 'set' and 'go' indication for each gear change.

Rev limiting can be hard or soft. Hard limiting simply switches off power to the fuel injectors and the engine immediately 'dies'; power does not come back until the RPM falls below a threshold value. Soft limiting reduces the fuel injector duty

cycle in stages so that the power is not killed abruptly. Either way, the engine is protected from damage due to over-revving.


Note that many cars these days already have inbuilt rev limiting, so you may choose not to implement this feature.

### Connections

The Shift Light Indicator (SLI) can either connect to the tachometer signal from the car's ECU (engine control unit) or to the ignition coil where there is no ECU. We have catered for just about every conceivable engine configuration: 1 to 12-cylinder 4-stroke, 1 to 6-cylinder 2-stroke, and 2 and 3-cylinder asymmetrical 4-stroke.

Other connections required are +12V power, 0V (chassis), ground and to the fuel injectors.

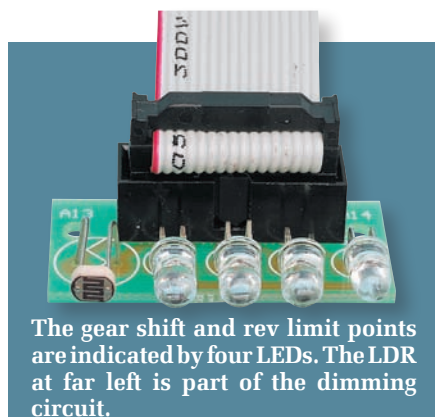The SLI unit can be located in a convenient location under the car's



The gear shift and rev limit points are indicated by four LEDs. The LDR at far left is part of the dimming circuit.



dashboard, while the separate display involving four high brightness LEDs can be mounted on the dashboard. The shift LEDs have automatic dimming so that they will not be too bright when driving at night, but the Rev Limiter does not have dimming – so when it comes on, you will be fully alerted!

## Shift points

Each shift point can be set and operates independently from the others. While the software has them labelled as Shift1, Shift2 and Shift3, they can each be set anywhere between 0 and about 12,500RPM, in 25RPM steps.

Setting shift points is easy and is done with a trimpot that produces a voltage directly proportional to RPM. So, if a shift point is required at 5500RPM, you set the trimpot wiper to 0.55V. You then press a switch to store the value.

The Shift LEDs light to indicate RPM at and above the stored values, as shown in Fig.1. An adjustment is provided to prevent them from flickering on and off when the RPM is hovering around the shift point. This adjustment causes the Shift LEDs to go out at an RPM lower than the shift setting. The difference in the thresholds is called the 'hysteresis'.

## Measuring engine revs

We measure engine revs in RPM (revolutions per minute) by monitoring the tachometer signal from the car's ECU. This delivers one pulse for every cylinder firing (ie, each spark plug firing). We also need to know the engine type (2 or 4-stroke) and the number

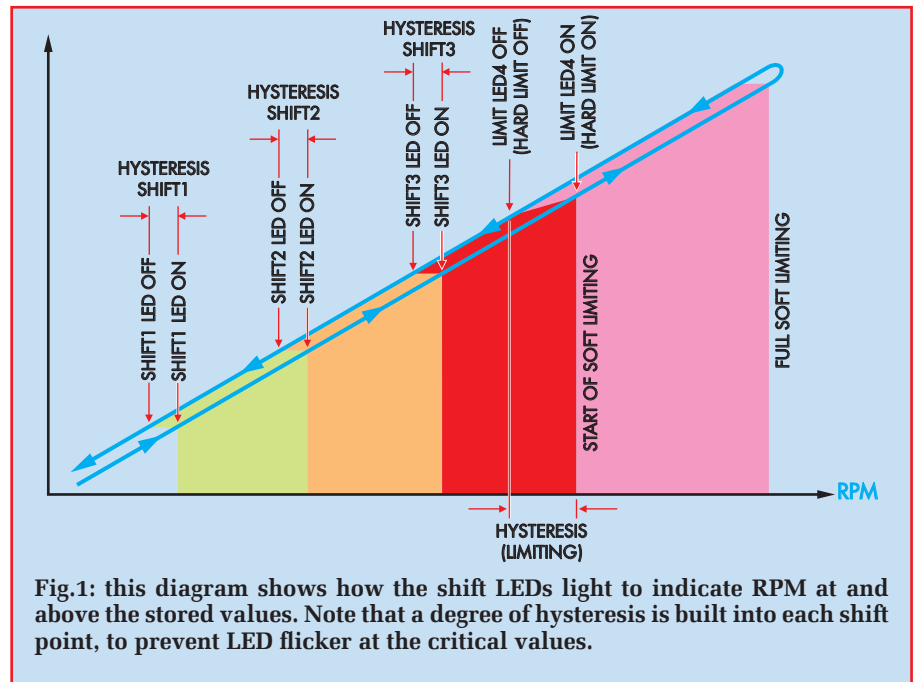


Fig.1: this diagram shows how the shift LEDs light to indicate RPM at and above the stored values. Note that a degree of hysteresis is built into each shift point, to prevent LED flicker at the critical values.

of cylinders in order to calculate engine RPM. For example, a 4-cylinder 4-stroke engine has two cylinder firings per revolution, a 6-cylinder has three firings, a V8 has four firings per rev, and so on.

A particular problem in measuring engine RPM is that we cannot just count pulses over a one minute or even a ten second period. That would mean that the SLI just would not react fast enough. Instead, we could use a 300ms period, which gives a count of 10 for a 4-cylinder 4-stroke engine running at 1000RPM.

But even this period is too long when you consider how fast engine

RPM could change – it could easily go from 1000RPM to 6000RPM or more, in that short time. In addition, a counting period of just 300ms means that the RPM cannot be measured accurately. That previous count of 10 pulses might mean the RPM is 900 or 1100RPM, a 200RPM uncertainty – not very good.

There is a better way, as shown in Fig.2, the block diagram of the circuit.

Here the RPM signal from the engine is filtered to prevent triggering on transient signals and then instead of counting the pulses, we measure the time between them, using a 2MHz signal. What happens is that each firing pulse gates the 2MHz signal to a counter. The

## How rev limiting is achieved

**T**HIS project achieves rev limiting by cutting power to the fuel injectors, and this involves switching the injector positive (+12V) supply rail. This can be done using one of two methods – either by using a relay to switch the supply for hard limiting, or by pulse width modulating power MOSFETs to give soft limiting – ie, a gradual reduction in engine power.

Fig.7(a) shows the standard fuel injector setup. As can be seen, the positive terminals of the fuel injectors are all connected to a common +12V supply rail. The engine management

unit computer (ECU) switches the negative side of each injector.


Hard limiting is achieved by wiring the relay in series between the positive terminals of the fuel injectors and the +12V injector supply rail. This relay, which is controlled by the limiter circuit, switches off the injectors (by opening its contacts) when the rev limit is reached and this immediately cuts engine power. Fig.7(b) shows this scheme.

Alternatively, soft limiting is achieved by wiring two parallel power MOSFETs in series between the fuel injectors

and the +12V injector supply rail. These MOSFETs are then pulse width modulated (PWM) by the limiter circuit when the rev limit is reached, which means that the injector supply rail is also pulse width modulated.

The higher the revs go, the lower the PWM duty cycle. As a result, the engine power is gradually reduced when the rev limit is reached. Fig.7(c) shows this scheme.

Why do we also include the relay in the soft limiting circuit? It's there for added reliability, as explained in another panel.

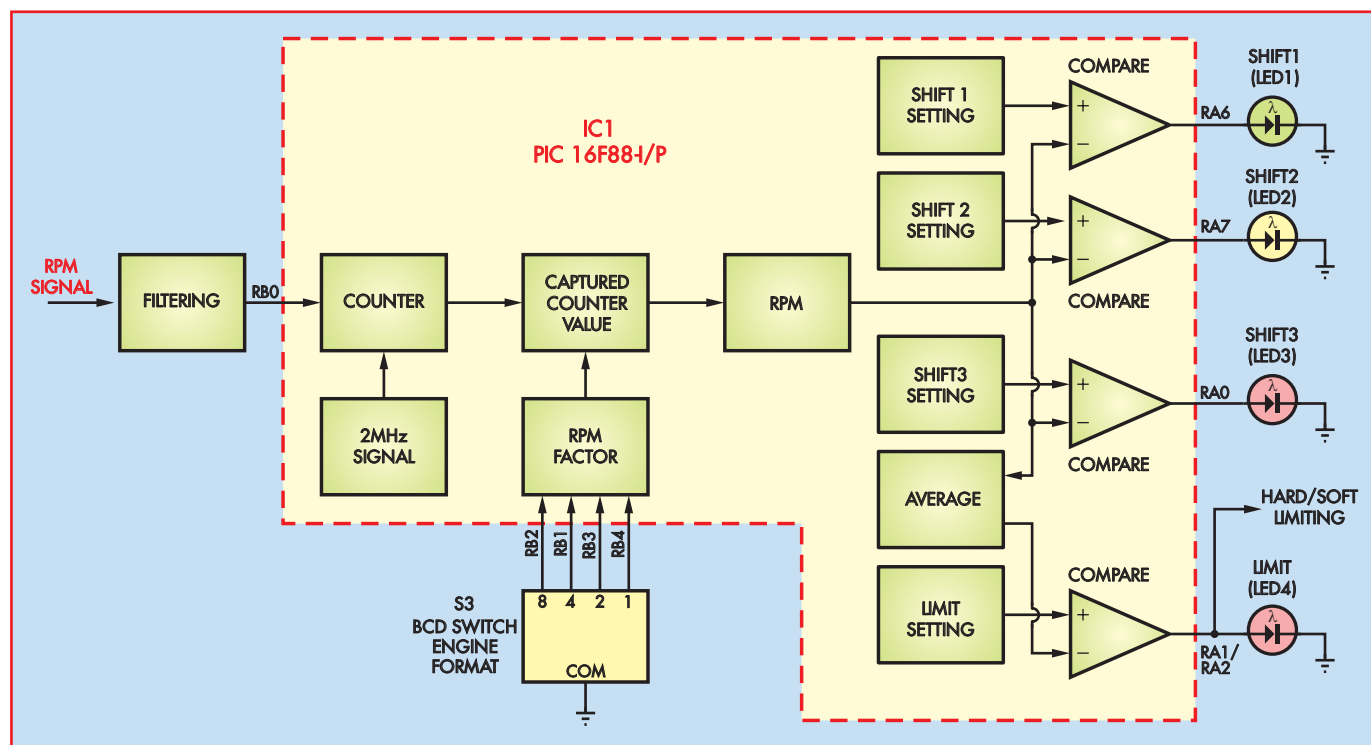

**Fig.2: block diagram of the Shift Indicator and Rev Limiter.** It measures RPM by using the tachometer signal to gate a 2MHz signal into a counter. The counter value is then divided into the RPM factor, as set by BCD switch S3, to give engine RPM.

next pulse places the count in memory and clears the counter, which then proceeds to count again.

For example, if the RPM signal is 33.333Hz, then the counter will reach 60,000 between pulses. This value is divided into the RPM factor, which for a 4-cylinder 4-stroke engine is 60 million. So in this case, the result of the division is 1000RPM.

Each RPM calculation takes 888μs; well before a new count is available. This RPM value is then compared against the settings for shift1, shift2 and shift3.

## Circuit description

The full circuit diagram for the Shift Indicator and Rev Limiter for Cars is shown in Fig.3. It is based on IC1, a PIC16F88-I/P microcontroller which monitors the RPM signal. It then makes the RPM calculations and comparisons with the 'set shift' and 'limit levels', and drives the associated LEDs and limiting circuitry. IC1 operates at 8MHz and is powered from a 5V supply derived from a 3-terminal voltage regulator, REG1.

Two RPM signal input options are provided: either from the ignition coil negative terminal (HI) via a 22kΩ resistor, or the nominal 5V signal from the ECU (LO). The ignition coil signal is

filtered using one or two 47nF capacitors (LK1 adds the second capacitor) and then AC-coupled via a 2.2μF capacitor to the next stage comprising a 100kΩ resistor and 16V Zener diode clamp (ZD2). Diodes D5 and D6 clamp the signal between +5.6V and -0.6V before it is fed to the RB0 input at pin 6 of IC1.

The inputs that connect to the BCD switch (S3) and to the Select (S1) and Set (S2) switches are normally pulled to +5V via internal resistors. When the respective switch is closed, its input is pulled low.

Switches S1 and S2 are continuously monitored by IC1.

## Engine selection

BCD switch S3 selects the engine type. This has four switches (at RB4, RB3, RB1 and RB2) and provides 16 possible combinations, ranging from all switches open to all closed.

The settings for S3 are checked by IC1 when it is first powered up; this sets the required engine type for RPM calculations.

Trimpot VR1 provides the RPM values for the shift and limit settings. The series 30kΩ and 10kΩ resistors connected to the trimpot's wiper reduce the maximum voltage at TP1 to 1.25V.

In practice, VR1 is adjusted to provide the desired RPM voltage at TP1

and 1V is equivalent to 10,000RPM. So, to set the RPM to 5500RPM, VR1 is adjusted so that the voltage at TP1 is 0.55V.

Trimpot VR2 sets the hysteresis range for each shift and limit setting. A 5V setting at TP2 provides 500RPM hysteresis and 1V gives 100RPM hysteresis.

Trimpot VR3 sets the ambient light threshold for dimming the LEDs. The LEDs are bright enough to be easily seen in daytime driving, and therefore need to be dimmed for night-time driving. The ambient light is monitored by a light-dependent resistor (LDR1) and it is connected in series with a 10kΩ resistor and trimpot VR3 to provide a voltage at IC1's AN5 input.

The 10μF capacitor at the AN5 input averages out changes in ambient light. This prevents the display rapidly changing in brightness if passing along a street-lit area at night.

Dimming is achieved by driving the LEDs with a duty cycle that can be varied from 1.56% through to 100% (full brightness) in 63 steps.

## Microcontroller outputs

Apart from the three shift LED outputs at pins 15, 16 and 17, there are two rev-limiting outputs at pins 18 and 1 (RA1 and RA2). Pin 1 (RA2) drives transistor




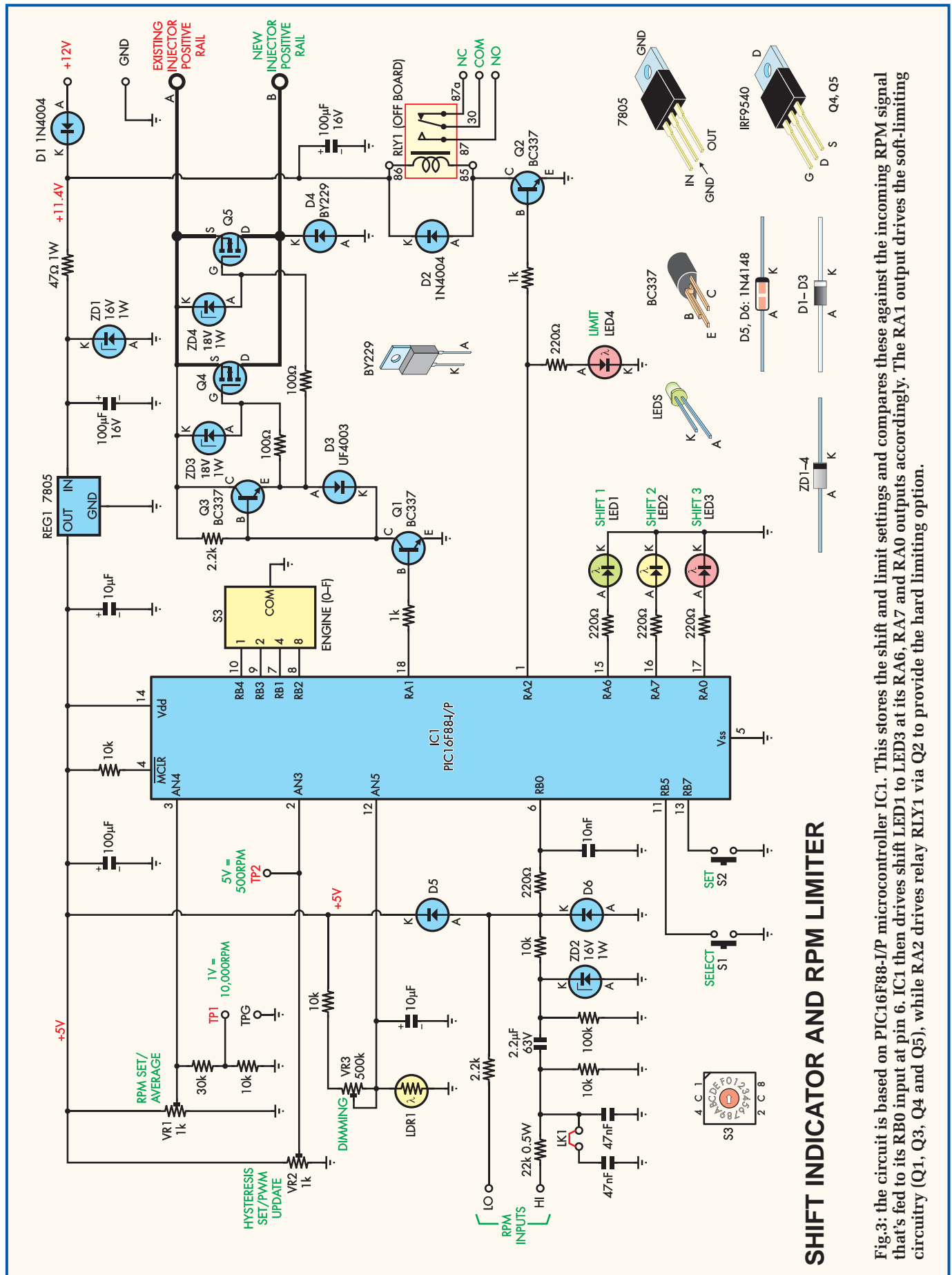


Fig.3: the circuit is based on PIC16F884-I/P microcontroller IC1. This stores the shift and limit settings and compares these against the incoming RPM signal that's fed to its RB0 input at pin 6. IC1 then drives shift LED1 to LED3 at its RA6, RA7 and RA0 outputs accordingly. The RA1 output drives the soft-limiting circuitry (Q1, Q3, Q4 and Q5), while RA2 drives relay RLY1 via Q2 to provide the hard limiting option.

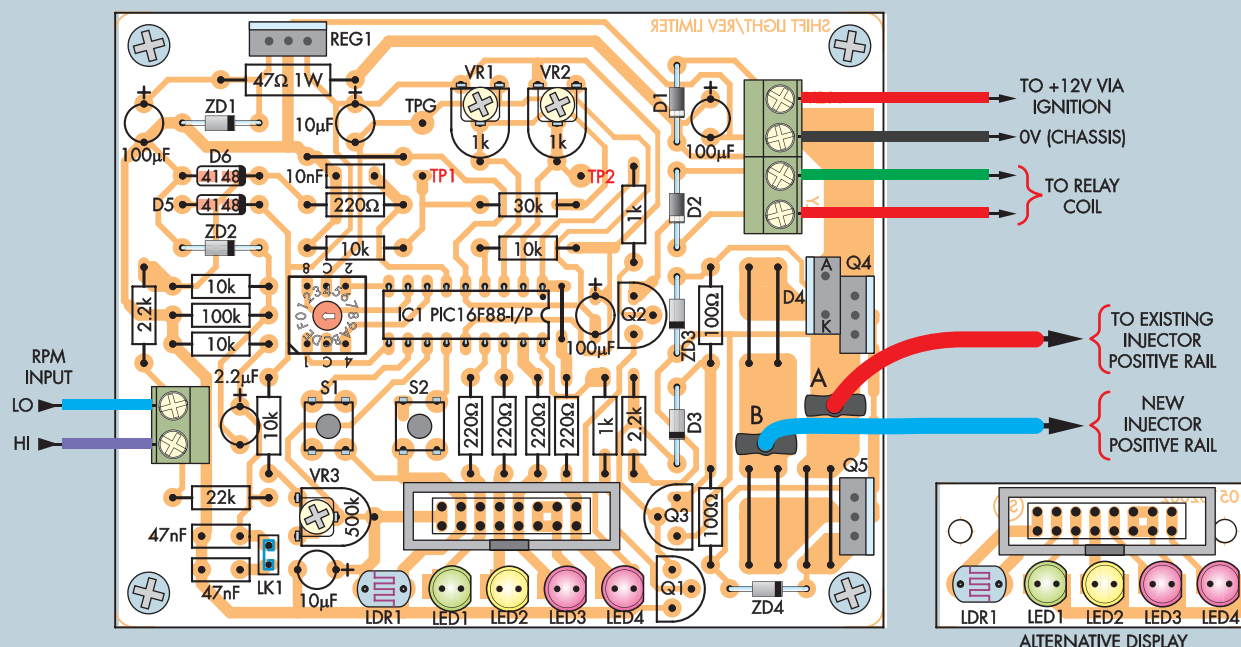

**Fig.4:** install the parts on the PC board as shown on this component layout diagram. You can either mount LED1 to LED4 and the LDR on the main board as shown, or you can mount these parts on a separate display PC board (shown at bottom right). The two boards are connected together via a 16-way ribbon cable fitted with IDC line plugs.

Q2, and this in turn drives an external relay (RLY1) for the hard limiting function. Diode D2 clamps any back-EMF spikes produced by the relay's coil when the transistor is switched off.

Pin 18 (RA1) drives transistor Q1 and this then drives the gates (G) of P-channel MOSFETs Q4 and Q5 for the soft-limiting function. Q4 and Q5 control the positive supply to the motor's fuel injectors, and this can be progressively reduced by varying the duty cycle of the pulse width modulation drive.

In operation, P-channel MOSFETs Q4 and Q5 provide 'high side' switching of the injector supply rail. Normally, the RA1 output pin is set high to turn on transistors Q1, Q4 and Q5 so that the injectors are fully powered. Above the set RPM limit, IC1's RA1

output (pin 18) will switch MOSFETs Q4 and Q5 with a duty cycle which is reduced gradually until there is no injector drive once the motor is over the set limit. The pulse frequency to the injectors is 30.5Hz.

MOSFETs Q4 and Q5 are driven in the following way: when Q1 is switched off, the base (B) of transistor Q3 is pulled high via a 2.2k $\Omega$  resistor to +12V. This turns on Q3, and so its emitter (E) pulls the gates of Q4 and Q5 towards the +12V supply and switches them off.

However, when Q1 is switched on, Q3 is switched off, and its emitter is pulled down to 0V via diode D3. This pulls the gates of Q4 and Q5 low and switches them on.

Diode D4 is included to protect Q4 and Q5 from the back-EMF spikes

produced by the injectors when they turn off.

## Power supply

Power for the circuit is derived from the vehicle's +12V rail via diode D1. This provides protection if the supply is connected the wrong way around. A 16V Zener diode (ZD1) clamps any spike voltages which may occur on the battery supply, and further filtering is provided by the 100 $\mu$ F capacitor for the supply to REG1, a 7805 5V regulator.

The 5V rail from REG1 is used to power IC1.


## Software

The software files are available via the EPE Library site, accessed via [www.epemag.com](http://www.epemag.com). Pre-programmed

### Table 1: Resistor Colour Codes

|   | No. | Value             | 4-Band Code (1%)          | 5-Band Code (1%)               |
|---|-----|-------------------|---------------------------|--------------------------------|
| □ | 1   | 100k $\Omega$     | brown black yellow brown  | brown black black orange brown |
| □ | 1   | 30k $\Omega$      | orange black orange brown | orange black black red brown   |
| □ | 1   | 22k $\Omega$      | red red orange brown      | red red black red brown        |
| □ | 5   | 10k $\Omega$      | brown black orange brown  | brown black black red brown    |
| □ | 2   | 2.2k $\Omega$     | red red red brown         | red red black brown brown      |
| □ | 2   | 1k $\Omega$       | brown black red brown     | brown black black brown brown  |
| □ | 5   | 220 $\Omega$      | red red brown brown       | red red black black brown      |
| □ | 2   | 100 $\Omega$      | brown black brown brown   | brown black black black brown  |
| □ | 1   | 47 $\Omega$ 1W 5% | yellow violet black gold  | not applicable                 |



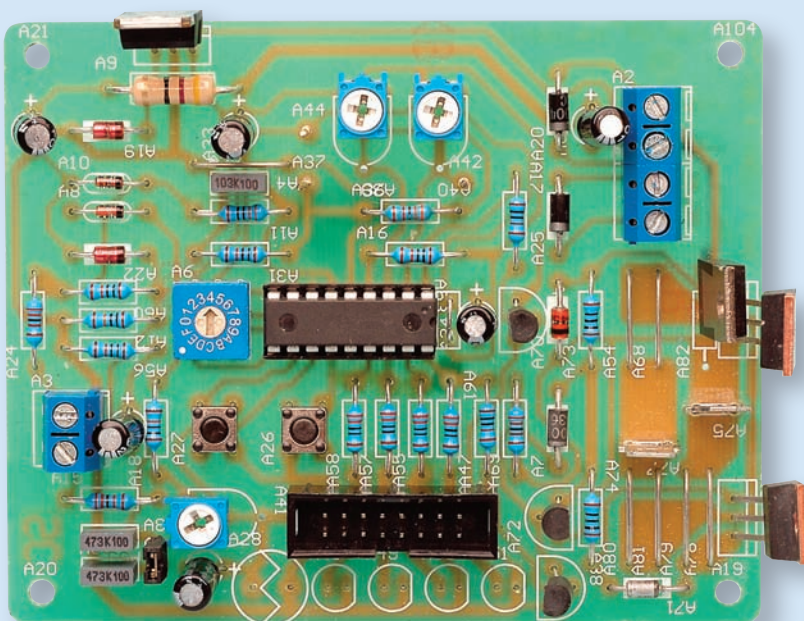

**Make sure that all polarised parts are correctly oriented when installing them on the board. The locating slot in the IDC header goes towards the bottom edge. Don't install the IC until the supply has been fully tested.**

PICs will also be available from Magenta Electronics – see their advert in this issue for contact details.

## Construction

The Shift Light Indicator is built on a PC board, code 749 Main (101 × 81mm), while a separate display board, code 750 Display (42 × 19mm) carries the display LEDs. Alternatively, the LEDs can be mounted on the main board. These boards are available as a set from the *EPE PCB Service*.

If you choose to use the separate display board, it's connected back to the main board via a 16-way ribbon cable fitted with IDC headers (Fig.6).

As usual, begin construction by checking the PC board for any defects such as shorted tracks and breaks in the copper. That done, check that the hole sizes are correct. The holes for the four corner mounting screws need to be 3mm in diameter, while the holes for the screw terminal blocks need to be 1.2mm.

Check also that the PC board fits into the box. If it doesn't fit, use a small file to round the corners until it does.

Fig.4 shows the parts layout on the PC board. Start the assembly by installing the wire links, followed by the resistors. Table 1 shows the resistor colour codes, but you should also check each one using a digital


multimeter before installing, as some colours can be hard to read.

Next, install the PC stakes for 'test points' TP GND, TP1 and TP2. That done, install the 2-way header for link LK1.

Follow these with the diodes and Zener diodes, taking care to install each with the correct orientation. Once these parts are in, install a socket for IC1 with its notched end towards Q2. Don't install the IC yet – that step comes later.

The capacitors can go in next, again taking care to ensure that the electrolytics are correctly oriented. That done, install transistors Q1 to Q5 and regulator REG1.

Note that REG1, Q4 and Q5 mount with their leads protruding through the bottom of the PC board by about 1mm. Later, this will leave sufficient

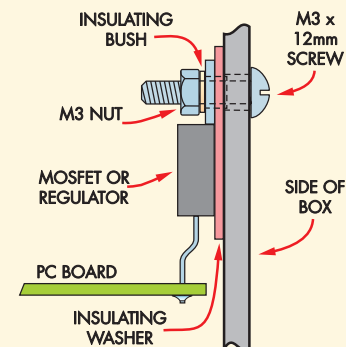

**Fig.5: the mounting details for REG1 and MOSFETs Q4 and Q5. Each device is electrically isolated from the case using an insulating washer and bush (see photo).**

lead length to allow the devices to be fastened to the side of the box.


Now install the trimpots and the BCD switch (S3). The correct orientation for S3 is with its corner dot to the lower left – see Fig.4. Switches S1 and S2 can now be inserted. These two switches will only fit on the PC board with the correct orientation.

The next step is to mount the two 6.8mm PC spade terminals, the 16-way IDC cable socket and the screw terminal blocks. Note that the 4-way terminal block consists of two 2-way blocks that are joined by sliding their moulded dovetails together.

## Display board assembly

Fig.4 also shows the display board assembly. It should only take a few minutes to assemble.

There are a couple of options here when it comes to mounting the LEDs and the LDR. One option is to bend the LED leads at right angles about 8mm from their bodies, and install them so that they sit at right angles to the PC board, as shown in the photo on the first page.

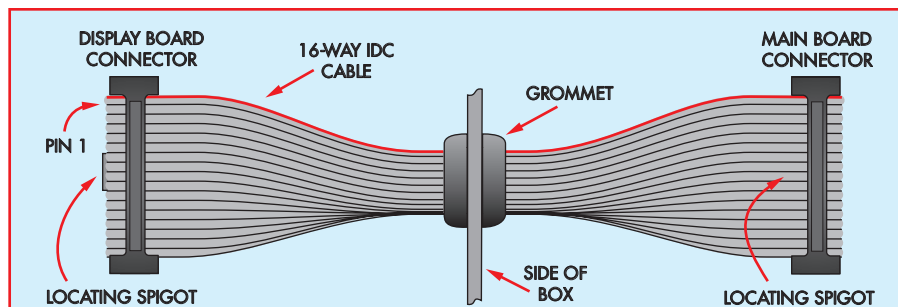

**Fig.6: here's how to make up the IDC cable that connects the display board to the main board. The header plugs can be clamped together using a small vice. Note the positions of the locating spigots on the plugs.**

## Features and specifications

### Features

- Three independent shift indicator LEDs
- One RPM limit LED
- Adjustable hysteresis for each shift setting and at the limit
- Relay switching of injectors at limit (hard limiting)
- Alternative soft limiting using pulse width modulation (PWM)
- Suits most petrol engines, including asymmetrical cylinder types
- Automatic dimming of shift LEDs and adjustable minimum brightness
- Easy adjustment of shift and RPM limit settings
- Easy engine selection – suits all engine types from 1 to 12 cylinders
- Easy adjustment of soft-limiting effect

### Specifications

**RPM accuracy:** typically <2% at 25°C with a 5.0V supply.

**Maximum shift and limit settings:** 12,500RPM for 1 to 12-cylinder 4-stroke engines (1 to 6-cylinder 2-stroke).

**Shift and limit RPM adjustment:** 0 to >12,500RPM in 25 RPM steps.

**Adjustment for RPM using VR1:** 1V = 10,000RPM, 0.5V = 5000RPM (5.0V supply).

**Hysteresis adjustment:** 0 to 500RPM in 2RPM steps

**Adjustment for hysteresis using VR2:** 1V = 100RPM, 5V = 500RPM (5.0V supply).

**Shift and limiting response:** RPM dependent (see Table 2). PWM limiting response is slowed using effects.

**Soft-limiting PWM:** 100% to 0% with a maximum of 250 steps over the hysteresis RPM range at a 30.5Hz rate.

**Soft-limiting effects:** PWM update after 1-16 PWM cycles, RPM measurement averaging over 1 to 64RPM values.

**Dimming of shift LEDs:** full range of 63 dimming steps from 1.5625% to 100% using PWM at 122Hz. The 0% PWM is not included. Minimum dimming can be adjusted to any one of the 63 settings.

Similarly, the LDR's leads can be bent at right angles about 11mm from its body before installing it on the board. A 7mm-wide cardboard spacer can be used to ensure that these parts all sit the same distance above the board.

Alternatively, you can push the parts right down onto the board so that the leads touch the board surface. Another option is to mount the LEDs and the LDR on the back of the PC board. It all depends on how you intend to ultimately mount the display board on the dashboard.

Whichever option you choose though, be sure to install each LED with the correct orientation – the anode (A) lead is always the longer

of the two. The LDR can go in either way around. Once these parts are in, install the IDC socket.

The other option is to install the LEDs and the LDR on the main PC board. In that case, you will have to later drill matching holes in the side of the case.

### Final assembly

A metal diecast case measuring 111 × 60 × 54mm is used to house the main board. This makes for a rugged assembly and provides heatsinking for regulator REG1 and the two power MOSFETs (Q4 and Q5).

The first step here is to drill the four mounting holes in the base for the

PC board. That done, fit four 10mm spacers to the case, then mount the board in position and secure it using M3 × 6mm screws and nuts.

Having secured the board, bend the leads for REG1, Q4 and Q5 so that their metal tabs sit flat against the sides of the case. Carefully mark out their tab mounting holes, then remove the PC board and drill these holes to 3mm. Be sure to de-burr each hole using an oversize drill to give a clean, flat surface (this is important to prevent punch-through of the insulating washers when the devices are secured to the case).

In addition, you will have to drill three 9.5mm holes in the side of the case to provide external wiring access. These holes should be opposite (and slightly above) the 2-way and 4-way terminal blocks and the IDC header. Use a small pilot drill to start these holes, then ream them to size and de-burr them before fitting the rubber grommets.

Note: the hole opposite the IDC header is not required if the LEDs and LDR are mounted on the main board. You will, however, have to drill five holes to accept the LED bodies and to allow light through to the LDR.

### Reinstalling the board

The PC board can now be reinstalled and REG1, Q4 and Q5 secured to the sides of the case. Note that their metal tabs must be electrically isolated from the case using TO-220 insulating washers and mounting bushes – see Fig.5. Each device is secured using an M3 × 10mm screw and nut.

Once these devices have been secured, use a multimeter to confirm that their metal tabs are indeed isolated from the case.

The IDC cable can now be installed. This is done by first rolling up the cable and feeding it through the hole opposite the IDC socket. The IDC plug can then be attached, making sure that the orientation is correct (see Fig.6). Use a small vice to clamp the header plugs together to secure the cable.

### Testing the PC board

The first step in the test procedure is to apply power to the +12V and 0V terminals on the 4-way terminal block. That done, check the voltage between pins 14 and 5 on the IC socket. This should be close to 5V (a range of 4.8V to 5.2V is acceptable).



If the voltage is below 4.8V, check for a short on the PC board. If there is no voltage, check that diode D1 is the right way around.

Assuming that everything is correct, switch off and install IC1 in its socket. It must be installed with its notched end towards transistor Q2.

Next, apply power and adjust trim-pot VR3 fully clockwise. Now press switch S1 and check that LED1 lights. Repeated pressings should now cause LED2, LED3 and LED4 to light in sequence, with only one LED on at a time. These correspond to the settings modes for Shift1, Shift2, Shift3 and Limit respectively.

If S1 is now pressed again, LED4 (Limit) should remain on while LED1 to LED3 should light up in sequence at a relatively fast rate. This is the soft limiting setting mode for the rev-limiting feature.

Pressing S1 yet again should turn on just LED1, LED2 and LED3. This is the selection for setting the minimum dimming level.

Finally, pressing S1 again should switch all the LEDs off. This returns the unit to its normal mode, whereby each LED lights when the incoming RPM signal reaches its respective threshold.

### Threshold adjustments

As noted already, trimpots VR1 and VR2 are used to set the Shift and Limit thresholds and hysteresis values.


The first step is to set these values for Shift1. The procedure is as follows:  
**Step 1:** press switch S1 so that LED1 lights.

**Step 2:** attach a multimeter between test point TP1 and TP GND, and adjust VR1 to set the desired RPM threshold. Note that the voltage on TP1 is directly related to the RPM setting, where 1V represents 10,000RPM. To set a 4000 RPM threshold, for example, adjust VR1 for a reading of 0.4V (400mV).

Note also, due to trimpot resolution, that you may not be able to adjust the voltage to better than 5mV (equivalent to 50 RPM) of the desired value.

**Step 3:** connect a multimeter between test point TP2 and TP GND.

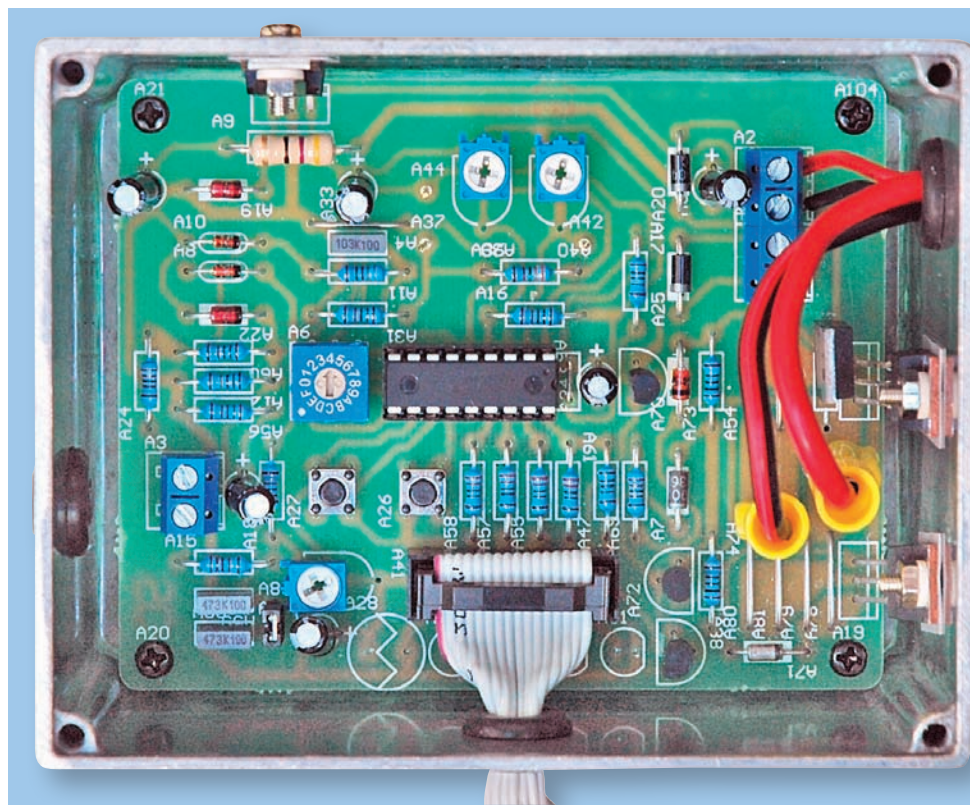**Step 4:** adjust VR2 to set the RPM hysteresis value. This can be adjusted from 0-500RPM. Note that 5V at TP2 sets the hysteresis to 500RPM, 4V gives 400RPM, and so on.



The PC board is mounted inside the case on 10mm spacers and secured using M3 × 6mm screws. REG1, Q4 and Q5 are then bolted to the case – see Fig.5. Note that the wiring to the fuel injectors is not required if you opt for hard limiting.

**Step 5:** press Set switch S2 to program the RPM threshold and hysteresis adjustments for Shift1 into IC1. LED1 will now flash five times to indicate that these settings have been saved.

Note: if you require the highest possible accuracy, you will have to scale the adjustment voltages to compensate for REG's output (ie, if this is not exactly +5V). In practice, it's just a matter of multiplying the threshold RPM required by the measured supply voltage and dividing the result by 5V.

For example, let's say that you want to set the RPM threshold to 4000RPM and that the supply voltage is 4.95V. In that case, the calculation is  $4000 \times 4.95V / 5V$ , or 3960. So, to adjust for 4000RPM when the supply is 4.95V, you must set VR1 to give 0.396V at TP1.

**Step 6:** press S1 so that LED2 lights and repeat the above steps (through to Step 5) to set the threshold and hysteresis values for Shift2. Repeat this procedure to set the values for Shift3, making sure each time that the correct LED is selected.

Don't forget to press S2 to save the changes each time you adjust VR1 and VR2 for each Shift setting. This must be done before moving on to the next

Shift light, otherwise the settings will not be saved.

### Rev limit adjustments

Now for the rev limit adjustments. Just follow these steps:

**Step 1:** press S1 after the Shift3 settings have been saved. This turns LED4 (Limit) on, while all the other LEDs are off.


**Step 2:** monitor the voltage at TP1 and adjust VR1 to set the rev limit. As before, 1V is equivalent to 10,000 RPM, so to set a limit of 6000RPM, for example, set VR1 for a reading of 0.6V.

**Step 3:** monitor TP2 and adjust VR2 to set the rev limit hysteresis. In this case, 1V is equivalent to 100RPM.

If you intend using PWM limiting, so that the engine power drops off gradually, use an initial value of 500 RPM (5V at TP2). Alternatively, if you intend using relay limiting, set the value to 200RPM (2V at TP2).

**Step 4:** press S2 to save these settings.

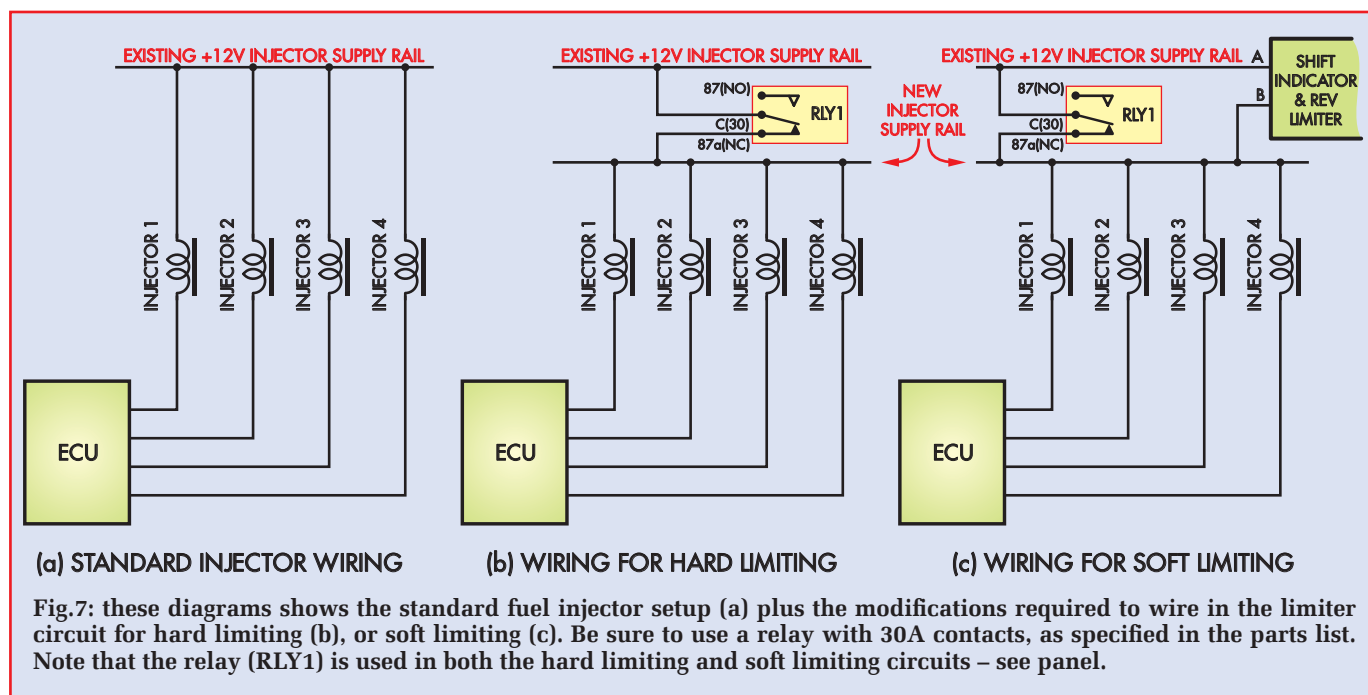**Step 5:** press S1 to bring up the soft limiting adjustment mode – ie, LED4 lit and LED1 to LED3 lighting in sequence.



Trimpot VR1 now adjusts the number of RPM calculations that are used in averaging the RPM reading, while VR2 adjusts the rate at which the PWM (pulse width modulation) that provides the soft limiting changes.

Setting VR1 fully clockwise gives an average of 64RPM calculations, while setting VR2 fully clockwise gives 16 PWM cycles before changes occur. Conversely, fully anticlockwise settings for VR1 and VR2 give no averaging and a PWM that can change with each cycle.

Setting both VR1 and VR2 to mid-way would provide a suitable soft limiting effect for most engines. However,

if the soft limiting subsequently proves to be too soft, so that the engine RPM overshoots the desired limit by a large margin, then the trimpots should be adjusted further anticlockwise.

Note that VR1 has an effect on both the soft limiting smoothness and the response time when it comes to limiting the engine RPM. Trimpot VR2 only affects the RPM limiting response speed.

**Step 6:** press S2 to save the soft limiting settings.

## Dimming adjustments

Pressing S1 again brings up the dimming adjustment mode (LED1 to LED3 all lit, LED 4 off).

It's now just a matter of covering the LDR sufficiently (both front and back) to bring the LED brightness down to the minimum level you require and then pressing the Set switch (S2) to save the setting. The three LEDs will then flash five times to indicate that this has now been stored.

Note that the above procedure is best carried out in a room with a low ambient light level (but not dark).


That done, adjust VR3 to set the ambient light level threshold at which dimming begins (this may take some trial and error).

By the way, changing the 10 $\mu$ F capacitor at pin 12 of IC1 to 1 $\mu$ F will increase the rate at which the LEDs dim or become brighter in response to ambient light changes.
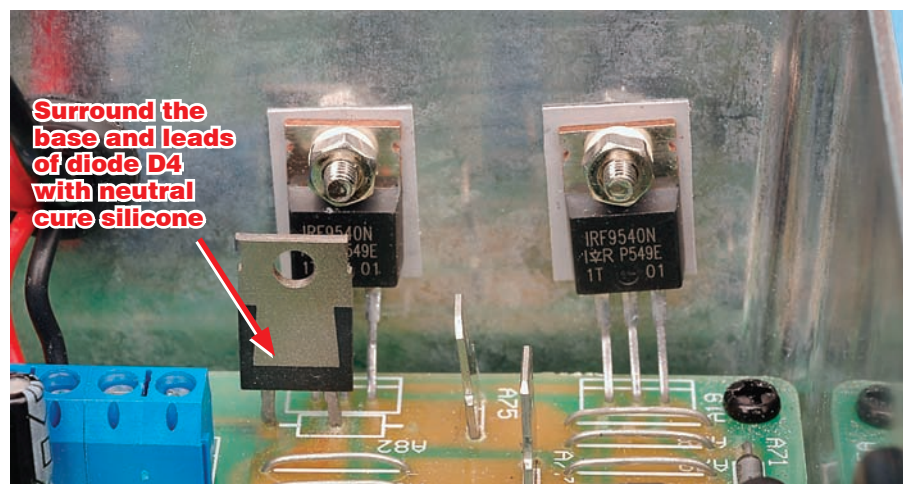
## Installation

The unit is relatively straightforward to install, and requires only a limited amount of external wiring. This involves wiring for the +12V and ground (0V) connections, the rev signal input and the connections to the fuel injectors.

The +12V supply can be obtained from the fusebox and must be switched on (or off) by the ignition. Note, however, that this supply rail must remain on when the engine is being cranked (ie, when the starter motor is running). The 0V rail can be connected to the vehicle's chassis. These supply connections can be



This view shows how power MOSFETs Q4 and Q5 are bolted to the case and their tabs isolated using insulating washers and bushes. Voltage regulator REG1 mounts in a similar fashion – see also Fig.5. Note that diode D4's leads should be surrounded with neutral-cure silicone to prevent them from vibrating and breaking.



## Parts List – Shift Indicator and Rev Limiter for Cars

1 PC board, code 749 (Main), size, 101 × 81mm  
 1 PC board, code 750 (Display), size, 42 × 19mm  
 Available as a set from the *EPE PCB Service*  
 1 diecast case, 111 × 60 × 54mm  
 1 SPDT 30A horn relay  
 1 relay base to suit horn relay (optional)  
 3 2-way PC-mount screw terminals (5.08mm spacing)  
 1 PC-mount 0-F BCD DIL switch (S3)  
 2 SPST micro tactile switches (S1, S2)  
 2 16-way IDC PC-mount headers  
 2 16-way IDC line plugs  
 2 6.8mm PC-mount spade terminals  
 2 6.8mm insulated spade crimp connectors  
 3 rubber grommets for 6mm cable diameter  
 3 TO-220 silicone insulating washers  
 3 3mm insulating bushes  
 4 M3 × 10mm tapped nylon standoffs  
 8 M3 × 6mm screws

3 M3 × 10mm screws  
 3 M3 nuts  
 1 2-way header with 2.54mm spacing (LK1)  
 1 jumper plug (for LK1)  
 3 PC stakes  
 1 1m length of 16-way IDC cable  
 1 160mm length of 0.8mm tinned copper wire  
 1 1m length of figure-8 20A automotive wire  
 1 1m length of red medium-duty automotive wire  
 1 1m length of black medium-duty automotive wire

### Semiconductors

1 PIC16F88-I/P microcontroller, pre-programmed – see text (IC1)  
 1 7805 +5V 3-terminal voltage regulator (REG1)  
 2 IRF9540 P-channel MOSFETs (Q4, Q5)  
 3 BC337 NPN transistors (Q1-Q3)  
 2 1N4004 rect. diodes (D1, D2)  
 1 UF4003 ultrafast diode (D3)  
 1 BY229 fast diode (D4)  
 2 1N4148 signal diodes (D5, D6)  
 2 16V 1W Zener diodes (ZD1, ZD2)

2 18V 1W Zener diodes (ZD3, ZD4)  
 1 5mm high-intensity green LED (LED1)  
 1 5mm high-intensity yellow LED (LED2)  
 2 5mm high-intensity red LEDs (LED3, LED4)

### Capacitors

3 100µF 16V radial elect.  
 2 10µF 16V radial elect.  
 1 2.2µF 63V radial elect.  
 2 47nF MKT polyester  
 1 10nF MKT polyester

### Resistors (0.25W 1% metal film)

1 100kΩ      2 1kΩ  
 1 30kΩ      5 220Ω  
 1 22kΩ 0.5W    2 100Ω  
 5 10kΩ      1 47Ω 1W  
 2 2.2kΩ

### Trimpots and LDR

2 1kΩ horizontal mount trimpots (VR1, VR2)  
 1 500kΩ horizontal mount trimpot (VR3)  
 1 LDR (50kΩ light and 10MΩ dark resistance) (LDR1)

run using medium-duty automotive hook-up wire.

The rev signal can be derived from the coil's negative terminal, and this wire connects to the HI input. Alternatively, in a multi-coil car, you can use the ECU tachometer signal, and this should go to the LO input.

### Injector wiring

Fig.7(a) shows the basic set-up for standard injector wiring. Note that the engine management system (ECU) switches the negative side of the fuel injectors.

**The first step is to disconnect the injectors from their existing common positive supply rail.** After that, it depends on whether you are opting for hard limiting or soft limiting.

If you are opting for hard limiting, it's simply a matter of wiring in the relay as shown in Fig.7(b). This involves first connecting the vehicle's existing +12V injector supply rail to the relay's common (C) contact. The normally closed (NC) contact is then connected to the positive injector terminals.

## Why use the relay with soft limiting?

Strictly speaking, if you elect to use soft rev limiting, the relay shown in Fig.7(c) is optional. However, we still recommend wiring it into the circuit for a couple of reasons.

First, by using the relay as shown, its NC contacts take the load off the soft limiting MOSFETs (Q4 and Q5) during normal engine operation. However, if the rev limit is reached, the relay quickly opens and the MOSFETs then take over to provide the soft limiting function – ie, they pulse-width modulate the new injector supply rail.

Second, the relay's contacts ensure that the injectors are still supplied with power during normal running if the MOSFETs become faulty or if a fault develops in the unit which switches them off. For this reason, we strongly recommend that you include the relay as shown in Fig.7(c) – it's a worthwhile safety and reliability feature.

**Note that all wiring to the relay contacts and to the injectors should be run using 20A automotive cable.**

Note also that, for hard limiting, no connections are made to points A and B on the circuit board.

Alternatively, if you are opting for soft limiting, then you need to wire the injectors as shown in Fig.7(c). In this case, **the vehicle's existing injector**

**positive supply rail is connected to point A on the main PC board. Point B on the circuit board then becomes the new injector positive supply rail.**

The relay is also wired into the circuit as before. Once again, be sure to use 20A automotive cable for the wiring to the injectors, the relay contacts and to points A and B on the PC board.

**Table 2: BCD switch settings and details for various engine types**

| BCD switch setting (S3) | Cylinders (4-stroke)  | Cylinders (2-stroke) | Pulses per RPM | RPM counter               | Frequency/1000 RPM | Shift light response @ 1000 RPM | Shift light response @ 2000 RPM |
|-------------------------|-----------------------|----------------------|----------------|---------------------------|--------------------|---------------------------------|---------------------------------|
| 1                       | 1                     | –                    | 0.5            | Between each pulse        | 8.33Hz             | 120ms                           | 60ms                            |
| 2                       | 2                     | 1                    | 1              | Between each pulse        | 16.66Hz            | 60ms                            | 30ms                            |
| 3                       | 3                     | –                    | 1.5            | Between each pulse        | 25Hz               | 40ms                            | 20ms                            |
| 4                       | 4                     | 2                    | 2              | Between each pulse        | 33.33Hz            | 30ms                            | 15ms                            |
| 5                       | 5                     | –                    | 2.5            | Between each pulse        | 41.66Hz            | 24ms                            | 12ms                            |
| 6                       | 6                     | 3                    | 3              | Between each fourth pulse | 50Hz               | 20ms                            | 10ms                            |
| 8                       | 8                     | 4                    | 4              | Between each fourth pulse | 66.66Hz            | 15ms                            | 7.5ms                           |
| 9                       | Asymmetric 3-cylinder | –                    | 3 over 2 RPM   | Between each fourth pulse | 25Hz               | 80ms                            | 40ms                            |
| A                       | 10                    | 5                    | 5              | Between each fourth pulse | 83.33Hz            | 12ms                            | 6ms                             |
| B                       | Asymmetric 2-cylinder | –                    | 2 over 2 RPM   | Between each fourth pulse | 16.66Hz            | 120ms                           | 60ms                            |
| C                       | 12                    | 6                    | 6              | Between each fourth pulse | 100Hz              | 10ms                            | 5ms                             |

Note that this wiring is run to the main board by feeding it through the adjacent rubber grommet and terminating it with spade crimp connectors. These connectors are then plugged into the A and B terminals.

Make sure that the crimp connections are nice and tight to ensure reliability and be sure to plug each into its correct terminal. A proper ratchet-driving crimping tool is a necessity here.

It's vital that all wiring is installed in a professional manner to ensure reliability. That means using proper

automotive connectors to terminate the wiring and securing the wiring with tape and cable ties.

## Testing

Once the wiring is complete, set the BCD switch to the number that suits your engine – see Table 2.

That done, start the engine and rev it to check that the shift and limit LEDs light at their correct RPM values. If you haven't programmed the unit yet, the initial settings are 1000RPM for shift1, 2000RPM for shift2, 3000RPM for shift 3 and 4000RPM for the limit.

The hysteresis is 200RPM for shift1 and 500RPM for the other thresholds.

If the shift points are incorrect and you are using the HI input, try installing link LK1 to change the input filtering. Alternatively, if you are using the LO input, LK1 has no effect and no adjustments to the input filtering should be necessary.

If the LEDs do not light at all, check that the RPM input signal is correctly connected.

## Peak hold injectors

Finally, note that the soft limiting option is **not** suitable for injectors that operate with a so-called peak hold drive. This is where an initial high current is used to close the injector, but then the current is reduced by rapidly switching the injector signal on and off (this keeps the injector open, but with reduced power to the injector solenoid).

Note, however, that you can use the hard limiting option, provided that the relay contacts can handle the peak currents that drive this type of injector.

How can you tell if you have a peak hold injector? It will typically have a solenoid coil resistance of less than 1Ω ('normal' injectors typically have a resistance of 4Ω to 5Ω). **EPE**

## Determining the shift points

How do you determine the best shift points to program into the Shift Indicator and Rev Limiter? In most cases, it's just a matter of driving the car and noting down a sensible RPM value for each gear change. The values can then be programmed into the unit, after which it's simply a matter of monitoring the LEDs to pick the gear-change points.

Alternatively, as mentioned in the text, you could set the three LEDs to give a 'ready', 'set' and 'go' indication for each gear change.

The rev limit can simply be set to just under the tacho's redline value. Note, however, that many modern cars include rev limiting as part of their engine management system. In that case, you won't need the rev limiting feature provided by this unit, and it's just a matter of leaving out the wiring between this unit and the fuel injectors (you can also leave out the relay, power MOSFETs Q4 and Q5 and transistors Q1-Q3).

If you are modifying a car for racetrack use, then the shift points would be set much more aggressively – typically at those points that provide maximum acceleration. In some cases, you might want to set the shift points at close to engine redline. In other cases, it may be a matter of picking the maximum engine power points.

Reproduced by arrangement  
with SILICON CHIP  
magazine 2010.  
www.siliconchip.com.au



THE ORIGINAL SINCE 1994  
**PCB-POOL**<sup>®</sup>  
 Beta LAYOUT  
 Specialising in Prototype PCBs

**NEW!** Free Laser Stencil  
 with all Prototype  
 PCB orders

**NEW!** 1 WD prototype  
 service

**NEW!** Chemical Tin Finish  
 (no extra cost)


Free  
 Phone  
 UK 0800 389 8560

@ Simply send your layout files  
 and order ONLINE  
 PCB-POOL.COM • sales@pcb-pool.com

Beta  
 LAYOUT

Free 2009 **Designer** **ETAN** cadence GraphiCAD **PRINTES** NATIONAL INSTRUMENTS Easy-PC **PULSONIX**

# CGR-101 7-in-1 USB Instrument

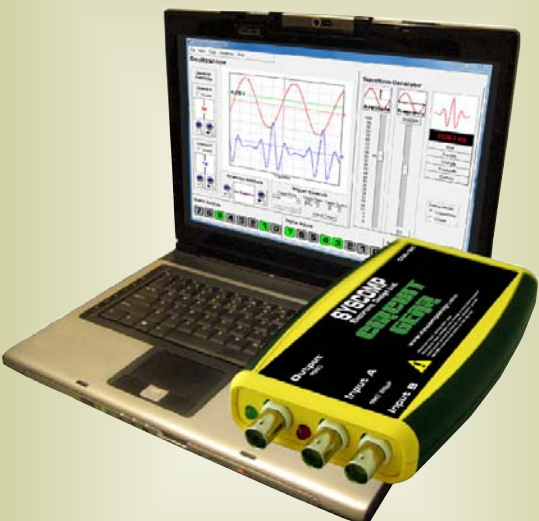

A USB-based 2-Channel Oscilloscope,  
 Waveform Generator, and Digital I/O port  
 integrated into one small, low cost unit.

Learn more: [www.audon.co.uk/cgr101.html](http://www.audon.co.uk/cgr101.html)

**audon** Electronics  
[www.audon.co.uk](http://www.audon.co.uk) | +44 (0)115 925 8412 | Fax +44 (0)115 925 9757

ANDRE LAMOTHE'S  
**XGAMESTATION**  
 LEARN STEP-BY-STEP HOW TO DESIGN  
 AND BUILD YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the Atari 800/2600,  
 Sinclair ZX Spectrum, Apple II & Commodore 64!

Complete Package eBook Integrated IDE

SX52 CPU  
 80 MIPS!

OPEN SOURCE!

**FEATURES:**

- Great for Hobbyists AND Students!
- Complete Software Development Kit!
- eBook on Designing the XGS Console!
- Parallax SX-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC  
 COMPATIBLE!

WWW.XGAMESTATION.COM  
 SUPPORT@NURVE.NET | PH 512.266.2399(USA)

**www.epemag.com**

# MAGENTA

## ELECTRONICS LTD

### MICROSTEPPER Stepping Motor Driver

May 09 EPE. 1/2 1/4 1/8 and 1/16  
 microstep driver for standard 4 phase  
 unipolar motors. Up to 46V at 3A.

Adjustable current with efficient  
 PWM control. Opto isolated in-  
 puts and outputs for computer  
 (LPT)# or logic level control.  
 SLA7062M driver chip contains  
 all sequencer logic - Only needs  
 Step and Direction inputs.  
 Kit includes PTH circuit board  
 Chip, and all components.  
 # Connection details and (Slow  
 speed) demo PC software: free  
 download from website.

**KIT 920**  
**£18.76**

**Special Offer - Kit 920 + MD23**  
**200 Step motor £31.91**

### 20W Stereo Amp.

Low distortion 11W/channel  
 Stereo/20W Mono. True (rms) Real  
 Power. High Slew Rate/bandwidth  
 & low noise. Ideal MP3 booster.  
 Short Circuit & Overtemp. Protect-  
 ed. STA7360 chip. Needs 8 to 18V  
 supply. EPE Project May2005.

**KIT 914**  
**£11.90**

Includes  
 all parts &  
 heatsink  
 for stereo  
 & mono

All Prices Include VAT, Add £3.00 P&P per order, or £7.99 for next  
 day. Chqs. P.O. & most major cards accepted. Mail Order Only.

135 Hunter Street Burton on Trent Staffs DE14 2ST  
 Tel: 01283 565435 Fax: 01283 546932  
[www.magenta2000.co.uk](http://www.magenta2000.co.uk) sales@magenta2000.co.uk



# Recycle It!



BY JULIAN EDGAR

## Using the convex lenses from fancy car headlights

**Good quality convex lenses can be salvaged for next to nothing from car wrecking yards. Here's how to use them to make a really bright handheld spotlight or a broad-beam bike light.**

**W**HEN you watch cars go by at night, you can see a variety of headlight designs on display. For example, old cars use sealed beams, which are often rather yellow in appearance. Then there are the whiter designs with replaceable halogen bulbs, while recent luxury cars feature high intensity discharge lights, which have a brilliant blue/white colour.

There are also lights that, when viewed at an angle, appear to have red or blue beams graduating to white as the car is seen face-on. These headlights have an abrupt beam cut-off and a very even spread of light within the beam. They are known as 'projector' headlights, and use a simple reflector teamed with a large convex glass lens.

Want to know something? Those large glass lenses can be obtained for nearly nothing from broken headlights at car breaker's yards. Want to know something else? They make excellent lenses for use in bike lights, torches and handheld spotlights.

### Projector headlights

A typical projector car headlight is shown in Fig.1. From the front, there's a cover plate of glass or plastic. Behind that is the convex glass lens (normally used only on low beam), followed by the bulb and then a simple reflector. The bulb is masked so that the upper part of the beam is abruptly cut off, to avoid blinding oncoming drivers.

The single headlight assembly also contains a high beam, which usually comprises a conventional halogen lamp and a reflector. The headlight is near worthless to car breaker's if the cover glass is broken, the high beam is broken, the low beam is broken or the rear plastic housing is shattered.

However, if the low beam convex glass lens is intact, the convex lens can be bought for next to nothing. For example, at a major wrecking yard, I found and salvaged three convex lenses and took them to the front counter.

I made the point that I hadn't needed to break any headlights to obtain the lenses and asked for a price. The man behind the counter was puzzled: what on earth did I want these lenses for? I told the truth – I was making a bicycle headlight – and he charged me £6 for all three.

On another occasion, when I was buying some other car bits, the convex lens didn't cost me anything extra.

Many recent cars have projector headlights; but also some older cars,



A projector headlight is easily recognised because of its convex glass lens.





Large convex glass lenses are easily salvaged from wrecked car headlights that use a 'projector' design. These lenses use high transmission glass and are optically accurate.

for example the Mazda 626 and Ford Mondeo. Some Nissan model's also have them, including one car that has two such lenses each side.

If you are salvaging the lens from a headlight with a broken cover glass, be very careful. It is extremely easy to cut yourself on the shards of glass, especially if you slip while wielding a screwdriver.

Incidentally, smaller lenses of a similar shape can also be salvaged from old slide projectors.

## Using the lens


So you have a bunch of high-quality, large, convex glass lenses that you've obtained for next to nothing. Now what? I could get all theoretical and talk about focal lengths, beam angles and point sources, but let's forget all that. The easiest way of coming up with the best design for your particular application is to simply play around with the light source and the different lenses.

For example, a Luxeon LED makes an excellent light source because it is small, very bright and has high efficacy. Power-up the LED (after mounting it on a suitable heatsink if it's a 3W or 5W design) and hold the convex lens in front of it.

Now view the beam pattern on a wall or the ceiling. By altering the distance between the lens and the LED, it's possible to change the beam from a broad diffuse beam to a narrow spot. In the case of the Luxeon, you can also try matching the glass lens with the various collimators available for these LEDs.



This photo shows the components needed for a bright, wide-angle light (from left and then clockwise): convex glass lens salvaged from a projector car headlight; shortened stainless steel drinking cup and bracket made from aluminium angle; and a 1W Luxeon LED and narrow angle collimator mounted on a salvaged aluminium block. Missing from this photo is a cut-down uPVC plumbing cap to hold the lens in place over the end of the cup.

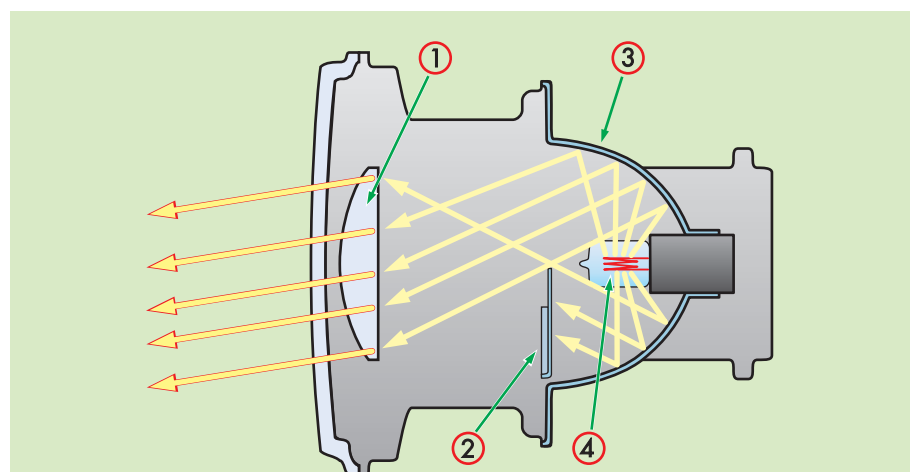

**Fig.1:** this diagram shows a 'projector' type car headlight. The main optical element is a large convex glass lens mounted within the headlight assembly (1) and this replaces the reflector and flat glass lens used on other headlights. A shield (2) prevents on-coming driver glare, while (3) is the rudimentary headlight reflector and (4) is the bulb. [Bosch]

The lenses can also be used with conventional incandescent bulbs and reflectors (and incidentally, lots of working torches with perfectly good reflectors are thrown away each day).

Again, it's a case of trying different combinations and looking at the results.

If the lens is placed very close to the light source, it's possible to get an extremely broad beam, which greatly

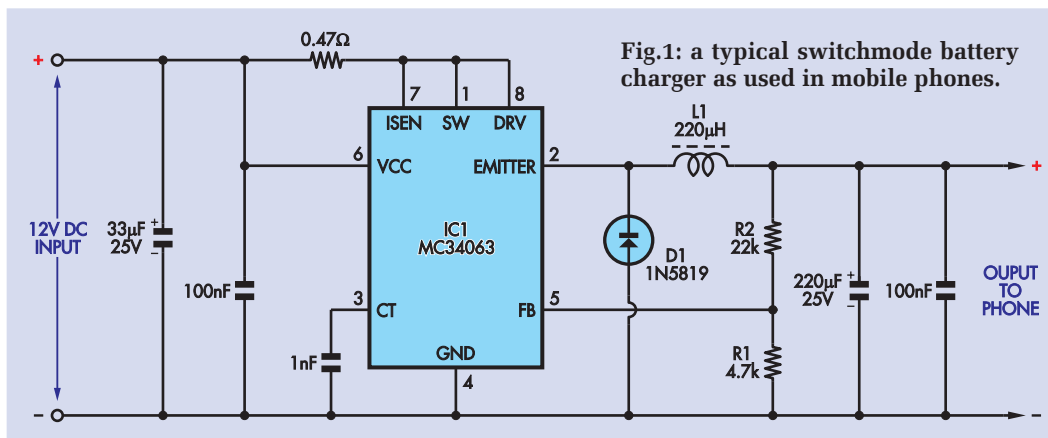


Fig.1: a typical switchmode battery charger as used in mobile phones.

connect anything to the metal heatsink of the Star; this **must** be isolated from the power supply terminals.

If you'd like to test the unit before connecting your (expensive) LED, temporarily connect a 10Ω 5W resistor in its place. Apply 9V to 24V to the input and measure the voltage drop across the 10Ω resistor; it should

remain constant at about 3.2V.

Note that not all chargers have an output filter capacitor installed. Typically, this is a 220μF 10V or 16V electrolytic unit. To save a few cents, the manufacturers sometimes leave this component out, relying on the mobile's battery to perform the filtering task.

If the 220μF capacitor is missing from your charger's PC board, it should be installed *before* the supply is used. Use a 25V rated part if you intend to power the unit from more than 16V. This allows for accidental disconnection of the LED with power applied, where the output voltage will rise close to the input voltage.

Finally, data on the MC34063 can be downloaded from [www.onsemi.com](http://www.onsemi.com) and a useful development aid is to be found at [www.nomad.ee/micros/mc34063](http://www.nomad.ee/micros/mc34063)

Dave Sime,  
Hughes, ACT.

## Cheap 1W Luxeon LED driver

Step-down switchmode power supplies are often used in preference to their linear counterparts in applications where there is a large input to output voltage differential. Such is the case when driving Luxeon 1W Stars and their derivatives from a 12V DC source, which is the focus of this circuit.

Mobile phone chargers based on the MC34063 switchmode controller IC are easily modified to operate as a simple constant-current source, suitable for powering a single 1W white or blue LED, or two 1W red LEDs in series. Defunct mobile phone chargers are readily available at local markets and on [ebay.com](http://ebay.com) for a few pounds.

These units are quite easy to pull apart. First, unscrew the metal nipple from the end and remove the fuse, then prise off the metal collar that holds the two halves together. You can then easily separate the two halves and extract the circuit board.

The circuit shown in Fig.1 is typical of most chargers, with some

including a few extra components for indicator LEDs. Resistors R1 and R2 set the regulated output voltage, which can be calculated using the formula  $V_{OUT} = 1.25(1 + R2/R1)$ . This will result in a 7.1V output using the values shown.

Because the MC34063 strives to maintain a constant 1.25V across R1, we can replace R2 with our 1W LED (Fig.2) and select a much smaller value for R1 using the formula  $I = 1.25/R1$ . Using a value of 3.9Ω, about 320mA of regulated current will flow through the LED.

To modify the charger, start by removing R1 and R2. Note that the labelling of the resistors on the circuit board will probably be different; use your multimeter or follow the tracks on the board to identify the resistors of interest.

Replace R1 with a 3.9Ω 1W resistor and wire the Luxeon Star into the R2 position using medium gauge hook-up wire. Keep the wire length as short as possible and make sure that you've connected the anode (+) to the positive output and the cathode (-) to the junction of R1 and R2. Do not

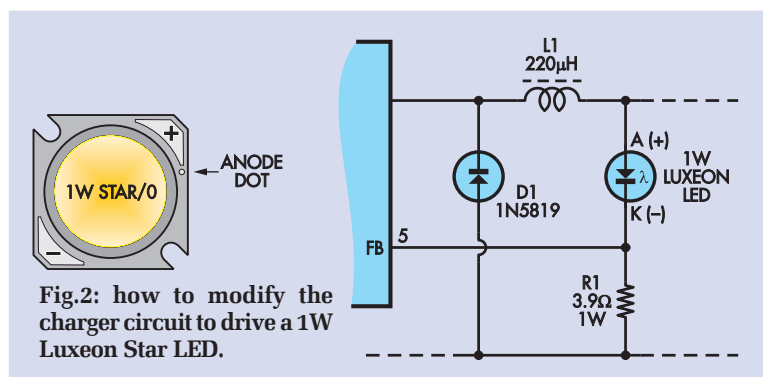


Fig.2: how to modify the charger circuit to drive a 1W Luxeon Star LED.



It's quite easy to modify a discarded mobile phone charger to drive a 1W Luxeon Star LED.





The Luxeon LED, its collimator and the mounting block are attached to the base of the cup using screws and nuts. The convex lens fits over the mouth of the cup to provide a broad, even beam.



Here the lens has been reversed compared to its normal automotive orientation, with the curved (convex) side facing the light source. This design is being used as a rear light on a road-going recumbent pedal trike.

enhances its visibility at night. It's just the shot for a flashing warning light or bicycle tail-light.

## Building a compact light

I used a convex lens from a car headlight to make a very bright, broad beam, flashing tail-light for a bike.

First, a stainless steel drinking cup was shortened in length using a hacksaw and file. This gave a housing with an opening that matched the diameter of the lens. A 1W red Luxeon LED and

a narrow-beam collimator were then installed on a small block of aluminium (a 1W Luxeon doesn't need a heatsink, but having one doesn't hurt), after which the block was mounted in the base of the cup.

Next, a uPVC plastic pipe cap to suit the diameter of the lens was obtained, and its inner diameter cut out with a holesaw. This gave a flange that fitted over the end of the cup, holding the lens in place. Silicone sealant was then used to secure the cap in place and to weatherproof the opening.

In this application, the best results were obtained by reversing the lens as compared to its normal car orientation – ie, it was mounted with the convex part of the lens facing the LED.

The Luxeon LED was powered by a 12V cigarette lighter phone charger adaptor, which was modified to act as

## Stainless steel cup

As detailed in the main text, a stainless steel drinking cup makes an excellent housing for the convex lens.

Single-wall stainless steel drinking cups can be hard to find, but a double-wall (ie, insulated) cup can be used instead, although it is heavier and a little more difficult to cut and drill.

## They're glass!

The convex lenses salvaged from car headlights are made from high quality optical glass. So if you drop them, hit them or squeeze them hard enough, they'll shatter!

## Rat It Before You Chuck It!



Whenever you throw away an old TV (or VCR or washing machine or dishwasher or printer) do you always think that surely there must be some good salvageable components inside? Well, this column is for you! (And it's also for people without a lot of dough.) Each month we'll use bits and pieces sourced from discards, sometimes in mini-projects and other times as an ideas smorgasbord.

And you can contribute as well. If you have a use for specific parts which can

easily be salvaged from goods commonly being thrown away, we'd love to hear from you. Perhaps you use the pressure switch from a washing machine to control a pump. Or maybe you have a use for the high-quality bearings from VCR heads. Or perhaps you've found how the guts of a cassette player can be easily turned into a metal detector. (Well, we made the last one up but you get the idea . . .)

So, if you have some practical ideas, do write in and tell us!

a constant current source (see 'Cheap 1W Luxeon LED Driver' on the opposite page).

So why go to all this bother when LED tail-light flashers are cheaply available? Well, you've never seen a flasher like this. It is extremely bright from directly behind and can be seen at distances of 500 metres or more.

The convex lens creates a broader beam than would otherwise be achieved, allowing the light to be visible over a much wider angle than just having the LED on its own. This effect is further enhanced by reflections from the internal walls of the stainless steel cup.

**EPE**

Reproduced by arrangement  
with SILICON CHIP  
magazine 2010.  
[www.siliconchip.com.au](http://www.siliconchip.com.au)

# TEACH-IN 2010

## LADDER LOGIC PROGRAMMING FOR THE PIC MICRO

### Part 5: Advanced Programming and Interfacing Techniques

By Walter Ditch



**T**HE fifth and penultimate part of this series begins by exploring basic concepts related to hardware interfacing, including methods of connection to input devices such as switches, and to outputs including LEDs, 7-segment displays, relays, solenoids and motors. This knowledge will give you an appreciation of the hardware design of an actual industrial PLC – although, of course, the circuits considered will be rather more basic than those of a commercially available product. Hardware design is also important in embedded control applications, where the PIC becomes an integral part of an electronic system, adding intelligence and flexibility.

We'll also use the chosen examples to demonstrate the use of computer-based electronic simulation software, as illustrated by Proteus VSM from Labcenter Electronics. A number of tips and suggestions will be provided for those users wishing to combine PLC-style program development with use of electronic simulation software.

The article concludes by discussing a range of programming concepts, which have been grouped together under the umbrella term of 'advanced programming'. Topics covered include:

- Byte-oriented programming (data transfer, combinational logic,

numeric comparison and arithmetic operations).

- Creation of simple state based systems by using the built-in sequencer feature.

Concepts covered here, and in previous parts of the series, will be pulled-together next month, with the final instalment focusing on the development of custom extensions to the software. A number of software solutions will be developed, making it straightforward to control the hardware devices discussed here, and many more besides.

#### Listings

As usual, all program listings for this series are available from the Library > Tutorials section of the *EPE* website ([www.epemag.com](http://www.epemag.com)). You'll also need the header files supplied with Part 1, which should be 'un-zipped' into a single folder, together with the sample files from each part of the series.

Make sure you have installed the freely available MPLAB IDE software, which will be needed to assemble the example programs. And of course, in order to actually test the programs, you will need a suitable PIC development board, fitted with one of the supported PIC microcontroller types, or simulation

software such as Proteus VSM from Labcenter Electronics.

#### Hardware design concepts

PIC microcontrollers are often used in 'embedded systems', where the PIC becomes a flexible and reprogrammable alternative to a hard-wired electronic circuit. Although sophisticated input/output circuitry is already provided in the commercial PLC, any interfacing hardware must be designed and built wherever a PIC microcontroller is deployed. Hardware design and software development are best thought of as two sides of the same coin, and must be considered together when any practical solution is being developed.

An appreciation of hardware interfacing techniques can also greatly add to the real world relevance of any ladder logic programs developed. It surely is more inspiring, for instance, to control a DC motor from a ladder logic output, rather than to simply turn an LED on and off – not least due to the many practical applications of motors.

Hardware interfacing concepts considered here will allow the PIC micro to be linked to a wide variety of hardware, including switches, LEDs, transistors, relays, motors, solenoids and optocouplers.



## Starting with the data sheet

The definitive source of information for the hardware designer is the appropriate PIC data sheet, which may be downloaded from the Microchip website ([www.microchip.com](http://www.microchip.com)) in PDF (Portable Document Format) format, and then viewed using the freely available Adobe Reader software.

PIC devices really do vary, particularly in their current handling capacity, so make sure that you carefully read the data sheet for the actual microcontroller being used, prior to designing any interfacing circuitry.

## Connecting input switches

PIC microcontrollers are based internally on CMOS technology, so any input circuits will draw negligible current, being effectively voltage controlled (input leakage currents of  $1\mu\text{A}$  or less, are defined in the data sheet using the  $I_{IL}$  parameter). Acceptable voltage ranges for high and low logic levels are specified in the data sheet using the  $V_{IH}$  and  $V_{IL}$  parameters respectively, typically using a calculation based on the positive supply voltage  $V_{DD}$ .

This can seem complex, but assuming a 5V power supply and standard input circuitry, a logic 0 will be recognised as a voltage in the range 0V to 0.75V ( $0.15 \times V_{DD}$ ), while a logic 1 will be any voltage in the range 2.05V to 5V ( $0.25 \times V_{DD} + 0.8\text{V}$ ).

This makes it relatively straightforward to supply input data by using switches, using nothing more complex

than a switch and a resistor for each port bit. This is illustrated by Fig.5.1.

(It is assumed here, and in following interfacing examples, that a simple ladder logic program is running, copying input port bits from Port A to the equivalent output port bits of Port B.)

Notice that the circuit shows three different switch interfacing methods, and several other circuit variations are possible. Switch SW1 provides a direct connection to logic 1 when closed, or a weak pull-down via resistor R1 when open. Switch SW2 and R2 provide the opposite polarity.

A further alternative is shown by switch SW3 and R3, where a weak pull-up or pull-down is applied. This latter circuit may be preferred for a general experimentation arrangement, particularly if there is any possibility of the port being configured as an output, since it avoids the possibility of an excessive output current.

Why use a 10k resistor? Well the precise value is not critical, but observe that the current flowing through the resistor of  $0.5\text{mA}$  (or  $500\mu\text{A}$ ) is considerably larger than the input port's leakage current of at most  $1\mu\text{A}$ , effectively overcoming any input port loading effects, and ensuring that input logic levels are correctly interpreted. The use of an appropriately sized pull-up/pull-down resistor also prevents the input port from acting as an antenna for stray electromagnetic interference, thus avoiding false triggering of input circuits.

Note: The supported PIC microcontrollers all have the capability to enable internal pull-up resistors connected to Port B. This option is disabled within the PLC software by default, but may be a customisation option in situations where Port B is configured as an input port (as in the PIC16F887 model).

While the circuit (Fig.5.1) is fine where input switches are directly linked to the PIC, it would not be adequate in cases where the user was allowed to make their own connections via input terminals. Higher voltages or incorrect polarities would be quite likely to occur, leading to the likelihood of damage to the microcontroller, or even the risk of electric shock to the user.

A more robust input circuit would be advisable in this case, incorporating some kind of electrical isolation of the low voltage and (potentially) high voltage sections. Optocoupler/optoisolator circuits are ideally suited to this purpose and these will be discussed shortly, following consideration of output devices.

## Interfacing outputs

According to the PIC data sheet, the maximum current capacity of a single output port is 25mA, both at logic 1 (current being 'sourced' or flowing out of the pin), and at logic 0 (current flowing into the pin or being 'sunk').

However, there will also be an overall maximum current limit, either for the output port or for all output ports combined – and this is quite device specific. Some examples are listed below:

- PIC16F627A/628A/648A – maximum current sunk/sourced by PORTA and PORTB (combined) = 200mA.
- PIC16F87-88 – maximum current sunk/sourced by PORTA or PORTB (separately) = 100mA.
- PIC16F887 – maximum current sunk/sourced by all ports combined = 90mA.

Design constraints also exist related to the maximum current sunk or sourced, plus the overall power dissipated by the entire device. For example, the PIC16F627A/628A/648A data sheet gives the following values:

- Maximum current out of  $V_{SS}$  pin (negative power supply pin) = 300mA.
- Maximum current into  $V_{DD}$  pin (positive power supply pin) = 250mA.

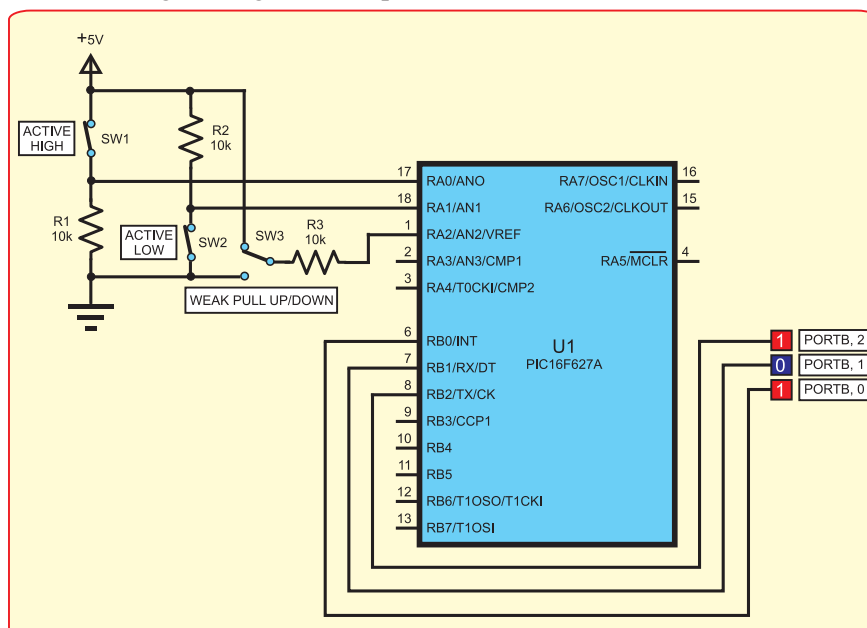


Fig.5.1. Methods of connecting input switches

- Total maximum power dissipation = 800mW (and the method of calculating this value is given in the data sheet).

A second consideration is the voltages involved, including both the supply voltage to the PIC itself, and also the actual worst case voltages likely to appear when a logic 1 or logic 0 is being outputted (stated as  $V_{OH}$  and  $V_{OL}$  respectively in the PIC data sheet). The minimum output voltage for a logic 1,  $V_{OH}$ , is defined as being  $V_{DD} - 0.7V$ , which for a 5V power supply, would be in the range 4.3V to 5V.

Similarly, the maximum output voltage for a logic 0,  $V_{OL}$ , is given as 0.6V, so a logic 0 output voltage will be in the range 0V to 0.6V. (These voltage levels are stated with output currents considerably less than the maximum of 25mA, so slightly worse figures may be found in practice.)

This gives us the necessary information to design output interface circuitry, noting that the PIC micro's powerful and symmetrical output drive circuitry provides us with great design flexibility ( $I_{max} = 25mA$ , both at logic 0 and also at logic 1).

## Driving LEDs

First, let us consider the interfacing options for directly connected LEDs, as shown in Fig.5.2.

As can be seen, the symmetrical drive capability allows us to connect the LED either way round, with D1 being illuminated by a logic 0 output, and D2 by a logic 1.

A typical LED forward voltage of 2V and a maximum current of 10mA is

assumed here, but forward voltages may vary depending on the colour of the LED, while the maximum current capacity will be related to the brightness of the LED and its power rating. Both voltage and current values should be obtained from the appropriate catalogue or data sheet and then used to calculate the value of the current-limiting resistor (R4 and R5).

The preferred value of  $270\Omega$  shown here will give a current of approximately 10mA, assuming that a voltage of 2.7V appears across the resistor terminals—or slightly less in the event of worst case output voltages of  $V_{OH}$  and  $V_{OL}$ .

## Controlling larger currents and higher voltages

Where higher voltages and/or higher currents must be controlled, then

a transistor output circuit is a good choice. Transistors come in many forms, including bipolar and field effect types, and high gain Darlington-pair composite devices are also available. To keep things simple, a circuit based on an NPN bipolar transistor will be considered here, as shown in Fig.5.3.

The NPN bipolar transistor is a three-terminal device, which is used here as a current controlled switch, with a relatively small current flowing into the base terminal (B) controlling a larger current flowing into the collector terminal (C). Essentially, either current is allowed to flow into the base terminal and the transistor turns on (and hence the lamp lights), or no current flows into the base, and the lamp and transistor are both off.

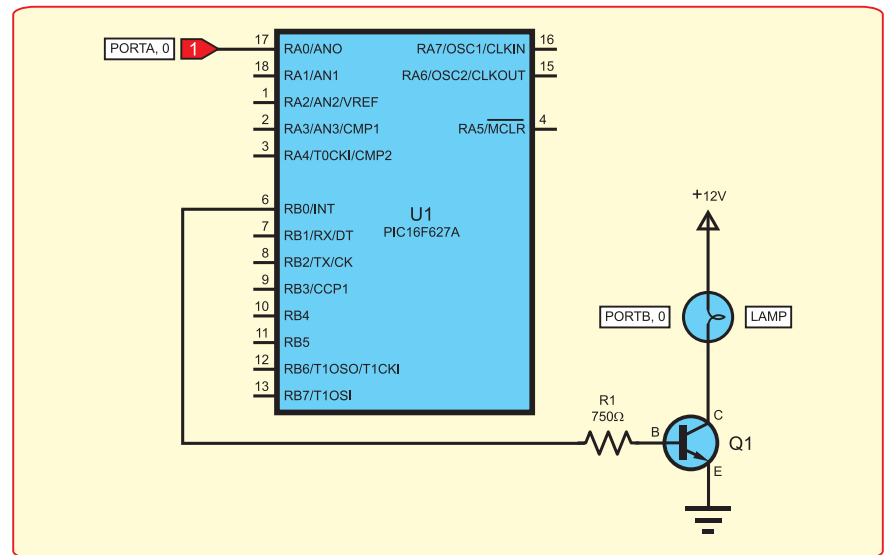


Fig.5.3. Controlling a 12V lamp by using a transistor switching circuit

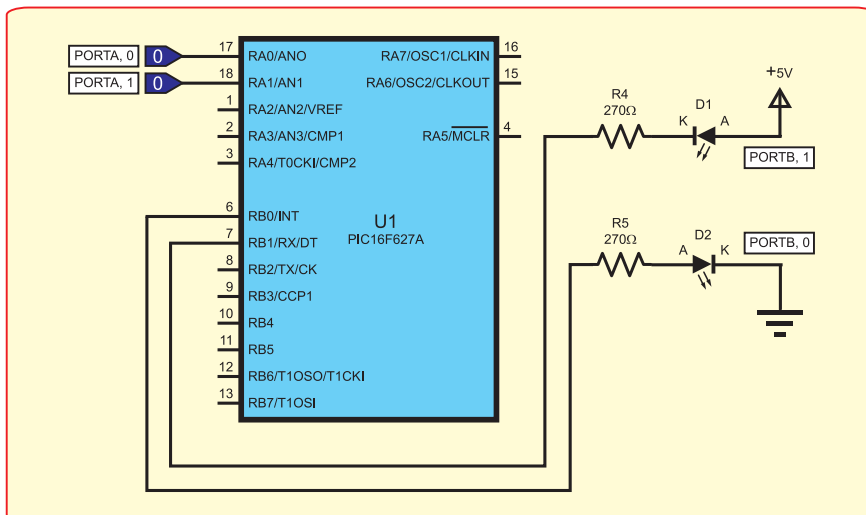



Fig.5.2. LED interfacing options

The transistor is enabled in the circuit of Fig.5.3 by outputting a logic 1 to bit 0 of Port B (pin 6), which in turn supplies a current of approximately 5mA to the base terminal of the transistor, via current limiting resistor R1. This small current is multiplied by the current gain of the transistor (referred to as  $h_{FE}$  or  $\beta$  in data sheets and equal to  $I_C/I_B$ ) to become a much larger collector current.

When the transistor is switched on, almost all of the 12V supply appears across the lamp terminals, with only 0.1V to 0.2V across the collector-emitter (E) junction of the transistor (so  $V_{CE} = 0.1V$  to  $0.2V$ , at which point the transistor is said to be 'saturated').

Strange as it may seem, this circuit is best designed by working



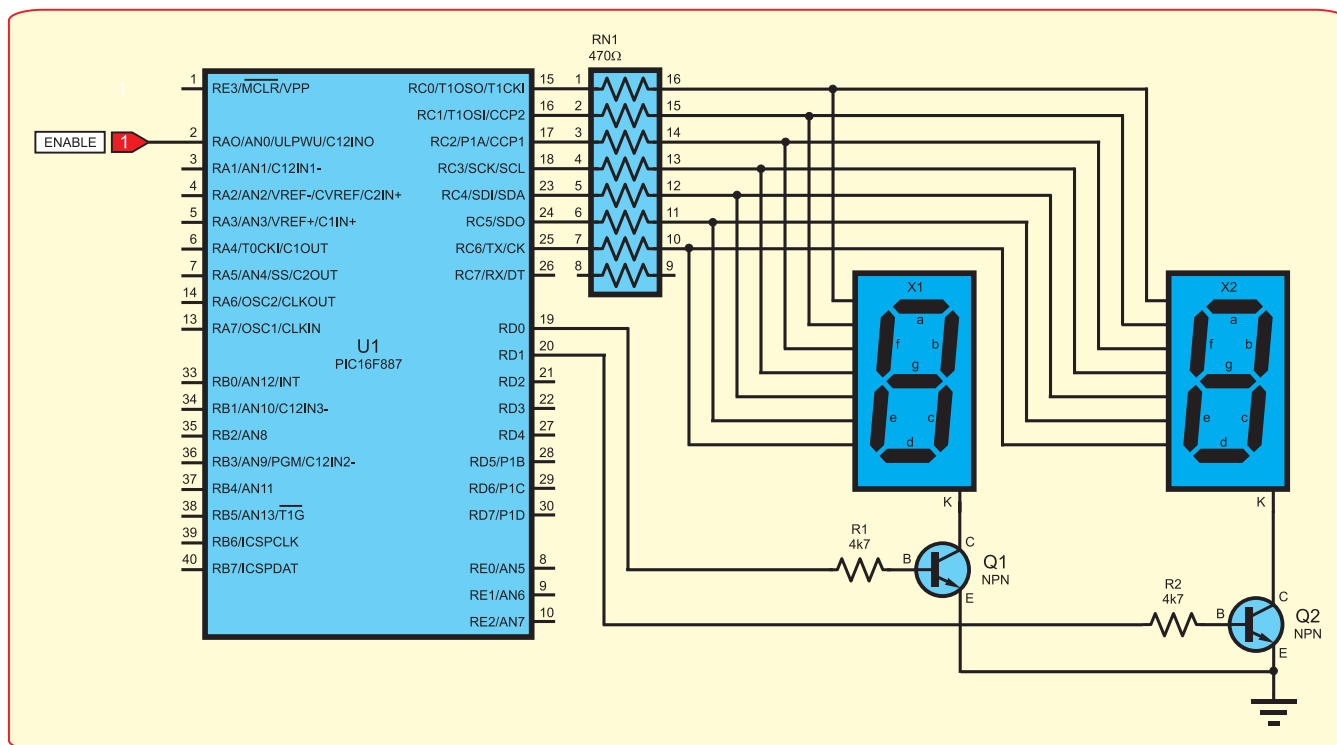

**Fig.5.4. A simple multiplexed LED display**

back from the output to the input, beginning with the lamp. To take an example, assuming the lamp is rated at 12V and has a resistance of 24Ω. A simple calculation shows that the lamp current will be 0.5A, so our first design conclusion is that we will need a transistor with a  $V_{CE(\text{man})}$  rating greater than 12V and  $I_C$  in excess of 0.5A, which is quite straightforward.

Next, the minimum  $h_{FE}$  is identified from the transistor data sheet and this is used to calculate the required base current ( $I_{B(max)} = I_C/h_{FE(min)}$ ). So for example, if  $h_{FE(min)} = 100$  and  $I_C = 500\text{mA}$ , then the required base current will be  $5\text{mA}$ . (Recall that we need to keep this base current under  $25\text{mA}$  in order to comply with the PIC's maximum current rating, so a value of  $5\text{mA}$  flowing out of Port B bit 0 will be fine.)

The base-emitter junction of a conducting transistor is effectively a silicon diode, so a voltage of approximately 0.7V appears across the base-emitter terminals when the transistor is switched on. Given that the required base current is 5mA, a simple calculation provides us with the value of the current-limiting base resistor:

$$R_1 = V_{R1}/I_B$$

$$= (V_{OH} - V_{BE})/I_B$$

$\approx 750\Omega$  (the nearest preferred value in the E24 / 5% resistor series)

## Further transistor switching applications

The previous transistor switching circuit is clearly useful in its own right, allowing larger current devices to be controlled, and also devices which have higher operating voltages. Equally importantly, it may be easily adapted to control devices such as 7-segment displays, or inductive loads such as relays, solenoids or even motors. As a first example, Fig.5.4 shows a pair of transistors used to alternately enable the digits of a multiplexed 7-segment common cathode display.

Each of the individual segments within the 7-segment display is a separate LED with its positive anode (A) connected via a current-limiting resistor to an output port bit. The negative cathodes (K) are internally linked and brought out to a terminal at the lower end of the 7-segment display (hence this is referred to as a ‘common cathode’ 7-segment display).

In a single digit display, the cathode connection may be simply grounded, but in a multiple-digit display (as shown in Fig.5.4), each display is enabled in a rapidly repeating sequence, giving the illusion that all digits are simultaneously illuminated. This ‘time division multiplexed’ arrangement is used in order to minimise the number of output ports bits required

by multiple-digit displays. (Calculation of the value of the current-limiting resistors is similar to that already seen for a single light emitting diode, but the brightness is normally increased, since each digit is only illuminated for a fraction of the time.)


We will revisit this application next month, when custom macros will be developed to drive single- and multiple-digit 7-segment displays.

## Inductive loads

A transistor may also be used to energise the coil of a relay, as illustrated by Fig.5.5.

In this example, the relay is shown energising a 24V lamp, but a more flexible arrangement would be to bring out the relay contacts to external screw terminals, allowing users to make their own connections, as appropriate. The addition of a normally reverse biased diode across the relay coil enables the energy stored in the magnetic field of the coil to harmlessly dissipate when it is de-energised, 'quenching' the momentary high voltage spike which would otherwise occur.

The same basic circuit may be used to energise other types of inductive load, such as a DC motors, stepper motors, or even solenoids – with electronic door locks and pneumatic

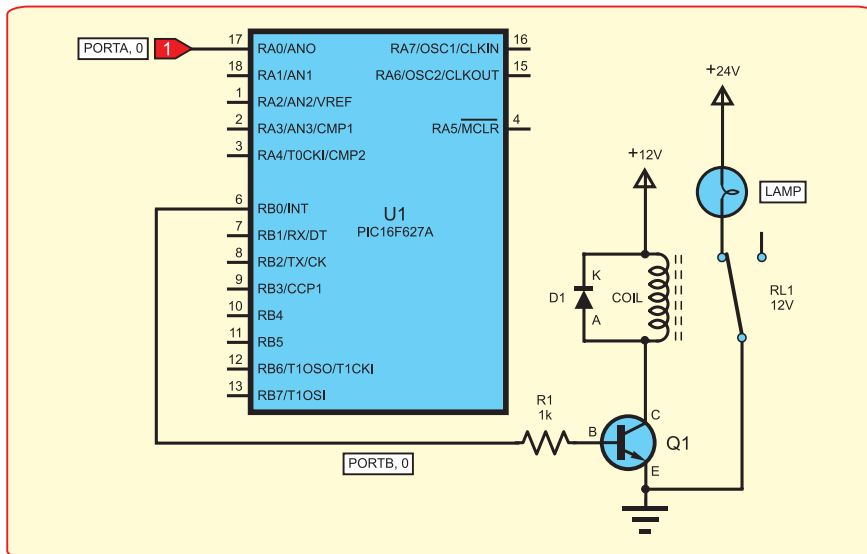

**Fig.5.5. Controlling a relay using a transistor switching circuit**

valves being just two applications of solenoids.

Although not considered here, it is also possible to use transistor circuits to provide bidirectional control of motors, or to energise the coils of a bipolar stepper motor with positive or negative polarity. Such a circuit would use two output port bits per controlled device, linked to a 'H-bridge' transistor circuit, with a small DC motor requiring one bridge (two port bits per motor) and a two coil stepper motor being linked to four output port bits.

Custom software routines to control stepper motors will be developed next month, in addition to the 7-segment displays already discussed.

## Isolating high and low voltages

The relay output circuit considered previously has the advantage of providing a degree of electrical isolation between the low voltage control circuit, and the potentially higher voltages connected to the switch contacts of the relay. This same safety principle may also be applied to input circuitry, but this time based on optocoupler technology, as illustrated by Fig.5.6.


In this example, a 24V DC input is connected via a switch and current-limiting resistor (SW1 and R1 respectively) to the LED inside the optocoupler. Closing the switch causes the optocoupler LED to light, thus enabling the photo-transistor connected to the output.

The transistor within the optocoupler is wired as an emitter

follower, which causes the emitter to be pulled up to almost 5V each time the internal LED is illuminated. This also illuminates the external indicator LED1 via current-limiting resistor R2, at the same time supplying a logic 1 input to the PIC microcontroller at pin 17 (RA0).

This type of input circuitry has two advantages. First, it allows connection of higher input voltages, and second it provides electrical isolation of potentially dangerous input voltages from the relatively expensive processor circuitry.

Bear in mind that the input protection circuitry of an actual PLC is likely to be more complex than that shown here, offering over-voltage and reverse polarity protection.

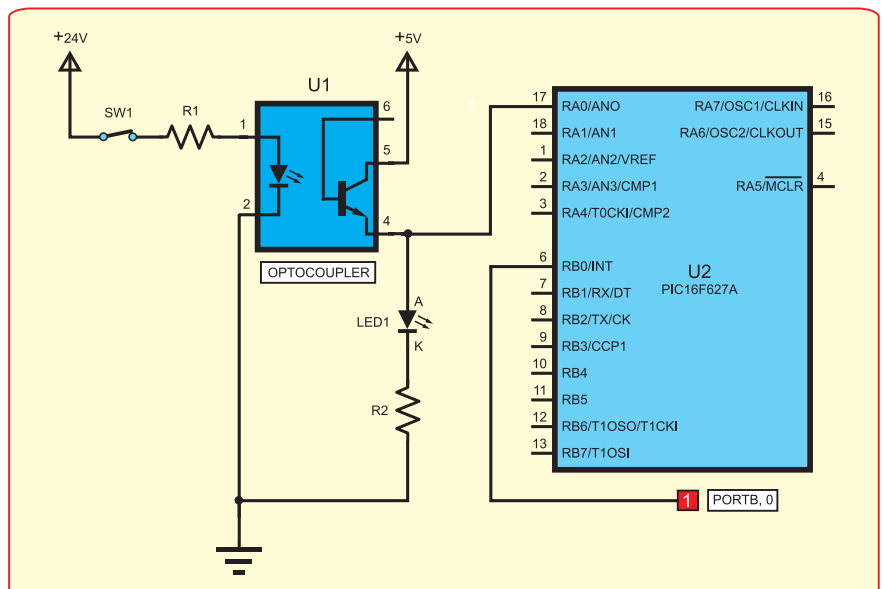

**Fig.5.6. Providing input isolation by using an optocoupler**

## Proteus VSM simulation tips

Observant readers may have noticed that the circuits of Figs.5.1 to 5.6 are based on screenshots produced by Proteus VSM software from Labcenter Electronics. (The annotations for the transistors, diodes and relay coil have been added.) This neatly demonstrates the feasibility of mixed hardware and software simulation.

If you have access to this powerful software application, then the following simulation and debugging tips may prove useful:

1. For simple application and viewing of logic levels, the 'logicstate' and 'logicprobe' components allow logic 0/logic 1 inputs to be applied and displayed respectively. A momentary action 'logictoggle' input device is also available, and logic probes are found in two different sizes.

2. The default oscillator frequency of 1MHz should be changed to 4MHz on each inserted microcontroller, thus ensuring that time-critical programs operate at the desired speed.

3. Proteus VSM provides a variety of 'animated' components, which may be used to give a visual indication of circuit operation during simulation. Animated devices include switches, LEDs, 7-segment displays, lamps, relays, DC motors and stepper motors.

4. The 'virtual instruments' feature emulates common measuring instruments such as the ammeter, voltmeter, signal generator and oscilloscope.



(Refer back to Part 2 Fig.2.2 to see the 'digital oscilloscope' in action.)

You also have the ability to pause the simulation and click on components in order to view instantaneous parameters, including voltage, current and power dissipation – which can often be simpler than placement of numerous measuring instruments. Dedicated microelectronics instruments are also available, including a multiple channel pattern generator and a logic analyser.

5. Proteus provides a built-in source code editor, plus a number of built-in assemblers, including MPASMWIN. Use of this assembler is an alternative to the MPLAB IDE, which has been used throughout this series. (Note that the MPASM assembler also supplied with Proteus does not recognise PIC16F887 source code files at the time of writing, although the MPASMWIN version seems to have no such problem.)

6. A variety of software debugging features are provided through a powerful integrated development environment (IDE). The 'watch window' is particularly useful for debugging ladder logic programs, allowing the content of selected internal registers to be viewed during run time. (Refer back to Part 3, Fig.3.3 to see this feature used when debugging a low-speed timer application.) Other IDE features include single step, breakpoints, source code view, plus register and memory view windows.

In general, I have found simulation of animated electronic devices to be trouble free, with a couple of minor exceptions. First, the connection of animated DC motors and stepper motors can give 'timestep too small' errors in mixed simulations. If you encounter this error, then one work-around might be to replace the motor with an animated lamp of the same rating, in order to demonstrate circuit operation.

Second, you may observe transient oscillation of outputs such as relay contacts in more complex simulations. This seems to relate to the method used by the PIC microcontroller to update an output port, in which the output port is first read (ie inputted), then updated and finally re-outputted. You can avoid this unwanted feedback effect by temporarily placing 'buffer' components between appropriate output ports and any external circuitry.

At this stage, you should now have a good appreciation of the hardware found in a typical PLC, and you should be able to design simple low voltage PIC interface circuitry for use in embedded control applications. The next section looks at the byte processing capabilities of the PLC software, which will be used to build a digital comparator, and also an adder/subtractor circuit.

## Working with bits and bytes

Ladder logic excels at the manipulation of individual bits – for example reading inputs, performing simple combinational logic operations, and outputting the results. Certain other commands already considered may be regarded as either bit-oriented or byte-oriented, depending on the application.

This includes counters, timers and shift registers, all of which make use of a byte-sized 'working register', which may be optionally used by the programmer. Recall that commands have also been introduced which can load a byte-sized value into a register, or copy a byte from one register to another (the 'puti' and 'putr' commands respectively, first introduced in Part 3).

Use of byte-oriented commands can greatly simplify the writing of certain programs, and a further advantage is their efficient coding and high speed of execution. The only potential downside, for those new to microelectronics at least, is the greater conceptual difficulty when working with byte values, compared with individual bits. This may include the need to work with a variety of numbering systems, such as binary, octal, hexadecimal and decimal, in addition to the representation of signed and unsigned numeric values (2's complement arithmetic for example.)

The PLC software's dedicated byte processing capabilities fall into the following categories:

- Byte data transfer – using the 'puti' and 'putr' commands, as discussed above. (Please refer back to Part 3,

Table 3.1, Listing 3.6, and associated text for more details.)

- Byte logical commands – performing combinational logic operations on each bit of a register simultaneously.
- Byte comparison – comparing byte values using operators such as 'less than', 'equal to', 'not equal to', 'greater than', and their combinations.
- Byte arithmetic – adding and subtracting byte values (with subtraction using 2's complement arithmetic).

## Byte logical commands

Byte logical commands perform combinational logic operations such as AND, OR, and XOR on each bit of a source register, combining the source with a 'mask' to produce a result byte. Careful choice of logical operation and mask byte allows a variety of operations to be performed, including setting, clearing, inverting or copying selected bits.

Each command offers a matched pair of operations, which is selected by the value of the mask bit:

- AND with 1 to copy the source bit unaltered. AND with 0 to clear the output bit to zero
- OR with 1 to set the output bit to 1. OR with 0 to copy the source bit unaltered
- XOR with 1 to invert the source bit. XOR with 0 to copy the source bit unaltered.


These possibilities are illustrated graphically by the example of Fig. 5.7, in which a binary source byte '1010 1010' at the centre of the figure is combined with a mask byte of '1111 0000' to produce three different result bytes by using AND, OR and XOR operations at the left, right and bottom respectively.

The PLC software offers two different versions of each command, as shown in Table 5.1.

As usual, command names are supplied in lower case and register names are upper case. Notice that command names ending with 'r' (register)

| Logical Operation | Syntax and Addressing Mode        |                                  |
|-------------------|-----------------------------------|----------------------------------|
|                   | (Register, Immediate) -> Register | (Register, Register) -> Register |
| AND               | andi SRC_REG, BYTE, DST_REG       | andr SRC_REG1, SRC_REG2, DST_REG |
| OR                | ori SRC_REG, BYTE, DST_REG        | orr SRC_REG1, SRC_REG2, DST_REG  |
| XOR               | xori SRC_REG, BYTE, DST_REG       | xorr SRC_REG1, SRC_REG2, DST_REG |

Table 5.1. Byte-oriented logic commands

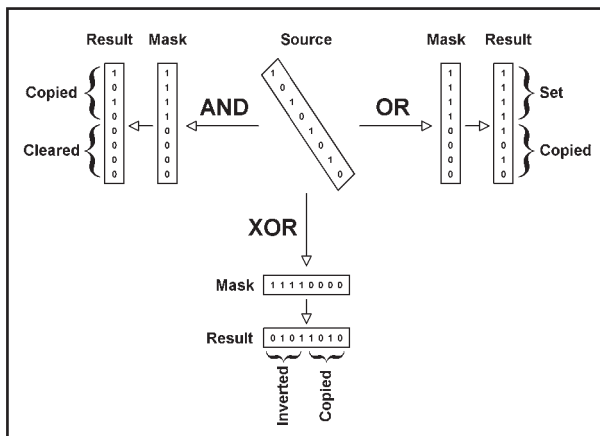

**Fig.5.7. Bit masking with byte logical commands**

combine a pair of registers, while an 'i' (immediate) combines an immediate value with a register. In each case, the result is written to a specified destination register.

A practical application will be given in the next section when bit masking and byte comparison commands are combined to make a digital comparator.

## Byte comparison commands

As their title suggests, byte comparison commands perform numerical comparisons between two values, producing a logic 1 value if the comparison is true. In fact, you may recall that we briefly discussed byte comparison commands in Part 3, making use of the 'eqi' (equal immediate) command to test an immediate value and a register, as part of the light chaser program of Listing 3.9.

The full range of byte comparison commands and options are given in Table 5.2.

As an example, we will design a digital comparator which will compare two 4-bit numbers, referred to as 'A' and 'B',

producing three outputs, 'A > B', 'A < B' and 'A = B'. A possible program is given in Listing 5.1, written for the PIC16F887 microcontroller.

The program is relatively straightforward, beginning by masking off the upper 4 bits of Ports A and B, storing the results in auxiliary registers AUX0 and AUX1. These intermediate values are then compared, with the three possible comparator results being

written in order to bits 0–2 of Port D.

## Byte arithmetic instructions

The PLC software provides the ability to perform addition and subtraction of byte values, with available command options shown in Table 5.3.

This is likely to be one of the lesser used features, and also one of the more

conceptually difficult, due to its use of 2's complement arithmetic. However, potential applications might include control-oriented systems in which a measured parameter such as temperature, pressure, or speed of rotation is compared with a set point, with a subtraction command producing a deviation value. This feature might, for example, form part of a PID (proportional, integral, derivative) controller.

The example of Listing 5.2 performs addition and subtraction of two 4-bit numbers, outputting the results to two 8-bit registers.

Unfortunately, a full discussion of 2's complement arithmetic is beyond the scope of this series, but note that the program of Listing 5.2 will display any negative subtraction results in 2's complement form on Port D. The following information may be useful when interpreting displayed results:

- In an 8-bit representation, positive 2's complement numbers are allowed

```
include "16F887.PLC" ; Defines PLC instructions

andi   PORTA, b'00001111', AUX0 ; Mask upper 4 bits of Port A,
                                   ; placing result in AUX0 (number 'A')
andi   PORTB, b'00001111', AUX1 ; Mask upper 4 bits of Port B,
                                   ; placing result in AUX1 (number 'B')

eql     AUX0, AUX1                ; Test if A = B
out     PORTD, 0                  ; outputting result to bit 0 of Port D

gtr     AUX0, AUX1                ; Test if A > B
out     PORTD, 1                  ; outputting result to bit 1 of Port D

ltr     AUX0, AUX1                ; Test if A < B
out     PORTD, 2                  ; outputting result to bit 2 of Port D

endp                               ; Marks end of PLC program
```

**Listing 5.1. A 4-bit comparator program (Lst5\_1.asm)**

| Arithmetic Operation | Syntax and Addressing Mode        |                                  |
|----------------------|-----------------------------------|----------------------------------|
|                      | (Register, Immediate) -> Register | (Register, Register) -> Register |
| Add                  | addi SRC_REG, BYTE, DST_REG       | addr SRC_REG1, SRC_REG2, DST_REG |
| Subtract             | subi SRC_REG, BYTE, DST_REG       | subr SRC_REG1, SRC_REG2, DST_REG |

**Table 5.3. Byte arithmetic commands**

| Compare Operation     | Syntax and Addressing Mode        |                                  |
|-----------------------|-----------------------------------|----------------------------------|
|                       | (Register, Immediate) -> Register | (Register, Register) -> Register |
| Less than             | lti SRC_REG, BYTE, DST_REG        | ltr SRC_REG1, SRC_REG2, DST_REG  |
| Less than or equal    | ltei SRC_REG, BYTE, DST_REG       | lter SRC_REG1, SRC_REG2, DST_REG |
| Equal                 | eqi SRC_REG, BYTE, DST_REG        | eql SRC_REG1, SRC_REG2, DST_REG  |
| Not equal             | nei SRC_REG, BYTE, DST_REG        | ner SRC_REG1, SRC_REG2, DST_REG  |
| Greater than          | gti SRC_REG, BYTE, DST_REG        | gtr SRC_REG1, SRC_REG2, DST_REG  |
| Greater than or equal | gtei SRC_REG, BYTE, DST_REG       | gter SRC_REG1, SRC_REG2, DST_REG |

**Table 5.2. Byte comparison commands**

to be in the decimal range 0 to +127, and negative decimal numbers are between -1 and -128. The most significant bit of the subtracted result indicates the sign, with zero indicating a positive result and one showing a negative 2's complement value.

- Positive binary numbers are converted to 2's complement 'negative' form by first inverting each bit, and then adding 1 to the



```
include "16F887.PLC"           ; Defines PLC instructions

andi    PORTA, b'00001111', AUX0 ; Mask upper 4 bits of Port A,
                                   ; placing result in AUX0 (number 'A')
andi    PORTB, b'00001111', AUX1 ; Mask upper 4 bits of Port B,
                                   ; placing result in AUX1 (number 'B')

addr     AUX0, AUX1, PORTC        ; Send result A + B to Port C
subr     AUX0, AUX1, PORTD        ; Send result A - B to Port D

endp                                ; Marks end of PLC program
```

**Listing 5.2. Addition and subtraction of two 4-bit numbers (Lst5\_2.asm)**

```
include "16F627.PLC"           ; Defines PLC instructions and sequencer data
                                   ; held in EEPROM - see org H'2100' section

ld       PORTA, 0                ; Enable input - single-shot sequence

seq      d'27', OSCL, 0          ; Sequencer with 27 steps (0-26)
                                   ; 8 Hz clock input (T = 131.1 ms)

putr     SEQ, PORTB              ; Copy sequencer value to Port B

endp                                ; Marks end of PLC program
```

**Listing 5.3. Producing a single-shot sequence with default data (Lst5\_3.asm)**

```
include "16F627.PLC"           ; Defines PLC instructions and sequencer data
                                   ; held in EEPROM - see org H'2100' section

ld_not   SEQFIN, 0               ; Enable input - continuously running

seq      d'27', OSCL, 0          ; Sequencer with 27 steps (0-26)
                                   ; 8 Hz clock input (T = 131.1 ms)

putr     SEQ, PORTB              ; Copy sequencer value to Port B

endp                                ; Marks end of PLC program
```

**Listing 5.4. Producing a repeating display (Lst5\_4.asm)**

```
                                   ; ** This section initialises EEPROM data

org      H'2100'                 ; Put EEPROM data here for use by the
                                   ; seq (sequencer) command
                                   ; Up to 256 bytes are available with the
                                   ; PIC16F88.
                                   ; Traffic light data is shown below:

de       B'00000100'             ; Step 0 - Red
de       B'00000110'             ; Step 1 - Red + Amber
de       B'00000001'             ; Step 2 - Green (1 of 5)
de       B'00000001'             ; Step 3 - Green (2 of 5)
de       B'00000001'             ; Step 4 - Green (3 of 5)
de       B'00000001'             ; Step 5 - Green (4 of 5)
de       B'00000001'             ; Step 6 - Green (5 of 5)
de       B'00000010'             ; Step 7 - Amber
```

**Listing 5.5. Custom traffic light sequencer data**

```
include "16F88_L.PLC"           ; Defines PLC instructions and sequencer data
                                   ; held in EEPROM - see 'ORG 2100H' section

ld_not   SEQFIN, 0                ; Enable continuous operation
and       PORTA, 0                ; with a separate enable input

seq      d'8', OSCL, 3            ; Sequencer with 8 steps (0-7)
                                   ; 1 Hz clock input

putr     SEQ, PORTB              ; Copy sequencer value to Port B

endp                                ; Marks end of PLC program
```

**Listing 5.6. The traffic light program (V1.01\_Files/Lst5\_6.asm)**

result. The inverse process of subtracting 1 and then inverting each bit converts a negative number back to positive form.

The next and final section introduces the sequencer feature, which extends the concept of byte processing to incorporate simple state-based systems.

## Sequencer-based systems

The built-in sequencer facility makes it easy to create complex animated sequences, with user-defined data in EEPROM memory being sent at regular intervals to the chosen destination register. Single-shot or repeating sequences may be produced with up to 255 steps, depending on the capacity of the EEPROM memory within the chosen microcontroller. Typical applications of the sequencer include toys, festive decorations, shop signs, running-light displays, and many more besides.

(Note that the 16F627A and 16F628A microcontrollers have 128 bytes of built-in EEPROM, while the 16F648, 16F88 and 16F887 offer 256 bytes. Please refer back to Part 1, Table 1.1 for a detailed list of microcontroller features.)

Writing sequencer-based programs is a little different to that seen so far, since the user's program is effectively merged with sequencer data contained within the PLC header-file during assembly. The first step is normally to create a separate folder to hold both the custom header file and the source code file for the sequencer project. Next, the header file is edited so that it contains the required sequencer data. Finally, a suitable ladder logic program is written and assembled in the normal way.

For the sake of simplicity, sample sequencer data

for a running light display has already been placed into the header files supplied with Part 1 of the series. The only remaining step is to write a short sequencer program, with a simple example shown in Listing 5.3.

This program produces a non repeating output sequence on Port B, which is triggered by an active-high enable input connected to bit 0 of Port A. This enable input must be held continuously high during the sequence, causing the sequencer to be reset when it goes low.

The sequencer itself is defined using the 'seq' command, which in this case has 27 steps in the sequence (to match the data defined in the header file supplied with Part 1 of the series). Output data from the current step in the sequence is held in the SEQ register, which is displayed on output port B by the 'putr' command.

It is quite simple to adapt this program in order to create a continuously running sequence, as shown in Listing 5.4. In this case, the 'sequencer finished' status bit, 'SEQFIN, 0' is first inverted and then used as the enable input to the sequencer. At first, the sequencer is enabled (because it is not yet finished), but the status bit becomes set on completion. This resets the sequencer, causing the sequencer to restart.

The sequencer feature is best suited to applications not requiring any great decision making capacity, where a fixed output sequence is to be generated at regular intervals. If a more flexible system is required then a 'finite state machine' may be a better choice, and this type of system will be explored as a customisation topic in the final part of the series.

## Creating a custom sequence

Having mastered the sequencer programming side of things, the next step is to create our own custom sequencer data. A simple traffic light display will be used as an example to illustrate the process involved.

If you have not already done so, you should download the file containing zipped program listings for Part 5 of the series; as usual, extracting these to the same folder used for other parts. You should notice that a sub-folder called 'V1.0.1\_Files' has been created. This folder contains an updated set of header files, which have been modified to include the traffic light sequencer data, with the relevant sequencer content for the PIC16F88 microcon-

troller being shown in Listing 5.5.

Notice that EEPROM data is specified as a series of data bytes, starting at hexadecimal memory location 2100. The actual sequencer data consists of eight steps, with the red, amber and green traffic lights assumed to be connected to the rightmost sequencer output bits.

Assuming that each step lasts for one second, then we can see that the green output will be active for five seconds, with all other states lasting one second each. The sequencer will operate in continuous mode, automatically returning to state 0 after the final state, thus giving an amber to red transition.

A suitable traffic light program is given in Listing 5.6, this time written for the PIC16F88 with low voltage programming enabled.

Notice that continuous operation has been enabled, and an additional enable input has been added, linked to bit 0 of Port A. (The updated software supplied in Version 1.0.1 turns-off the sequencer output when it is disabled, and makes other minor corrections, as detailed in the release notes.)

Readers with Proteus VSM simulation software may optionally connect a 'traffic lights' component to the output port, as shown in Fig.5.8. For others, the program may easily be adapted to run on supported hardware platforms, in which case the colour of the traffic light LEDs may need to be imagined!

An interesting exercise for the reader would be to extend the above system to control a pair of traffic lights at a crossroads (north-south and east-west operation). You may also like to think of other applications of sequencers, including electronic toys and decorations. Development of new systems and applications can be both interesting and creative, and will also give you

plenty of opportunities to practise your hardware design skills.

## Summary

We have covered a lot of ground this month, ranging from hardware design and the use of computer-based simulation, to byte-oriented programming, and even simple sequencer-based systems. Several of these topics will be expanded in the next and final part of the series, which will focus on customisation of the software.

## Next Month

In the final part of the series we will add a number of custom extensions to the PLC software, creating an updated version in the process. This will greatly extend the range of potential applications of the software. Topics considered will include:

- Configuring device options (port directions, watchdog timer, option and configuration register settings).
- Conditional subroutines – executing a block of code if a condition is true.
- Using lookup tables for code conversion – converting binary codes to and from other formats (a technique with a surprisingly large range of potential applications).
- Finite state machine – creation of powerful and flexible state-based systems.

These extensions will enable us to control devices, including 7-segment displays, DC motors and stepper motors, with the possibility of digital position measurement using Gray code.

We will also revisit the traffic light application one last time, demonstrating that a finite state machine approach offers increased flexibility compared to the sequencer-based method considered above.

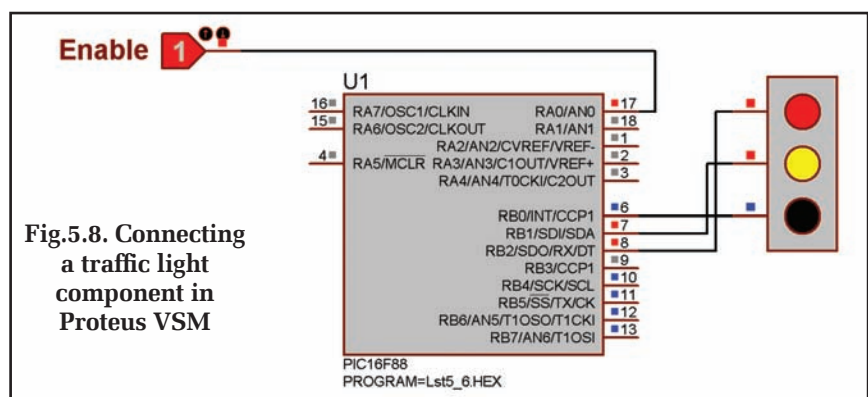


Fig.5.8. Connecting a traffic light component in Proteus VSM



## Why Do They Do That?

**I**N *Circuit Surgery* we usually try to answer 'how do I do that?' type questions, but this month, it is more of a case of 'why do they do that?' Where 'they' are the designers of the ICs we use, and the 'why' relates to the use of low supply voltages for modern electronics.

The choice of this topic was prompted by the following question posted by **Thomas Scarborough** on the *EPE Chat Zone* ([chatzones.co.uk](http://chatzones.co.uk)).

*My experience of electronics tells me that it is awkward to try to run anything off less than about three volts: CMOS, discrete, and so on. However, take a digital recorder/player I recently bought: 1.2 volts. Among other things, it has an orange LED! How do these things ever work?*

A number of replies on the forum suggested the use of voltage step-up ICs, with *epithumia* citing the MAX1947 as an example. This is how LEDs and other parts of systems which have to have higher voltages to operate are powered when the battery voltage is below their working voltage. However, it is not the whole story. Many readers will be aware that the supply voltage (core voltage) of microprocessors, such as Intel's Core-2 chips, is typically in the range of about 0.85V to 1.4V. So, it is evident that digital circuits can work at these low voltages. In fact, they *have* to run at these low voltages, something we will return to shortly.

### Stepping-up

If a step-up chip is used, then at least one part of the system must work at the lower voltage to run the step-up process. The approach taken by the MAX1947 is quite interesting in this respect. The datasheet (see [maxim-ic.com](http://maxim-ic.com)) reveals that it uses a 'bootstrap' approach. It contains a start-up oscillator, which can run on the minimum specified input voltage for the device, which is about 0.7 to 0.8V.

This oscillator runs a switching conversion which brings the output voltage to around 1.6V. Once this output level is achieved, it is used to power the remainder of the IC's internal circuitry – the main DC-to-DC converter, which boosts the output voltage to the required value.

It is common for modern portable personal electronic gadgets, such as the music player Thomas mentions, to run off low-voltage battery supplies. This is convenient because a single small battery

can be used, but often requires other voltages to be generated. LEDs require higher voltages because the physics of their operation determines the 'forward voltage' required for them to emit light. For an orange LED this is typically about 2.2V, for blue and white LEDs it is higher, usually at least 3.3V.

Many digital ICs require low voltages, often in the 1V to 3.3V range, because higher voltages would destroy the transistors used in their circuits, and because lower power consumption (and hence battery life) is a critical requirement in such gadgets – using lower supply voltages helps achieve lower power consumption. The fact that different parts of such products might require different voltages is reflected in the vast number of DC-to-DC conversion and power management ICs aimed at designers in this market.

### In perspective

The perspective stated by Thomas, 'that it is difficult to get anything to work below 3V' is one based on designing with discrete components, using traditional circuit techniques. A bipolar transistor requires about 0.7V to switch on, so a 1.2V supply does not give you much headroom. However, the IC designers working on modern digital chips will be using circuits based on MOSFET transistors (CMOS) with threshold voltages typically below 0.5V, maybe around 0.3V or even lower.

The basic circuit structure of logic gates remains the same at these low supply voltages, but analogue circuit designs may be radically different. Many new approaches to low-voltage analogue design have been published over the last twenty years, but often these designs are based on silicon (not discrete components) and some approaches employ special device

structures, such as multi-input floating gate MOSFETs.

It is developments in digital, rather than analogue circuits, which have caused the move to low supply voltages. Digital circuitry dominates modern products such as MP3 music players and mobile phones, and analogue design has adapted to its requirements. The low power supply voltages we have today are a direct consequence of the dramatic increase in performance of electronic products over the last few decades. This exponential growth in electronic functionality was predicted by Gordon Moore in 1965; known as Moore's law, it states that the number of transistors on an integrated circuit would double approximately every 18 months to two years.

For example, Intel's first 8-bit processor, the 8008, was produced in 1972 and contained 3,500 transistors. The recent Intel Core i7 64-bit processor, launched in 2009, has about 780 million transistors. We need between 17 and 18 'doublings' to produce this two-hundred-thousand-fold increase over 37 years (18.5 two-year periods), so this is in line with Moore's Law.

Moore's Law has held for over forty years, although it may not continue much longer due to the fact that transistors are becoming so small that atomic and quantum effects may prevent much further progress. However, other 'fundamental' limits have been predicted before and passed.

### Scaling theory

Behind the empirical data of Moore's Law lies *scaling theory*, this is what has driven the improvement in circuit performance. The basic idea behind scaling is that by making transistors smaller you get faster circuits, which take up less space on the silicon, or of course you can put more functions on a chip the same size.

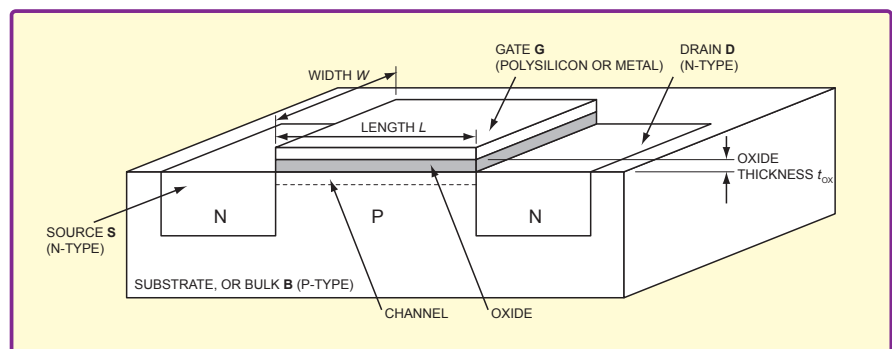


Fig.1. Structure of an NMOS transistor

Doing this is not trivial, because you have to develop new fabrication technology which is capable of reliably manufacturing large quantities of chips using the smaller transistors. However, scaling theory does allow you to predict how the next generation of technology will behave and what you can achieve with it.

Scaling theory was first developed by Robert Dennard and his colleagues at IBM in 1972 and published in a paper in 1974 in the *IEEE Journal of Solid-State Circuits*. Dennard is also notable as the inventor of Dynamic Read Only Memory (DRAM) in 1967 (patented in 1968).

Fig.1 shows a simplified schematic of an NMOS transistor, showing key physical dimensions: the channel length,  $L$ , the channel width  $W$ , and the gate oxide thickness,  $t_{ox}$ . In scaling a technology, these physical dimensions are reduced by multiplying by a factor  $k$ . So the minimum transistor channel length changes from  $L_{min}$  to  $kL_{min}$ , and similarly the oxide thickness is reduced to  $kt_{ox}$ . Other transistor parameters are scaled in the same way.

The usual value for  $k$  is 0.7 (ideally  $1/\sqrt{2}$ ), that is physical sizes are scaled down by 30% to go to the next generation of circuits. Capacitance in transistors is proportional to their area divided by the oxide thickness,  $WL/t_{ox}$  (capacitance increases if you increase the size of the plates or bring them closer together). This means capacitance scales by  $(0.7 \times 0.7)/0.7$  which is 0.7. Circuit delays scale down by 0.7, which means clock frequency can increase by a factor of 1.43 (ie  $1/0.7$ ).

The area of a chip is proportional to the area of all the transistors, each of which has area  $W \times L$ , which scales by  $0.7 \times 0.7$ , which is about 0.5. So the circuitry takes up half the space on the new generation technology; or to put it another way, you can have double the number of transistors on a chip and hence twice the functionality running 43% faster.

IC technology generations are described in terms of a characteristic size relating to the manufacturing process, which is based on the smallest feature size possible in that generation. Initially, this was measured in micrometres ( $\mu m$ ), but now it is in nanometres (nm). These values are often referred to as *technology nodes*.

Until 2005, this was usually taken as being the half-pitch of metal interconnections on DRAM; which was representative for all types of IC. More recently, as IC technology and scaling has got more complex, this single representative node idea is less meaningful.

Readers interested in the details of IC technology development should consult *The International Technology Roadmap for Semiconductors* (ITRS). This is a regularly published assessment of the next fifteen years of the semiconductor industry's future technology requirements, and contains a large amount of technical data. Their website is at [itrs.net](http://itrs.net).

## Powerful issue

An interesting issue with scaling is what to do with the power supply voltage. Ideally, it should be scaled by  $k$  like everything else, but that may be inconvenient. If each new generation of chips uses different supply

voltages, then their logic levels will not be compatible between generations, possibly making system design and interfacing difficult. Not scaling the voltage down also means that potentially the clock frequency can be increased by more than 1.43 times because CMOS delay decreases at higher supply voltages.

During the 1980s, supply voltages were not scaled and new chip generations kept the same supply voltage at 5V. The consequence of this so called *constant voltage scaling* is that the electrical field strengths (volts per meter) inside the chips increase. Scaling in which the supply voltage is reduced proportionately is called *constant field scaling* because the electric field strengths in the chip remain constant.

The increasing field strengths in constant voltage scaling cause problems such as hot

remain viable after the 1980s ( $0.8\mu m$  technology node) and hence the 1990s saw a reduction in power supply voltages, particularly for advanced logic ICs such as microprocessors. This is illustrated in Fig.2, which shows supply voltage ( $V_{DD}$ ) and MOSFET threshold voltage ( $V_{TH}$ ) against technology node.

The scaling theory we just described is somewhat simplified in a number of ways. In practice, voltages and transistor dimensions are not scaled by the same factor as they should be in pure constant field scaling. Also, it is not possible to scale everything by factor  $k$ ; for example, MOSFET threshold voltages is one area in which scaling is difficult. It can be seen in Fig.2 that the threshold voltage has not scaled down at the same pace as supply voltage.

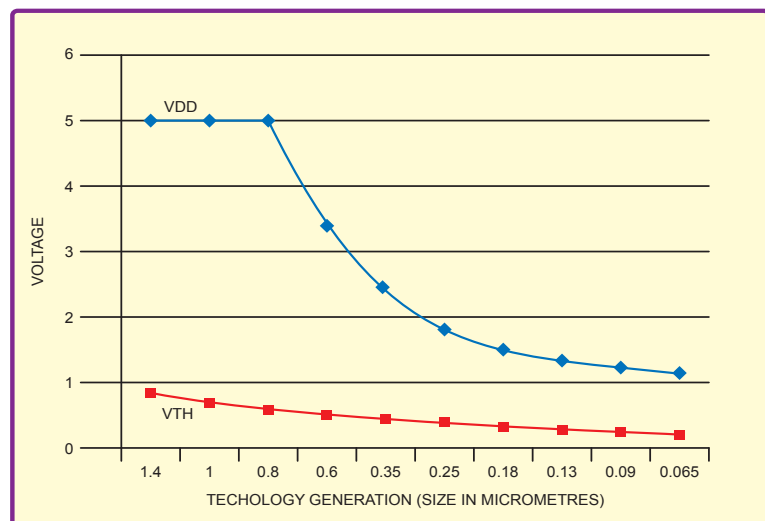


Fig.2. Changes in supply voltage ( $V_{DD}$ ) and MOSFET threshold voltage ( $V_{TH}$ ) with IC technology generation. The change from constant voltage scaling (5V supplies) to constant field scaling at the  $0.8\mu m$  node is clearly seen

carrier injection (HCI), in which charge carriers (electrons) are accelerated so much that they are able to penetrate parts of the chip where they should not be, causing damage to the chip and degrading performance. High field strength in the gate oxide causes time-dependent dielectric breakdown (TDDB) and hence transistor failures.

Another consequence of constant voltage scaling, is excessive power dissipation and chip heating. Switching power consumption in CMOS circuits is proportional to  $V^2fC$  where  $V$  is the supply voltage,  $f$  is the (clock) frequency and  $C$  is the load capacitance being driven (which in the simplest analysis is proportional to the transistor gate capacitance).

For constant voltage scaling, this power remains constant, or increases by  $(1/k)$  depending on the scaling of the clock frequency. This means that the power dissipation per unit area of the chip (power density) increases significantly ( $1/k^2$  to  $1/k^3$ ). Use of constant field scaling reduces power dissipation problems because switching power is reduced by  $k^2$ , the same factor as transistor area, so power density remains constant from one generation to the next.

## No longer viable

The problems with constant voltage scaling meant that this approach did not

Low threshold voltage is a problem because the transistors do not turn off very well, resulting in leakage currents. Although the leakage of each transistor is small, when it is multiplied millions of times it represents a significant power demand and is a serious problem in the most recent IC generations. Another complicating factor in scaling is that developments in circuit design techniques change the characteristics of circuits (such as maximum operating frequencies) and again cause deviations for idealised scaling theory.

A consequence of the fact that 'perfect' constant field scaling has not been possible is that power density and power dissipation did not remain constant as technology developed in the 1990s. This means that chips such as microprocessors have continued to produce more and more heat. Anyone familiar with PC motherboards as they progressed from using early 386s, via various Pentiums, to the latest models will have been aware of the increasing importance of the heatsink and cooling fan for the processor.

Back in the late 1990s, if you had plotted the trend for the power density of an Intel processor, and projected it forward to now you would have predicted processor power densities approaching that of the surface of the Sun (which is around  $6000 W/cm^2$ ).



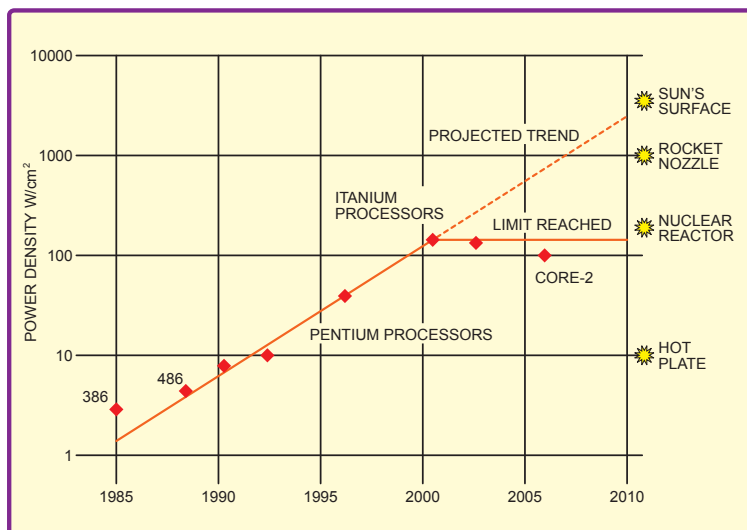


Fig.3. Intel Processor power dissipation. This graph is usually attributed to Shekhar Borkar of Intel

This is illustrated in Fig.3, which along with the Sun's surface, has a hot plate, a nuclear reactor and a rocket nozzle as power density reference points.

This figure is widely reproduced (in various forms) in technical papers, articles and presentations. It is often attributed to Shekhar Borkar, now director of Intel's Microprocessor Technology Lab. Borkar did as we just described, and analysed

the trends, at that time, in processor development, publishing a paper in the IEEE's *Micro* magazine in 1999. This was a very real problem for Intel – they cancelled the 4GHz Pentium 4 in 2001 due to heat dissipation problems. Subsequently, they announced dual core processors.

Like the move away from constant voltage scaling to lower supply voltages, this was another breakpoint where continuing to scale

in the same way as before was not going to work. Forced water cooling could probably handle processors dissipating up to around several hundred W/cm², but this would not be economically viable for everyday office and home PCs. Thus, power dissipation for processors has levelled off and increased performance has been achieved by improvements in processor architecture – moving to multiple core designs.

In this article, we have just scratched the surface of a large and complex subject. However, we hope we have shown the reason that modern digital (and mixed analogue and digital) ICs often use very low power supply voltages and why supply voltages have been changing over the last couple of decades.

## References

R. H. Dennard *et al*, 'Design of ion-implanted MOSFETs with very small physical dimensions,' *IEEE Journal of Solid-State Circuits*, SC-9, pp.256-268, 1974.

Borkar, S. 'Design challenges of technology scaling,' *Micro*, IEEE, vol.19, no.4, pp.23-29, Jul-Aug 1999

Haron, N.Z. Hamdioui, S. 'Why is CMOS scaling coming to an END?,' *3rd International Design and Test Workshop*, IDT 2008, pp.98-103, 20-22 Dec. 2008

*The International Technology Roadmap for Semiconductors*. [www.itrs.net](http://www.itrs.net)

## EPE BINDERS

**KEEP YOUR MAGAZINES SAFE –  
RING US NOW!**

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place. The binders are finished in hard-wearing royal blue PVC with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £7.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each). Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to:

Everyday Practical Electronics, Wimborne Publishing Ltd, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU.  
Tel: 01202 873872. Fax: 01202 874562.  
E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk)  
Web site: <http://www.epemag.com>

We also accept card payments. Mastercard, Visa, or Maestro. Send your card number and card valid from and expiry date plus Maestro Issue No. and the security code on the back of the card with your order.



**TO ADVERTISE IN  
EVERYDAY PRACTICAL  
ELECTRONICS**

**PLEASE CONTACT**

**Stewart Kearn on  
01202 873872**

**or email  
[stewart.kearn@wimborne.co.uk](mailto:stewart.kearn@wimborne.co.uk)**

**Laser**

*Why tolerate when you can automate?*



Home Automation



KAT5 AV transmission and IR control system



Barix Ethernet based MP3, communications and control systems

[www.laser.com](http://www.laser.com)

**Integrators, Installers, Trade  
and Retail customers welcome**



**C-Bus Shop  
C-Bus and  
C-Bus Wireless**

[www.cbus-shop.com](http://www.cbus-shop.com)

**Laser Business Systems Ltd**  
Tel: +44 (0) 20 8441 9788  
Fax: +44 (0) 20 8449 0430  
Email: [info@laser.com](mailto:info@laser.com)  
16 Garthland Drive, EN5 3BB

## SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

|       |                                 |       |   |
|-------|---------------------------------|-------|---|
| SP1   | 15 x 5mm Red Leds               | SP133 | 20 x 1N4004 diodes                          |
| SP2   | 12 x 5mm Green Leds             | SP134 | 15 x 1N4007 diodes                          |
| SP3   | 12 x 5mm Yellow Leds            | SP135 | 5 x Miniature slide switches                |
| SP5   | 25 x 5mm 1 part Led clips       | SP136 | 3 x BFY50 transistors                       |
| SP6   | 15 x 3mm Red Leds               | SP137 | 4 x W005 1.5A bridge rectifiers             |
| SP7   | 12 x 3mm Green Leds             | SP138 | 20 x 2.2/63V radial elect caps              |
| SP8   | 10 x 3mm Yellow Leds            | SP142 | 2 x Cmos 4017                               |
| SP9   | 25 x 3mm 1 part Led clips       | SP143 | 5 Pairs min. croc.clips (Red+Blk)           |
| SP10  | 100 x 1N4148 diodes             | SP144 | 5 Pairs min. croc. clips (assorted colours) |
| SP11  | 30 x 1N4001 diodes              | SP146 | 10 x 2N3704 transistors                     |
| SP12  | 30 x 1N4002 diodes              | SP147 | 5 x Stripboard 9 strips x 25 holes          |
| SP18  | 20 x BC182B transistors         | SP151 | 4 x 8mm Red Leds                            |
| SP20  | 20 x BC184B transistors         | SP152 | 4 x 8mm Green Leds                          |
| SP23  | 20 x BC549B transistors         | SP153 | 4 x 8mm Yellow Leds                         |
| SP24  | 4 x Cmos 4001                   | SP154 | 15 x BC548B transistors                     |
| SP25  | 4 x 555 timers                  | SP156 | 3 x Stripboard 14 strips x 27 holes         |
| SP26  | 4 x 741 Op-amps                 | SP160 | 10 x 2N3904 transistors                     |
| SP28  | 4 x Cmos 4011                   | SP161 | 10 x 2N3906 transistors                     |
| SP29  | 4 x Cmos 4013                   | SP164 | 2 x C106D thyristors                        |
| SP33  | 4 x Cmos 4081                   | SP165 | 2 x LF351 Op-amps                           |
| SP34  | 20 x 1N914 diodes               | SP166 | 20 x 1N4003 diodes                          |
| SP36  | 25 x 10/25V radial elect caps   | SP167 | 5 x BC107 transistors                       |
| SP37  | 12 x 100/35V radial elect caps  | SP168 | 5 x BC108 transistors                       |
| SP38  | 15 x 47/25V radial elect caps   | SP172 | 4 x Standard slide switches                 |
| SP39  | 10 x 470/16V radial elect caps  | SP173 | 10 x 220/25V radial elect caps              |
| SP40  | 15 x BC237 transistors          | SP174 | 20 x 22/25V radial elect caps               |
| SP41  | 20 x Mixed transistors          | SP175 | 20 x 1/63V radial elect caps                |
| SP42  | 200 x Mixed 0.25W CF resistors  | SP177 | 10 x 1A 20mm quick blow fuses               |
| SP47  | 5 x Min. PB switches            | SP178 | 10 x 2A 20mm quick blow fuses               |
| SP49  | 4 x 4 metres stranded core wire | SP181 | 5 x Phono plugs - assorted colours          |
| SP102 | 20 x 8 pin DIL sockets          | SP182 | 20 x 4.7/63V radial elect caps              |
| SP103 | 15 x 14 pin DIL sockets         | SP183 | 20 x BC547B transistors                     |
| SP104 | 15 x 16 pin DIL sockets         | SP186 | 8 x 1M horizontal trim pots                 |
| SP109 | 15 x BC557B transistors         | SP189 | 4 x 4 metres solid core wire                |
| SP112 | 4 x Cmos 4093                   | SP192 | 3 x Cmos 4066                               |
| SP115 | 3 x 10mm Red Leds               | SP195 | 3 x 10mm Yellow Leds                        |
| SP116 | 3 x 10mm Green Leds             | SP197 | 6 x 20 pin DIL sockets                      |
| SP118 | 2 x Cmos 4047                   | SP198 | 5 x 24 pin DIL sockets                      |
| SP124 | 20 x Assorted ceramic disc caps | SP199 | 4 x 2.5mm mono jack plugs                   |
| SP130 | 100 x Mixed 0.5W CF resistors   | SP200 | 4 x 2.5mm mono jack sockets                 |
| SP131 | 2 x TL071 Op-amps               |       |   |

### RESISTOR PACKS - C.Film


|      |                                   |       |
|------|-----------------------------------|-------|
| RP3  | 5 each value - total 365 - 0.25W  | £3.45 |
| RP7  | 10 each value - total 730 - 0.25W | £4.75 |
| RP10 | 1000 popular values - 0.25W       | £6.70 |
| RP4  | 5 each value - total 305 - 0.5W   | £4.30 |
| RP8  | 10 each value - total 610 - 0.5W  | £6.95 |
| RP11 | 1000 popular values - 0.5W        | £9.15 |

Catalogue available £1 inc. P&P or FREE with first order.

P&P £2.25 per order. NO VAT  
Cheques and Postal Orders to:  
**SHERWOOD ELECTRONICS,**  
**10 NEWSTEAD STREET,**  
**MANSFIELD, NOTTS. NG19 6JJ**

pico<sup>®</sup>  
Technology
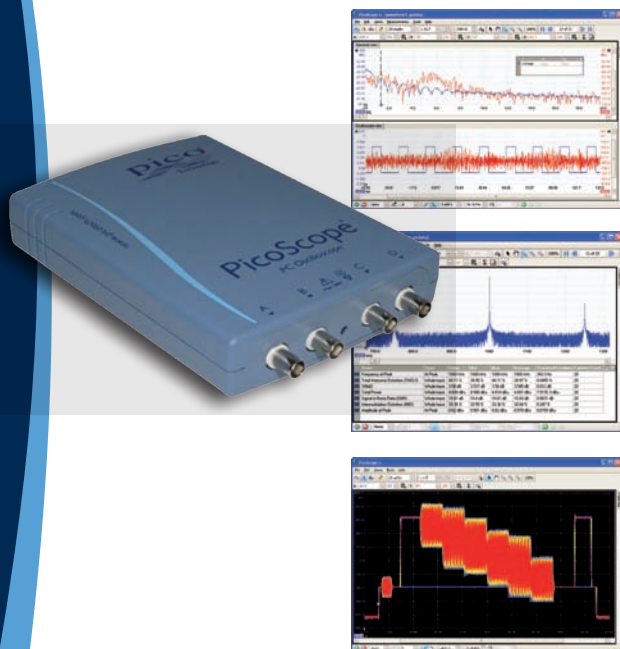
## The new PicoScope 4000 Series high-resolution oscilloscopes



PicoScope 4000 Series

The PicoScope 4224 and 4424 High Resolution Oscilloscopes have true 12-bit resolution inputs with a vertical accuracy of 1%. This latest generation of PicoScopes features a deep memory of 32 M samples. When combined with rapid trigger mode, this can capture up to 1000 trigger events at a rate of thousands of waveforms per second.

- **PC-based** - capture, view and use the acquired waveform on your PC, right where you need it
- **Software updates** - free software updates for the life of the product
- **USB powered and connected** - perfect for use in the field or the lab
- **Programmable** - supplied with drivers and example code

|               |  |
|---------------|--|
| Resolution    | 12 bits (up to 16 bits with resolution enhancement)  |
| Bandwidth     | 20 MHz (for oscilloscope and spectrum modes)   |
| Buffer Size   | 32 M samples shared between active channels  |
| Sample Rate   | 80 MS/s maximum  |
| Channels      | PicoScope 4224: 2 channels<br>PicoScope 4424: 4 channels                                     |
| Connection    | USB 2.0  |
| Trigger Types | Rising edge, falling edge, edge with hysteresis, pulse width, runt pulse, drop out, windowed |

[www.picotech.com/scope1053](http://www.picotech.com/scope1053)  
01480 396395

**e CRICKLEWOOD ELECTRONICS**  
Established 1981



Frustrated with your supplier?  
Visit our component packed website for a vast range of parts - old and new, many unavailable elsewhere!  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)

**1000's OF PRICES REDUCED!**

Alternatively phone us on  
020 8452 0161 with your requirements.



Visit our Shop, Call or Buy online at:  
[www.cricklewoodelectronics.com](http://www.cricklewoodelectronics.com)

**020 8452 0161** Visit our shop at:  
40-42 Cricklewood Broadway  
London NW2 3ET



## Easing Software Development

**W**hen writing software for a new project, particularly when using a new microcontroller in a new circuit, it's essential to start with a working and reliable framework. Creating this *each time* you build a new circuit becomes very time consuming, and you will find yourself repeating old mistakes, which gets very frustrating. Wouldn't it be better to design a simple framework once, and then reuse it?

We've covered this idea before in assembly language but it's worth taking a look at how we can address the issue when programming in 'C', a language we are told is 'portable'.

### In the frame

Having a flexible, reusable debugging and development framework that can be easily reused does require that the language you have written it in is itself portable between different processors. Assembly language is one of the least portable languages around, and even porting between a PIC16 and a PIC18 processor will prove a challenge.

Worse, if you design it with the 'lowest common denominator' in mind, then you will need to make compromises that reduce the utility of the software, making it hardly worth the effort. 'C' does indeed improve on this, but does itself suffer from portability issues. The difference is, however, that in 'C' the non-portable aspects can be isolated into a small portion of the code, with the rest being easily transferable between processor types – so long as you take a little care up front.

Fans of the 'C' programming language will tell you how portable a language it is, and that is true, up to a point. However, most PIC processors have a highly unusual 'non-standard' processor architecture, which does not fit well with the 'C' language. 'C' was designed for processors with a common code and data address bus, and a stack that exists within the normal address space.

The lower-end PIC processors have a separate code and data address space, and a very limited hardware stack. 'C' compilers that target these processors have to be somewhat imaginative in their application, and rely on some 'extensions' to the language to work.

The higher-end processors, such as the PIC32, have a completely different architecture to the PIC18 or PIC16 families (the PIC32 is, in fact, not a Microchip core at all, but a MIPS) and so do not suffer from this problem. As most of us will use C on a PIC18 or PIC24, we will have to take the differences into account.

### Framework

As with any other project it's important to define what you want to achieve before sitting down and writing code. Here is our list:

- Easy to modify for new projects
- Provide a template for source file layout
- Provide a stable hardware configuration
- Utilise low power operation
- Provide a serial interface for debugging
- Easy-to-enhance debugging facilities.

The first point is obvious, but the second may be less so. When you write software, especially a lot of it, the code can be much more readable if you use a consistent style. Comment headers for files and individual functions help you understand what the program does when you come back to it after a long break (or decide to reuse old code in a new project.)

The debugging features are not essential, but will prove very useful, if you have a spare UART interface available. If your application will require the only UART present on the chip, then it is still worth keeping a debugging interface during initial development until your code is stable. You should, as a minimum, try to keep a single I/O pin free for debugging output – even turning a pin high or low can help solve problems.

Once you have a serial port available for debugging it's possible to add very powerful software 'tools' into your framework to inspect variables and read or write to flash memory. Every application has its own particular features that benefit from inspection during development, so having an easy-to-expand debugging system should be on our wish list.

### Stable setup

The most important feature of any framework is to provide a known, stable setup. Even with a trivial hardware design, there is nothing more frustrating than spending hours

de-soldering and resoldering a circuit, trying to locate a hardware fault, only to find it's a software error. Just ask any hardware engineer.

Investing the time in getting a reliable system early on means that you can relax and concentrate on the fun stuff, progressing easily through the design. The initial implementation of a framework requires you to have a clear understanding of the inner workings of your hardware and microprocessor – or more specifically, the nuances of its datasheet – and getting this done first will mean no surprise circuit changes later on. Having an existing framework that you can 'port' to your new design will speed this process up too, and help you get to the fun stuff more quickly.

### Practical example

Although a standard framework may provide more features than you need or have code space for, these features can be removed as your own design progresses.

So let's not spend any more time talking about it, and take a look at a practical example.

We've put together a framework based around the PIC18F45K20. It's a fairly standard PIC18F processor, chosen simply because it's the part fitted to the PicKit3 Demo Board, and so it is easy to experiment with. (We'll be reviewing the PicKit3 in a later issue.)

The software is available on the *EPE* website, in this month's archive. The file is called *PicNMix-C-framework.zip*. We have

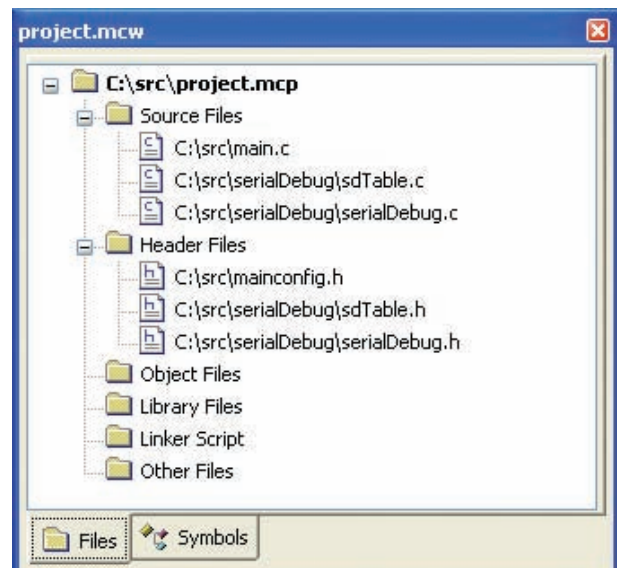


Fig.1. Source code layout

used the Microchip MPLAB integrated development environment and C18 C compiler as these are free and very powerful. Ironically, porting this code to a different vendor's compiler could be more difficult than porting it to another Microchip processor because different vendors handle the PIC's C language extensions in different ways.

## Organisation

The source code organisation can be seen in Fig.1. Including the Microchip .mcw and .mcp project files, only eight small files are required for implementation. Your own source code is placed in **main.c**, and you can add further project files as you see fit. The serial debugging support code has been isolated in its own subdirectory as it is completely independent of your project code.

Your main program source code is placed in the file **main.c**, located in the top level directory with the two MPLAB project files. You are free to add additional source files and link them into **main.c**; this file simply adds the hardware initialisation and debugging support. **mainconfig.h** adds a single location in which to store the configuration bit settings for your chosen processor.

The **main()** function within **main.c** is a simple loop, typical of main embedded application control loops. There are two calls of interest here: **Sleep()** and **serialDebug()**.

The **sleep** call is optional, and is used to place the processor into a lower power state. The call effectively halts program execution until an interrupt has taken place. It's only of use if you wish to run the processor at low power.

The **serialDebug** call is the 'hook' into the debugging support system. It normally executes just two simple 'if' statements and then returns, so consumes very little of your processing time. Only if a command has been entered via the serial port does it activate and run whatever command you have entered. It then outputs whatever message your debug handling routine provides, and then goes back to 'quiet mode'.

## Debug command

The **SerialDebug** function is implemented in the file **serialDebug.c**. The only other function in this file, **sdRxChar()**, is the routine called by the main application whenever a character has been received

```
/* See if we can find the command requested */
cmdLen = strlen(rxBuff);

if ( (rxBuff[0] == '\r') || (rxBuff[0] == '\n') ) {

    /* Looks like just the enter pressed. Show prompt */
    putsUSART((const far rom char *)"\r\n> ");
} else {

    /* Has a valid command name been entered? */
    while (
        (sdp->name != NULL) &&
        (strncmpram2pgm((far rom char *)sdp->name, rxBuff, cmdLen) )
    ) {

        sdp++;
    }

    /* If we have, call the handler, otherwise display error msg */
    if ( sdp->name != NULL ) {
        putsUSART((const far rom char *)"\r\n");
        sdp->funcptr(ptr);
        putsUSART((const far rom char *)"\r\n> ");
    } else {
        putsUSART((const far rom char *)"\r\nInvalid command. Try 'help'\r\n> ");
    }
}

/* Allow the debugger to receive further commands */
cmdReceived = 0;
}
```

Fig.2. Debug command selection

for the debugger. You would call this from whatever method you use for receiving serial data from the outside world. The **main.c** file provides an example interrupt driver receive function, which calls **sdRxChar**, but you can replace it with your own code if you wish – even a bit-bashed serial receive interface.

A debug command can have parameters expressed in decimal or hexadecimal, and enable you to implement complex commands, such as display regions of flash or ram memory. The way the commands are processed by **SerialDebug** is shown in Fig. 2.

The highlighted line of code in Fig. 2 does all the work. A data structure variable **cmdTable** (pointed to by **sdp**) is defined in **sdTable.c**. This variable is a table listing the commands available with the function names and a short textual description.

Using a table like this significantly simplifies adding new functions into a debugging system. Once your new feature is implemented, you simply add a single line to the **cmdTable** variable and your function will become available and visible in the list of commands.

## Smaller processors

And what about the PIC16, and smaller families? C compilers do exist, but the challenge is greater. Smaller processors are less complex and so can be mastered quickly anyway, making a portable development framework less important. There may be less code and data space available for a debug system too. In cases such as these, you have to rely on a simulator to debug the code, and perhaps an LED being controlled by debug statements at interesting points.

## Coming up

Next month, we step away from the Microchip range of processors for a change and take a look at a very unusual one – the humorously named 'Propeller' processor from Parallax Inc, the people who brought us the Basic Stamp. This processor has on-chip video generation support hardware, and promises colour video generation. It looks like it could be very interesting!



**EPE Online**  
www.epemag.com

Get your magazine 'instantly' anywhere in the world – buy and download from the web.

**TAKE A LOOK, A FREE ISSUE IS AVAILABLE**

A one year subscription (12 issues) costs just \$18.99(US)

Back issues are also available





# Practically Speaking

Robert Penfold looks at the Techniques of Actually Doing it!

**W**HEN I first started building electronic projects, which was probably long before most *EPE* readers were born, electronic kits were all the rage. In the kit's accompanying instruction leaflet you were frequently encouraged to handle all the components to familiarise yourself with them, and to ensure that you could accurately identify each one.

This might still sound like a good idea, and it certainly has some merit, but it is not advice that you are likely to be given these days. In fact, you are likely to be warned against any unnecessary handling of some components.

## Hands-free

I suppose that this change in approach has been brought about by two changes in electronics. One is simply that the components used to be relatively large and tough. Some of the older valves (tubes) had glass cases that would almost certainly break if they were dropped on the floor, but most components were large by current standards, and pretty robust. Most modern components are primarily designed for automated construction methods, and in normal use they receive little or no handling.

This is not to say that they will fall apart in your hands. However, the 'look but don't touch' approach has some merit with modern components, and when you do need to handle them it is usually best to adopt the 'kid gloves' approach. In particular, it is not a good idea to start bending and forming leadout wires until it is actually time to fit the components into place. The way in which the leadout wires are connected to the body of the component seems to be a weakness with some modern components.


Pulling the leads can cause problems, but the more usual source of trouble is when bending a leadout wire close to the body of the component, and it is something that should be avoided as far as possible. There seem to be a variety of reasons for this action causing damage, which is often in the form of a leadout wire breaking off completely. In less severe cases, it seems to be a weakness in the body of the component that results in part of it close to the lead breaking away.

Glass-cased diodes are perhaps the most common source of this problem, but it can occur with resistors and other axial components (the tubular type that have a lead at each end). The damage does not necessarily prevent the component from working and staying within its specification. However, a component that shows obvious signs of physical damage is unlikely to have good reliability, and it is advisable to

discard it and obtain a replacement. There should be nothing to worry about if the damage is simply damage to the paint.

A drawback of some small resistors is that the manufacturing process seems to make the leads quite weak where they enter the body of the component. This has to be regarded as a design flaw, and if you obtain any resistors of this type it is probably best to avoid buying any more. Again, the problem comes to a head if the leadout wire is bent close to the body of the component. The wire bends at the weak point, and if you are unlucky it breaks off.

There is often no way of telling whether a component is one of the more vulnerable types or one that is relatively tough, so it is probably best to handle and use all of them with due care. Avoid any unnecessary flexing or bending of the leadout wires, and when forming leadout wires, avoid any bends very close to the bodies of the components. A strategically placed fingernail or screwdriver blade makes it easy to produce a bend at the required point in a lead, while not placing undue force on the nearby sections of the lead.

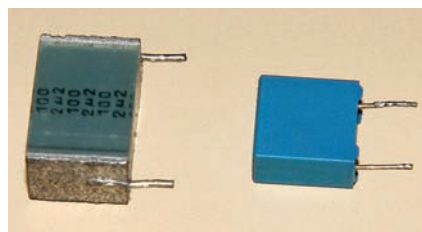

*Fig. 1. Open construction capacitors like the one on the left are far less hardy than the cased type on the right. Any capacitors that lack a proper casing should be treated very carefully*

## End of a capacitor

Some printed circuit mounting (PCM) capacitors used to be notorious for the ease with which one of the leads would part company from the rest of the component. Any outward pressure on the leads was likely to result in one of the leads splitting away from the body to which it was soldered. With this type of capacitor it was not just a matter of avoiding unnecessary handling. When fitting a component of this type it was important to make sure that it dropped easily into place and, where necessary, to carefully straighten the leads in order to make the component a proper fit prior to fitting it onto the circuit board. Simply squeezing a component into place if it was a poor fit was likely to result in one of the leads coming adrift.

Modern PCM capacitors are mostly much tougher than the early types, which often lacked a proper casing to give overall strength to the component. An old PCM capacitor is shown in Fig.1 (left), and its open construction is readily apparent. Fig.1 (right) shows a modern equivalent, which has a fairly tough plastic case that protects the component and holds the leads firmly in place.

There are still open-style PCM capacitors in circulation, and they must be treated with due care if you use them. It is also worth bearing in mind that some PCM capacitors that appear to have a plastic case actually have something that could more realistically be regarded as a thick coating of paint. This type of coating is good at keeping out moisture and other forms of contamination, but does not really impart a great deal of strength to the component. Capacitors such as these need to be treated with due care, and are not much tougher than the open construction type.

It is really non-electrolytic PCM capacitors that tend to suffer from the problem of dropping leads. PCM electrolytic capacitors use a different form of construction that makes them physically quite tough. The problem is mainly associated with the larger non-electrolytic components that have some form of plastic dielectric, which mainly means the polycarbonate, polyester, and Mylar types.

These days it is perhaps the physically tiny capacitors that tend to be the most vulnerable. Some types, such as ceramic and tantalum capacitors, seem to be designed with small physical size as the priority, and physical strength as an afterthought. In addition to problems with detached leads, some ceramic capacitors are quite thin and brittle. Pieces can break off if they are not handled and used carefully.

## Charged atmosphere

A major difference between the components of today and those of (say) 50 years ago, is that the components of yesteryear were not vulnerable to high voltages. They were mostly designed to operate with potentials of a few hundred volts, or even a few thousand! By comparison, modern components seem to be predominantly designed for use on supply potentials of just a few volts. Voltages even slightly higher than this can prove to be fatal for many modern integrated circuits.

This vulnerability to quite modest voltages becomes a serious problem when it is combined with the various MOS technologies that are used in the manufacture of many modern semiconductors. The components are reasonably safe once fitted

into a completed circuit board, but there is a real risk of them being zapped before they actually reach the circuit!

The source of the problem is the voltages present in a normal environment, some of which are surprisingly high. Most of the time you are left unaware of their presence and these voltages only become apparent when they reach sufficient magnitude to grab your attention. This usually means something like your hair standing on end, or a spark being generated each time you stroke the cat.

Semiconductors that are not manufactured using MOS technology tend to be regarded as safe from static charges, while MOS devices are regarded as highly vulnerable. There is some truth in this belief, but it is probably not a strictly accurate way of viewing the matter. The majority of semiconductor manufacturers now warn against getting any semiconductor components close to large static charges.

While semiconductors are mostly untroubled by short bursts of high current, excessive voltages, even when extremely short in duration, tend to damage components sufficiently to leave them in an unusable state. Whether the source of the voltage is a static charge or a normal power source such as a battery is of no practical importance. Either way, a suitably high potential will result in damage to a semiconductor component.

Therefore, it is advisable to keep all semiconductor components away from possible sources of high voltage static charges. If you have any prolific generators of static electricity in your home you will probably be all too aware of them already. Common sources are TV sets, computer monitors, carpets, and pets. It is perhaps worth pointing out that although loose components are the most vulnerable, it is still possible for damage to occur once components have been fitted onto a circuit board. The components should be safe once the circuit board has been housed in a case, but the semiconductors it contains remain vulnerable until it is protected by some form of housing.

## At risk

Practically all semiconductors are to some extent vulnerable to static charges, but it is certainly the MOS types that are at the greatest risk. It is quite normal for an MOS device to have an extremely high input resistance of a million megohms or more. The equivalent figure for ordinary bipolar transistors is more like a few kilohms, which quickly leaks away any static charges long before dangerously high potentials are reached. By contrast, the input resistance is so high for MOS devices that, even over a period of time, static charges are not significantly leaked away. Instead, they are left to build up, possibly reaching such a high potential that the device breaks down and is destroyed.

It is important to realise that MOS components can be damaged by relatively small static voltages, and that we are not necessarily talking in terms of a few hundred volts or more with sparks flying. Voltages of sufficient magnitude to damage MOS devices are often found in everyday environments, but these voltages are often too low to make their presence obvious. You

can pick up an MOS component and accidentally zap it without there being any noticeable sign of a problem. You only become aware that all is not well when the completed project fails to work.

## Sent packing

Vulnerable devices should be supplied in some form of anti-static packing, and they are completely safe from static charges while they are kept in this packaging. There are several forms of anti-static packing in common use, including conductive foam, blister packs, plastic tubes, and conductive plastic bags. Some typical examples of anti-static packing are shown in Fig.2.

There are two basic approaches to protecting the components, and one of these is to 'short-circuit' all the pins or leads of the components together. While this does not actually keep high voltages at bay, it prevents a high voltage from existing between two of the component's terminals. This has the desired effect because it is not a high voltage *per se* that causes the damage. It is a high voltage between two pins that 'blows' one or more semiconductor junctions and destroys the device.

The second approach is to insulate components from the outside world, and this is the one taken with the plastic tubes. The blister packs that have a conductive foil backing take a 'belt and braces' approach, with both types of protection being provided.

Unnecessary handling of MOS devices should obviously be avoided, and they should be left in their anti-static packaging until it is time for them to be fitted to the circuit board. Semiconductors sometimes come complete with various warning notices which imply that the components have no chance of survival unless they are handled in an environment that is protected by some very expensive anti-static equipment.

These notices tend to exaggerate the problem though, and it is certainly not essential to use expensive equipment, even when dealing with the most vulnerable components. This is just as well, since a few simple precautions are the only option available to most electronic hobbyists.

An important precaution is to keep the components well away from any known or likely sources of static charges. In a similar vein, when building projects do not wear clothes that might generate static charges. These days, manmade fibres are normally mixed with natural fibres, and this has made the problem far less common than it used to be. However, if you have any clothes that shown any signs of producing static charges; do not wear them when building electronic projects.

Another important precaution is to fit integrated circuits to the circuit board via sockets. This is definitely advisable with any integrated circuits, MOS or otherwise, but it is essential with the MOS variety.

Always try to avoid touching the pins any more than is absolutely necessary when fitting semiconductors to a circuit board. Unfortunately, it will not usually be possible to avoid touching them altogether. It might be possible if you have an integrated circuit insertion tool, but there will still be



Fig.2. Three types of anti-static packaging. Blister pack (top left), conductive foam (top right), and a conductive plastic bag (bottom)

the occasional awkward component that requires some straightening of the pins by hand before it will fit into the holder.

## Down to earth

Although much of the available anti-static equipment is probably too expensive for serious consideration by amateur users, there are two items that are practical propositions. Both rely on the fact that static charges can be removed by leaking them away to 'earth'. An earthing wristband almost certainly represents the most cost-effective item of anti-static equipment. In addition to the wristband itself, there is an earthing plug, and a lead to connect this to the wristband (Fig.3).

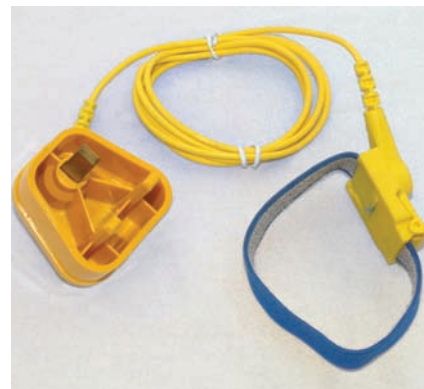


Fig.3. An earthing wristband can be obtained quite cheaply these days, and enables sensitive components to be handled without fear of zapping them


The plug looks a bit like an ordinary mains plug, but it only carries an earth connection, and the other two pins are dummies made from plastic. There is probably no realistic chance of getting a severe electric shock from one of these devices, but a high value protection resistor is included in the lead anyway.

An earthing mat can be used on the workbench, and it is simply a mat made from a conductive material that is earthed in the same way as an earthing wristband. The presence of the mat guarantees that there can be no build-up of static charges in the work area. Anything brought into the work area should be placed on the mat, where any static charges will be earthed before they have a chance to cause any problems.



# EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

## ELECTRONICS PROJECTS

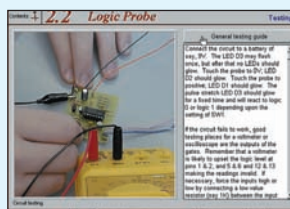


Logic Probe testing

*Electronic Projects* is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.

## ELECTRONIC CIRCUITS & COMPONENTS V2.0

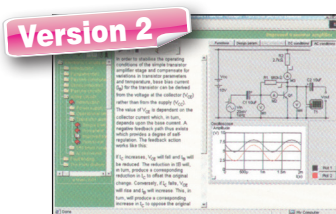


Circuit simulation screen

*Electronic Circuits & Components V2.0* provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units and multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op amps, logic gates. **Passive Circuits**. **Active Circuits**. **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams.

Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

## ANALOGUE ELECTRONICS

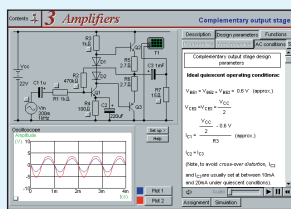


Complimentary output stage

*Analogue Electronics* is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections). **Op Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections). **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections). **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

## DIGITAL ELECTRONICS V2.0

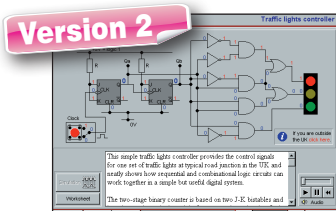


Virtual laboratory - Traffic Lights

*Digital Electronics* builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (above), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

## ANALOGUE FILTERS

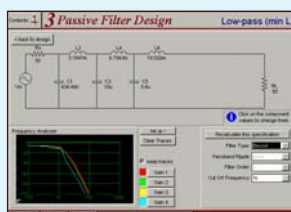

Filter synthesis

*Analogue Filters* is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

## PRICES

Prices for each of the CD-ROMs above are:  
(Order form on third page)

|   |      |          |
|---|------|----------|
| Hobbyist/Student .....                        | £45  | inc VAT  |
| Institutional (Schools/HE/FE/Industry) .....  | £99  | plus VAT |
| Institutional 10 user (Network Licence) ..... | £249 | plus VAT |
| Site licence .....                            | £499 | plus VAT |

(UK and EU customers add VAT at 15% to 'plus VAT' prices)



## ROBOTICS & MECHATRONICS



Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations

# PICmicro TUTORIALS AND PROGRAMMING


## HARDWARE

### VERSION 3 PICmicro MCU development board

*Suitable for use with the three software packages listed below.*

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

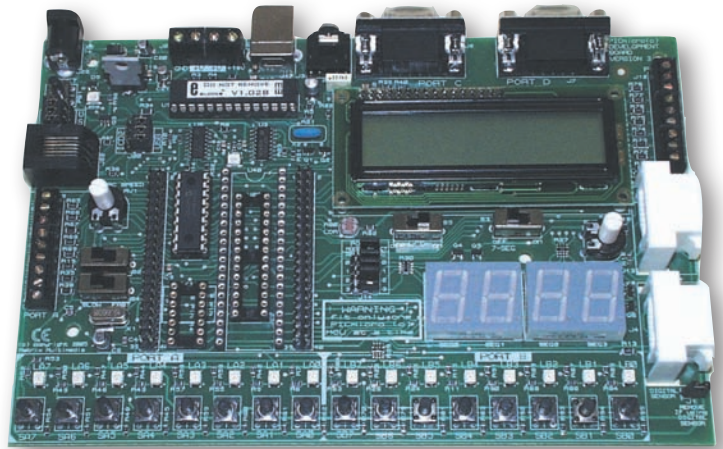- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



**£158 including VAT and postage, supplied with USB cable and programming software**

## SOFTWARE


### ASSEMBLY FOR PICmicro V3

(Formerly PICTutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICTutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

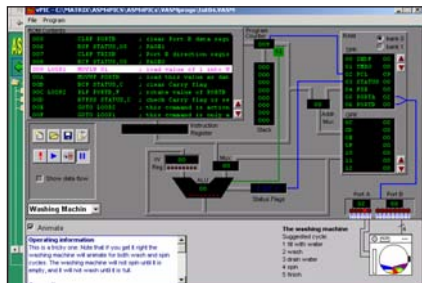


### 'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

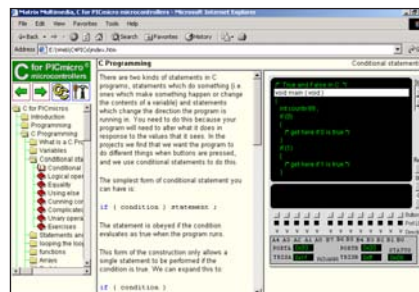- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.  
Flowcode will run on XP or later operating systems

### FLOWCODE FOR PICmicro V4

**FREE** with Flowcode V4 (student and institutional versions) ECIO board – a 28-pin reprogrammable microcontroller.

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- pulse width modulation
- I2C. New features of Version 4 include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



## PRICES

Prices for each of the CD-ROMs above are:  
(Order form on next page)

(UK and EU customers add VAT at 15% to 'plus VAT' prices)

|  |      |          |
|--|------|----------|
| Hobbyist/Student .....                                     | £45  | inc VAT  |
| Institutional (Schools/HE/FE/Industry) .....               | £99  | plus VAT |
| Institutional/Professional 10 user (Network Licence) ..... | £350 | plus VAT |
| Site Licence .....   | £699 | plus VAT |
| Flowcode Institutional (Schools/HE/FE/Industry) .....      | £149 | plus VAT |
| Flowcode 10 user (Network Licence) .....                   | £399 | plus VAT |
| Flowcode Site Licence .....                                | £799 | plus VAT |



## SPECIAL PACKAGE OFFER

### TINA Pro V7 (Basic) + Flowcode V3 (Hobbyist/Student)

#### TINA Analogue, Digital, Symbolic, RF, MCU and Mixed-Mode Circuit Simulation, Testing and PCB Design

TINA Design Suite is a powerful yet affordable software package for analysing, designing and real time testing analogue, digital, MCU, and mixed electronic circuits and their PCB layouts. You can also analyse RF, communication, optoelectronic circuits, test and debug microcontroller applications.

Enter any circuit (up to 100 nodes) within minutes with TINA's easy-to-use schematic editor. Enhance your schematics by adding text and graphics. Choose components from the large library containing more than 10,000 manufacturer models. Analyse your circuit through more than 20 different analysis modes or with 10 high tech virtual instruments. Present your results in TINA's sophisticated diagram windows, on virtual instruments, or in the live interactive mode where you can even edit your circuit during operation.

Customise presentations using TINA's advanced drawing tools to control text, fonts, axes, line width, colour and layout. You can create, and print documents directly inside TINA or cut and paste your results into your favourite word-processing or DTP package.

TINA includes the following Virtual Instruments: Oscilloscope, Function Generator, Multimeter, Signal Analyser/Bode Plotter, Network Analyser, Spectrum Analyser, Logic Analyser, Digital Signal Generator, XY Recorder.

**Flowcode V3 (Hobbyist/Student)** – For details on Flowcode, see the previous page.

This offer gives you two separate CD-ROMs – the software will need registering (FREE) with Designsoft (TINA) and Matrix Multimedia (Flowcode), details are given within the packages.

**Get TINA + Flowcode for a total of just £58, including VAT and postage.**

**£58.00  
inc. VAT  
and p&p**

## PROJECT DESIGN WITH CROCODILE TECHNOLOGY

### An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more.

Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams.

Nearly all the circuits can be instantly simulated in Crocodile Technology\* (not included on the CD-ROM) and you can customise the designs as required.

#### WHAT'S INCLUDED

Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays, Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.

#### Runs in Microsoft Internet Explorer

\*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: [www.crocodile-clips.com](http://www.crocodile-clips.com).

Animated diagrams run without Crocodile Technology.

**Single User £39.00 inc. VAT.**


**Multiple Educational Users (under 500 students) £59.00 plus VAT. Over 500 students £79.00 plus VAT.**

(UK and EU customers add VAT at 15% to "plus VAT" prices)

**Over 150 pages  
Over 600 images**



## DIGITAL WORKS 3.0

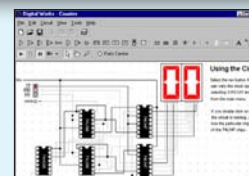

#### Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning.

**Hobbyist/Student £45 inc. VAT.**

**Institutional £99 plus VAT.**

**Institutional 10 user £249 plus VAT.**

**Site Licence £599 plus VAT.**

## ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Now contains Irfan View image software for Windows, with quick-start notes included.

**Price £19.95 inc. VAT**



Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

## Please send me: CD-ROM ORDER FORM



- ☐ Electronic Projects
- ☐ Electronic Circuits & Components V2.0
- ☐ Analogue Electronics
- ☐ Digital Electronics V2.0
- ☐ Analogue Filters
- ☐ Electronics CAD Pack
- ☐ Robotics & Mechatronics
- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode V4 for PICmicro + ECIO
- ☐ Digital Works 3.0

#### Version required:

- ☐ Hobbyist/Student
- ☐ Institutional
- ☐ Institutional/Professional 10 user
- ☐ Site licence

**Note:** The software on each version is the same, only the licence for use varies.

- ☐ PICmicro Development Board V3 (hardware)

- ☐ TINA Pro V7 Basic + Flowcode V3 Hobbyist/Student
- ☐ Electronic Components Photos; Version 1.1
- ☐ Project Design – Single User
- ☐ Project Design – Multiple User (under 500 students)
- ☐ Project Design – Multiple User (over 500 students)

Full name: .....

Address: .....

Post code: ..... Tel. No: .....

Signature: .....

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £ .....

☐ Please charge my Visa/Mastercard/Maestro: £ .....

Valid From: ..... Card expiry date: .....

Card No: ..... Maestro Issue No. ....

Card Security Code ..... (The last 3 digits on or just under the signature strip)

## ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world EU residents outside the UK add £5 for airmail postage per order

**Institutional, Multiple User and Deluxe Versions** – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add 15% VAT or provide your official VAT registration number).

**Send your order to:**  
**Direct Book Service**  
**Wimborne Publishing Ltd**  
**Sequoia House, 398a Ringwood Road**  
**Ferndown, Dorset BH22 9AU**

To order by phone ring  
**01202 873872. Fax: 01202 874562**

Goods are normally sent within seven days

**E-mail: [orders@wimborne.co.uk](mailto:orders@wimborne.co.uk)**

**Online shop:**  
**[www.epemag.com](http://www.epemag.com)**



# READOUT

Email: [editorial@wimborne.co.uk](mailto:editorial@wimborne.co.uk)

Matt Pulzer addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly



**WIN AN ATLAS LCR ANALYSER WORTH £79**  
An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd, will be awarded to the author of the Letter Of The Month. The Atlas LCR automatically measures inductance from 1mH to 10H, capacitance from 1pF to 10,000µF and resistance from 1Ω to 2MΩ with a basic accuracy of 1%. [www.peakelec.co.uk](http://www.peakelec.co.uk)

## ★ LETTER OF THE MONTH ★

### Short circuit test warning

Dear Editor

I am concerned at some of the comments made in the January 2010 issue of *EPE* in the *Ingenuity Unlimited* item 'Wartbox' about plug top ('wall-wart') power supply units (PSU).

The writer suggests shorting the output to determine the output current. Depending on the design of the circuit in the PSU, this is not normally a good idea. You could damage it and the resulting current value will be the short-circuit value, not the normal maximum rated output current.

These plug-top PSUs come in five types:

- Transformer unit – contains a transformer only, markings should show output is AC.
- Unregulated unit – contains transformer, rectifier and smoothing capacitor; output is DC, but is unregulated. With no load, or a low current load, the output voltage will be much higher than the rated output voltage, because the capacitor

charges up to the peak voltage of the secondary of the transformer (about 1.4 times the transformer secondary RMS voltage). The marked voltage on the unit is normally the voltage when the rated current is being delivered. To estimate the voltage at the rated current, divide the off-load voltage by 1.28.

- Regulated unit – transformer, rectifier, smoothing capacitors and linear regulator circuit. Provided the unit stays within its current rating, the voltage is constant and independent of load.

- Switched-mode type that uses a mains transformer – similar to the linear regulated unit, but uses a switched-mode regulator circuit. Again, within its current rating, the voltage is constant and independent of load.

- Switched-mode type that directly uses the mains voltage. This type does not use a normal mains transformer (and is therefore smaller and lighter). Instead, it rectifies the mains to produce about 330V DC (when used on 230V AC mains supplies) and then converts this to a high frequency AC current, which is fed to a high frequency transformer. The output is rectified and smoothed. The result is a regulated DC output.

Some regulated units and switched-mode types have current-limiting protection, and/or short-circuit protection. However, the other PSUs normally only have a thermal fuse (and some of the really cheap imported ones don't even have that). The fuse is part of the transformer and is not replaceable; once 'blown', the unit is scrap.

In the types that don't have a regulator circuit to limit the current (until the thermal fuse 'blows'), the only component that provides any limiting factor is the transformer. But these are cheap transformers, and by shorting the output you are putting them under a great deal of stress – not recommended.

**Mark Kinsey,  
Weston-super-Mare, by email**

*Useful advice Mark, and thank you for the overview of the 'wall-wart' types. Plus, I'd like to reiterate that readers should only tackle this kind of mains-based work if they are quite clear they understand the dangers and correct use of mains electricity.*

### Soldering advice

Dear Editor

Having read Alan Winstanley's soldering guide on the internet, I have to congratulate him. Everything I've ever read flies straight into 'solder this item to that'. This was the first time I encountered anything sensible on the art of soldering, and anyone new to electronics needs to read this prior to attempting any soldering project.

I have worked with stained glass extensively over a period of time, so I have a fair amount of soldering experience, although of a totally different nature. This type of fine soldering with limited heat input is new to me, so thank you again for providing me with this helpful guide.

**Chris Watkins, South Africa,  
by email**

*We're glad to be of help! Other readers can access Alan's advice at: [www.epemag.wimborne.co.uk/solderfaq.htm](http://www.epemag.wimborne.co.uk/solderfaq.htm)*

### Thanks for thanks!

Dear Editor

Many thanks for the 'Honourable mention' in December's issue, your comment is most kind and I must say that I and Chris, my 'tother half, are really touched (but she's not surprised as I'm always trying to help mend things for people!). I'm sure that if John Becker had been alive, he'd have approved too.

From the technical point of view, this was a first-time experience for me because I mended Terry Buchanan's exposure meter by remote control! I never had the physical equipment, only photographs sent by email. (What Terry

lacks in electronic knowledge, he certainly makes up for in his mastery of photography.)

I did email the manufacturer for circuit details, but all I got back was a firm refusal written in polite German.

Ah well, not everyone wants to help.

**Godfrey Manning,  
Edgware, by email**

*Again, well done Godfrey! – troubleshooting is always tricky, but you succeeded without having access to the equipment in question and a polite if unhelpful brush off from the manufacturer.*



**IF YOU HAVE A SUBJECT YOU WISH TO  
DISCUSS ON THIS PAGE  
PLEASE EMAIL US AT:  
[editorial@wimborne.co.uk](mailto:editorial@wimborne.co.uk)**



# Ingenuity Unlimited


Our regular round-up of readers' own circuits

## WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser
- Frequency Meter
- Multimeter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours.

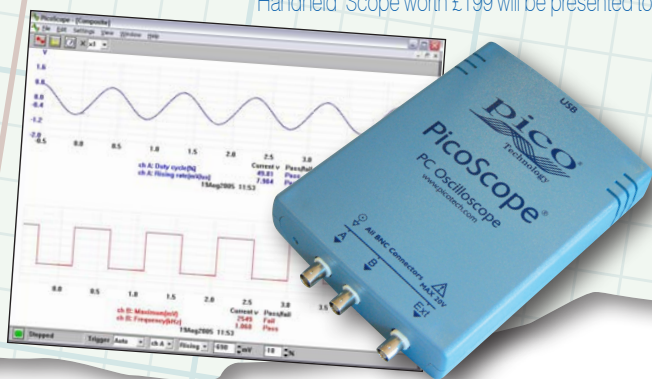After every 20 published IU circuits, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.



We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas must be the reader's own work and must not have been published or submitted for publication elsewhere.

The circuits shown have NOT been proven by us. Ingenuity Unlimited is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. Please draw all circuit schematics as clearly as possible. Send your circuit ideas to: Ingenuity Unlimited, Wimborne Publishing Ltd, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Email: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk). Your ideas could earn you some cash and a prize!

## Spectra-Lite II – a colourful display

In February 1992, *EE* magazine published the *Spectra-Lite*, a colourful LED display which enabled one to advertise one's hobby (electronics) on one's lapel. This circuit, claimed *EE*, would have people 'intrigued and speechless'.

The circuit of Fig.1 accomplishes much the same as the *Spectra-Lite*, only in a more simple fashion, continually cycling a tri-colour LED (LED1/LED2) through red, orange, green, and back again.

### How it works

The circuit which surrounds IC1a is a simple clock generator, which produces a slow sawtooth waveform at input pin 1, and a squarewave waveform at output pin 2. IC1b and IC1c are wired in parallel to boost output current. This circuit is repeated, except in inverted form, by IC1f. A sawtooth waveform is produced at the junction of resistor R3 and capacitor C3, while a squarewave waveform is produced at output pin 12. Again, IC1d and IC1e are used to boost output current. In short, while the voltage at IC1a input pin 1 rises, so the voltage at IC1f input pin 13 falls, and vice versa.

The resistors which charge and discharge timing capacitors C2 and C3 (R2 and R3 respectively) are of a sufficiently low value to illuminate an LED, while simultaneously charging and discharging C2 and C3. Zener diodes ZD1 and ZD2 drop 3V each, so as to adjust the voltage across LED1/LED2 downward to a suitable level for controlling the brightness of these two LEDs. If desired, 1N4001 diodes may be wired in series with Zener diodes ZD1 and ZD2 to tweak the performance of the LEDs.

The circuit requires a number of 'ground rules' in order to work. Resistor R1 and R4 should have significantly higher values than R2 and R3, or capacitors C2 and C3 will fail to charge. R1 and R4, calculated in series with R2 and R3, should have sufficiently low values to illuminate the LEDs brightly. Capacitors C2 and C3 should have sufficiently high values to keep the values of R2 and R3 low, though not too low, so as not to overload IC1. Components surrounding IC1a and IC1f should ideally be matched.

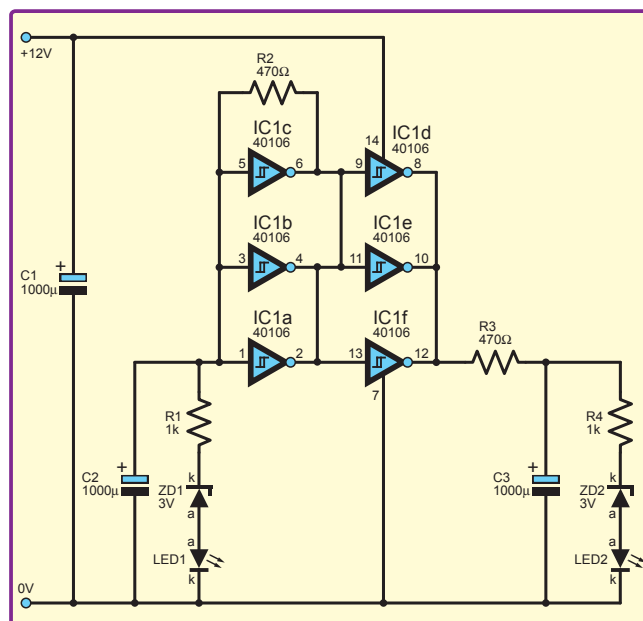


Fig.1. Complete circuit diagram for the Mk2 version of the *Spectra-Lite*

After switch-on, C3 requires a few cycles longer than C2 to attain its full charge and discharge cycle. The circuit has a moderate current consumption at about 20mA. The tri-colour LED is a dual red/green type in a single package, with a common cathode (k).

Thomas Scarborough  
Cape Town, South Africa



# Max's Cool Beans

By Max The Magnificent

## Book it!

**W**ELL, I'm a very happy person at the moment, because my wife – Gina the Gorgeous – presented me with my first 'toy' based on electronic paper as my Christmas present this year. Much to my surprise, she gave me a Kindle electronic book reader from Amazon ([www.amazon.com/gp/product/B0015T963C](http://www.amazon.com/gp/product/B0015T963C)). Meanwhile, my 15-year old son gave me a leather cover for the little rascal (by which I mean my Kindle, not my wife), and the two dogs and the cat – Henri, Lili, and Rocket, respectively – surprised me with a clip-on LED-based night light (at least, that's what it said on the wrapping paper; goodness only knows where they got the money).

I've been pondering buying one of these little beauties for ages and ages, but I never took the plunge ... now I'm kicking myself that I waited so long. At the time of writing, there are two models available. Gina gave me the smaller version that is 203mm (8in) tall, 135mm (5.3in) wide, and 9mm (0.36in) thick, with a 152mm (6in) diagonal display. This really is amazing. It's about the same size (area-wise) as a typical paperback book and only as thick as a pencil – see photo. It's also incredibly light; even with its leather cover (not shown here), it weighs only about as much as a regular paperback book.

This version holds about 1500 books and has international wireless capability that works in about 100 countries around the globe. The great thing here is that you don't have to sign up for a wireless service or anything – it just comes with the Kindle, with no monthly fees and no annual contracts. Also, you don't need to go hunting for a 'wireless hotspot' – it works pretty much wherever you are, just like a cellphone.

Not surprisingly, when the wireless is on, it does tend to drain the battery faster than when it's off, but you only need the wireless to be powered-up when you are searching the Amazon store (or the rest of the web) and when you are downloading a book or a magazine or whatever. Once you've loaded any items you wish to read onto your Kindle, you can turn the wireless off (I make a point of deactivating the wireless when I'm not using it). I've been using my Kindle for an average of about one hour a day; and after two weeks it still shows that the battery is half full from its original charge, which I think is jolly impressive.

Now, in order to download books you do need to have an account at Amazon, but I already had one (I typically purchase two or three books a week), so all I had to do was enter my account details (user name and password) into the Kindle, and I was ready to 'rock and roll' and download my first book.

I decided to dip my toes in the water with a recent science fiction book, which would have sported a price-tag of around \$10 (£6) as a physical paperback book, but which cost only \$6 (£4) in its electronic incarnation. The download took less than a minute, after which I was up and running.

## Good experience

To be honest, the reason I had held back from purchasing a Kindle in the past was that I wasn't sure how good the 'user experience' would be. As it happens, I'm delighted to report that it's great; plus, there are all sorts of advantages to the electronic version, such as the fact that you can change the size of the font on the fly. Also there's an inbuilt dictionary, so if you are unsure of a word, you can move a cursor over it and an associated

dictionary definition immediately pops up. Also, you can set electronic bookmarks, add notes, cut out clippings... and the list goes on.

There's also a larger version of the Kindle – the Kindle DX ([www.amazon.com/Kindle-Wireless-Reading-Display-Generation/dp/B0015TG12Q](http://www.amazon.com/Kindle-Wireless-Reading-Display-Generation/dp/B0015TG12Q)) – that may be more appropriate for some folks. This really does look rather tasty; it has a much bigger display screen and it can hold up to 3500 books, periodicals and other items.

This little beauty also offers some cool features like an auto-rotating screen, which means that the display auto-rotates from portrait to landscape as you turn the device, thereby allowing you to easily view full-width maps, graphs, tables, and web pages (you have to set this manually on the smaller model).

I was going to say that the main downside to the Kindle DX (apart from its substantially higher price-tag) is the fact that its wireless works only in the US, but I just bounced over to Amazon and I see that the latest version now has global wireless capability. In fact, I just clicked the 'Coverage Map' link on Amazon, and I see that just about every country I'm every likely to visit is covered for both Kindles, including India, where I will be presenting a number of papers at a conference this coming summer (I'll tell you more about that in a future column).

Of course, there will always be a place in my heart for real, physical books printed on paper, but when it comes to travelling to visit my mom in the UK, or jetting around the globe to 'do stuff', from this point on I think I will be carrying only my Kindle.



**Check out 'The Cool Beans Blog' at [www.epemag.com](http://www.epemag.com)**

*Catch up with Max and his up-to-date topical discussions*



# Net Work

Alan Winstanley



This month, I'll start with a timely nag about taking backups: a recent near-total disaster involving a friend's IBM desktop server running RAID necessitated a full reinstallation of essential data and software. She depends entirely on her system for her business, and we were fortunate enough to recover data from the damaged hard disks. However, all software had to be reinstalled from scratch: you do keep serial numbers, log-ins and passwords safely locked away somewhere for such times, don't you? So consider off-site backups such as Carbonite, Netgear ReadyNAS Vault, or F-Secure Online Backup.

When rebuilding systems, a reader has suggested a useful online tool that helps with downloading and installing useful essential applications (apps). Ninite from [www.ninite.com](http://www.ninite.com) is a brilliant Windows fetcher and installer that provides a shopping list of all the best downloadable applications, including Firefox, AVG Anti Virus, Skype, MalwareBytes, CCleaner, Google Earth and very many more. Simply tick the apps you want and the downloader is created automatically. Ninite is small, fast and light – not even Ninite is installed. Check their website for a list of available downloads, and why not suggest your own apps. too?

## A flashy smartphone

Regular readers will know that I'm a big fan of my HTC Tytn II Windows Mobile phone, which allows me to check email on the move and surf the web with some limitations. This has only become more practical in the last year or so as network coverage has increased. Tariffs seem more generous too, with the networks striving to outdo each other in the scramble to poach customers from rivals. Despite the 'unlimited' GPRS or 3G data quotas now on offer, I still only download the first few kilobytes of an email just to get the feel, before fetching interesting-looking emails in full, individually.



A hugely useful downloader to help installing essential software is **Ninite.com**

A few weeks ago my patience finally ran out with my provider (Orange) due to poor coverage and I felt the phone wasn't paying for itself. I migrated to rival O2, which provides a SIM only with a so-called unlimited data tariff on a 30-day rolling contract, without being locked into an 18- or 24-month contract. The data coverage is far better and now the phone is rapidly becoming indispensable, unchaining me from my office PC into the bargain as well!

Several weeks elapsed before Orange could unlock my phone, so a 95p SIM card from Tesco Mobile (which is powered by O2), dropped into an ancient Nokia phone, helped me over a transition period. eBay is a useful source of spares and chargers for such legacy hardware. I felt that an old Nokia car charger for £1 was also worth buying as a backup, because you never know when something might fail, as my IBM-desktop owning friend (above) found to her cost.

## Oh no?

So now I have an Orange-supplied HTC Tytn II running on O2. A variety of websites such as <http://xda-developers.com> are dedicated to the technology of updating or 'flashing' phones with the latest ROM upgrade, but it seems a huge risk to take, just to scrub out an Orange splash screen and delete some trivial Orange customisation or other: a job for another day perhaps.

The more urgent problem of using O2's mobile data service then arose. I needed their network's Access Point Name (APN) so that my phone could utilise GPRS. Disappointingly, O2 refused to help, citing an 'unsupported handset' and suggesting that I ask the handset manufacturer instead! Once again, the web came to the rescue, and I must commend the UK website [www.filesaveas.com](http://www.filesaveas.com), which listed all the necessary GPRS settings for all UK networks. Armed with this information, at last my reinvigorated phone sprang into life on the new network. I configured the AuthSMTP service settings to send mobile email, and a few test emails confirmed all was well.

As an extra attraction, my TomTom satellite navigation and phone now work together perfectly via Bluetooth, thanks to a TomTom windscreen holder with built-in microphone scrounged off eBay. Also sourced via eBay (Argos Clearance Bargains, no less!) was an in-car 'safe' for storing my satnav in an impregnable box. And I finally had crystal clear hands-free calling as well.

More websurfing turned up some indispensable free software for use with my Windows smartphone. MyMobiler from [www.mymobiler.com](http://www.mymobiler.com) allows the phone screen to be viewed on the PC desktop; just connect via USB, start MyMobiler and the smartphone's display appears in a window pane. You can navigate around the phone using the mouse, play with the address book and dial out on the mobile with the keyboard's numpad. Where necessary, use the arrow keys instead of the D-pad on the phone.

MyMobiler claims to support Windows Mobile 2003, Mobile 5 and 6, and it worked immediately on my WM6.1 phone, though connecting it does start Microsoft Active Sync as well. (Newer versions of Windows utilise Microsoft Device Stage instead; more details from <http://windows.microsoft.com/en-GB/windows7/What-is-Device-Stage>)

You can email me at [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk).



Author's mobile phone screen displayed on a Windows desktop using MyMobiler free from [www.mymobiler.com](http://www.mymobiler.com)

## Electronics Teach-In CD-ROM

### Mike Tooley

A broad-based introduction to electronics – find out how circuits work and what goes on inside them. The CD-ROM contains the whole *Teach-In 2006* series (originally published in *EPE*) in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the *Teach-In* series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.


The *Teach-In* series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC. There is also a MW/LW Radio project in the *Teach-In* series.

The interactive Review tests will help you to check your knowledge at the end of each part of *Electronics Teach-In*. You can take these tests as many times as you like, improving your score with each attempt.

The final test covers all aspects of *Electronics Teach-In* and will provide you with a means of checking your overall knowledge of electronics. Once again, you can take the test as many times as you like.

CD-ROM

Order code ETI – CD-ROM £8.50

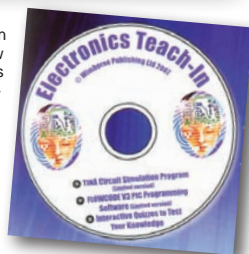

## ROBOTICS

### INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various 'click-together' components supplied in the basic RIS kit. Then explains in simple terms how the 'brain' of the robot may be programmed on screen using a PC and 'zapped' to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages – large format

Order code BP901 £14.99

### MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

198 pages

Order code BP902 £14.99

### ANDROIDS, ROBOTS AND ANIMATRONS Second Edition – John Iovine

Build your own working robot or android using both off-the-shelf and workshop constructed materials and devices. Computer control gives these robots and androids two types of artificial intelligence (an expert system and a neural network). A lifelike android hand can be built and programmed to function doing repetitive tasks. A fully animated robot or android can also be built and programmed to perform a wide variety of functions.

The contents include an Overview of State-of-the-Art Robots; Robotic Locomotion; Motors and Power Controllers; All Types of Sensors; Tilt; Bump; Road and Wall Detection; Light; Speech and Sound Recognition; Robotic Intelligence (Expert Type) Using a Single-Board Computer Programmed in BASIC; Robotic Intelligence (Neural Type) Using Simple Neural Networks (Insect Intelligence); Making a Lifelike Android Hand; A Computer-Controlled Robotic Insect Programmed in BASIC; Telespresence Robots With Actual Arcade and Virtual Reality Applications; A Computer-Controlled Robotic Arm; Animated Robots and Androids; Real-World Robotic Applications.

224 pages

Order code MGH1 £16.99

## DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF *EPE*

3

All prices include UK postage

## RADIO

### BASIC RADIO PRINCIPLES AND TECHNOLOGY Ian Poole

Radio technology is becoming increasingly important in today's high technology society. There are the traditional uses of radio which include broadcasting and point to point radio as well as the new technologies of satellites and cellular phones. All of these developments mean there is a growing need for radio engineers at all levels.

Assuming a basic knowledge of electronics, this book provides an easy to understand grounding in the topic.

Chapters in the book: Radio Today, Yesterday, and Tomorrow; Radio Waves and Propagation; Capacitors, Inductors, and Filters; Modulation; Receivers; Transmitters; Antenna Systems; Broadcasting; Satellites; Personal Communications; Appendix – Basic Calculations.

263 pages

Order code NE30 £28.99

### PROJECTS FOR RADIO AMATEURS AND S.W.L.S. R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets;

A wavetrap to combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages

Order code BP304 £4.45

### AN INTRODUCTION TO AMATEUR RADIO I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the last century. This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages

Order code BP257 £5.49

## COMPUTERS AND COMPUTING

### ELECTRONICS TEACH-IN 2 USING PIC MICROCONTROLLERS A PRACTICAL INTRODUCTION

This *Teach-In* series of articles was originally published in *EPE* in 2008 and, following demand from readers, has now been collected together in the *Electronics Teach-In 2* book.

The series is aimed at those using PIC microcontrollers for the first time. Each part of the series includes breadboard layouts to aid understanding and a simple programmer project is provided.

Also included are 29 *PIC N' Mix* articles, also republished from *EPE*. These provide a host of practical programming and interfacing information, mainly for those that have already got to grips with using PIC microcontrollers.

An extra four part beginners guide to using the C programming language for PIC microcontrollers is also included.

The free cover-mounted CD-ROM contains all of the software for the *Teach-In 2* series and *PIC N' Mix* articles in this book, plus a range of items from Microchip – the manufacturers of the PIC microcontrollers. The material has been compiled by Wimborne Publishing Ltd. with the assistance of Microchip Technology Inc.

The Microchip items are: MPLAB Integrated Development Environment V8.20; Microchip Advance Parts Selector V2.32; Treelink; Motor Control Solutions; 16-bit Embedded Solutions; 16-bit Tool Solutions; Human Interface Solutions; 8-bit PIC Microcontrollers; PIC24 Microcontrollers; PIC32 Microcontroller Family with USB On-The-Go; dsPIC Digital Signal Controllers.

160 pages + CD-ROM

Order code ETI2 £9.50

FREE  
CD-ROM

### BUILD YOUR OWN PC – Fourth Edition Morris Rosenthal

More and more people are building their own PCs. They get more value for their money, they create exactly the machine they want, and the work is highly satisfying and actually fun. That is, if they have a unique beginner's guide like this one, which visually demonstrates how to construct a computer from start to finish.

Through 150 crisp photographs and clear but minimal text, readers will confidently absorb the concepts of computer building. The extra-big format makes it easy to see what's going on in the pictures. The author goes 'under the hood' and shows step-by-step how to create a Pentium 4 computer or an Athlon 64 or Athlon 64FX, covering: What first-time builders need to know; How to select and purchase parts; How to assemble the PC; How to install Windows XP. The few existing books on this subject, although outdated, are in steady demand. This one delivers the expertise and new technology that fledgling computer builders are looking for.

224 pages – large format

Order code MGH2 £16.99

### PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24 Lucio Di Jasio (Application Segments Manager, Microchip, USA)


A Microchip insider tells all. Focuses on examples and exercises that show how to solve common, real-world design problems quickly. Includes handy checklists to help readers perform the most common programming and debugging tasks. FREE CD-ROM includes source code in C, the Microchip C30 compiler, and MPLAB SIM software, so that readers gain practical, hands-on programming experience.

Until recently, PICs didn't have the speed and memory necessary for use in designs such as video- and audio-enabled devices. All that changed with the introduction of the 16-bit PIC family, the PIC24. This new guide teaches readers everything they need to know about the architecture of these chips, how to program them, how to test them and how to debug them. Lucio's common-sense, practical, hands-on approach starts out with basic functions and guides the reader step-by-step through even the most sophisticated programming scenarios.

Experienced PIC users and newcomers alike will benefit from the text's many thorough examples, which demonstrate how to nimbly side-step common obstacles and take full advantage of all the 16-bit features.

496 pages + CD-ROM

Order code NE45 £38.00

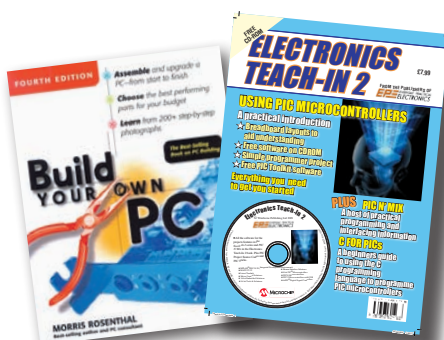



## NEW FULL COLOUR COMPUTING BOOKS

### WINDOWS 7 - TWEAKS, TIPS AND TRICKS Andrew Edney

This book will guide you through many of the exciting new features of Windows 7. Microsoft's latest and greatest operating system. It will provide you with useful hints, tips and warnings about possible difficulties and pitfalls. This book should enable you to get much more out of Windows 7 and, hopefully, discover a few things that you may not have realised were there.

Among the topics covered are: A brief overview of the various versions of Windows 7. How to install and use Upgrade Advisor, which checks to see if your computer meets the minimum requirements to run Windows 7 and that your software and drivers are supported by Windows 7. How to use Windows Easy Transfer to migrate your data and settings from your Vista or XP machine to your new Windows 7 computer. Exploring Windows 7 so that you will become familiar with many of its new features and then see how they contrast with those of earlier versions of Windows. How to connect to a network and create and use Home Groups to easily share your pictures, videos, documents, etc., with the minimum of hassle. Why Windows Live Essentials is so useful and how to download and install it. A brief introduction to Windows Media Center. The use of Action Center, which reports security and maintenance incidents. Windows Memory Diagnostic to detect the fairly common problem of faulty memory and Troubleshooting tools.

120 pages

Order code BP708 £8.49

### HOW TO BUILD A COMPUTER MADE EASY R.A. Penfold

Building your own computer is a much easier than most people realise and can probably be undertaken by anyone who is reasonably practical. However, some knowledge and experience of using a PC would be beneficial. This book will guide you through the entire process. It is written in a simple and straightforward way with the explanations clearly illustrated with numerous colour photographs.

The book is divided into three sections: *Overview and preparation* - Covers understanding the fundamentals and choosing the most suitable component parts for your computer, together with a review of the basic assembly. *Assembly* - Explains in detail how to fit the component parts into their correct positions in the computer's casing, then how to connect these parts together by plugging the cables into the appropriate sockets. No soldering should be required and the only tools that you are likely to need are screwdrivers, small spanners and a pair of pliers.

*BIOS and operating system* - This final section details the setting up of the BIOS and the installation of the Windows operating system, which should then enable all the parts of your computer to work together correctly. You will then be ready to install your files and any application software you may require.

The great advantage of building your own computer is that you can 'tailor' it exactly to your own requirements. Also, you will learn a tremendous amount about the structure and internal workings of a PC, which will prove to be invaluable should problems ever arise.

120 pages

Order code BP707 £8.49

### AN INTRODUCTION TO eBAY FOR THE OLDER GENERATION

Cherry Nixon

eBay is an online auction site that enables you to buy and sell practically anything from the comfort of your own home. eBay offers easy access to the global market at an amazingly low cost and will enable you to turn your clutter into cash.

This book is an introduction to eBay.co.uk and has been specifically written for the over 50s who have little knowledge of computing. The book will, of course, also apply equally to all other age groups. The book contains ideas for getting organised for long term safe and successful trading. You will learn how to search out and buy every conceivable type of thing. The book also shows you how to create auctions and add perfect pictures. There is advice on how to avoid the pitfalls that can befall the inexperienced.

Cherry Nixon is probably the most experienced teacher of eBay trading in the UK and from her vast experience has developed a particular understanding of the issues and difficulties normally encountered by individuals.

So, if you are new to computers and the internet and think of a mouse as a rodent, then this is the book for you!

120 pages

Order code BP709 £8.49

### GETTING STARTED IN COMPUTING FOR THE OLDER GENERATION

Jim Gatenby

You can learn to use a computer at any age and this book will help you achieve this. It has been especially written for the over 50s, using plain English and avoiding technical jargon wherever possible. It is lavishly illustrated in full colour.

Among the many practical and useful subjects that are covered in this book are: Choosing the best computing system for your needs. Understanding the main hardware components of your computer. Getting your computer up and running in your home. Setting up peripheral devices like printers and routers. Connecting to the internet using wireless broadband in a home with one or more computers. Getting familiar with Windows Vista and XP the software used for operating and maintaining your computer. Learning about Windows built-in programs such as Windows Media Player, Paint and Photo Gallery.

Plus, using the Ease of Access Center to help if you have impaired eyesight, hearing or dexterity problems. Installing and using essential software such as Microsoft Office suite. Searching for the latest information on virtually any subject. Keeping in touch with friends and family using e-mail. Keeping your computer running efficiently and your valuable data files protected against malicious attack.

This book will help you to gain the basic knowledge needed to get the most out of your computer and, if you so wish, give you the confidence to even join a local computer class.

120 pages

Order code BP704 £8.49

## THEORY AND REFERENCE

### ELECTRONIC CIRCUITS - FUNDAMENTALS & APPLICATIONS

Third Edition

Mike Tooley

A comprehensive reference text and practical electronics handbook in one volume - at an affordable price!

New chapter on PIC microcontrollers - the most popular chip family for use in project work by hobbyists and in colleges and universities.

New companion website: spreadsheet design tools to simplify circuit calculations; circuit models and templates to enable virtual simulation; a bank of on-line questions for lecturers to set as assignments, and on-line self-test multiple choice questions for each chapter with automatic marking, to enable students to continually monitor their progress and understanding.

The book's content is matched to the latest pre-degree level courses, making this an invaluable reference for all study levels, and its broad coverage is combined with practical case studies, based in real-world engineering contexts throughout the text.

The unique combination of a comprehensive reference text, incorporating a primary focus on practical applications, ensures this text will prove a vital guide for students and also for industry-based engineers, who are either new to the field of electronics, or who wish to refresh their knowledge.

400 pages

Order code NE43 £25.99

### BEBOP TO THE BOOLEAN BOOGIE

Third Edition

Clive (Max) Maxfield

This book gives the 'big picture' of digital electronics. This indepth, highly readable, guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more. The author's tongue-in-cheek humour makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. Comes with a free CD-ROM which contains an eBook version with full text search plus bonus chapter - An Illustrated History of Electronics and Computing.

Contents: Fundamental concepts; Analog versus digital; Conductors and insulators; Voltage, current, resistance, capacitance and inductance; Semiconductors; Primitive logic functions; Binary arithmetic; Boolean algebra; Karnaugh

maps; State diagrams, tables and machines; Analog-to-digital and digital-to-analog; Integrated circuits (ICs); Memory ICs; Programmable ICs; Application-specific integrated circuits (ASICs); Circuit boards (PWBs and DWBs); Hybrids; Multichip modules (MCMs); Alternative and future technologies.

500 pages

Order code BEB1 £32.99

### BEBOP BYTES BACK (and the Bebopter Computer Simulator)

CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to Bebopter to the Boolean Boogie is a multimedia extravaganza of information about how computers work. It picks up where "Bebopter" left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

CD-ROM

Order code BEB2 CD-ROM £21.95

### FUNDAMENTAL ELECTRICAL AND ELECTRONIC PRINCIPLES

Third Edition

C. R. Robertson

Covers the essential principles that form the foundations for electrical and electronic engineering courses. The coverage of this new edition has been carefully brought in line with the core unit 'Electrical and Electronic Principles' of the 2007 BTEC National Engineering specification. This qualification from Edexcel attracts more than 10,000 students per year.

The book explains all theory in detail and backs it up with numerous worked examples. Students can test their

understanding with end of chapter assignment questions for which answers are provided. In this new edition, the layout has been improved and colour has been added. A free companion website with additional worked examples and chapters is also available.

368 pages

Order code NE47 £21.99

### STARTING ELECTRONICS

Third Edition

Keith Brindley


A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages

Order code NE42 £13.99

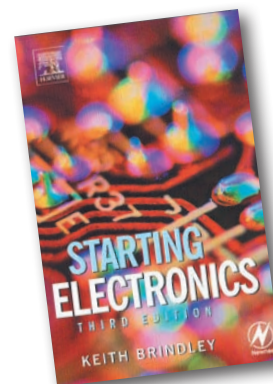

## MUSIC, AUDIO AND VIDEO

### MAKING MUSIC WITH YOUR COMPUTER

Stephen Bennett

Nearly everyone with musical aspirations also has a computer. This same computer can double as a high quality recording studio capable of producing professional recordings. This book tells you what software and hardware you will need to get the best results.

You'll learn about recording techniques, software and effects, mixing, mastering and CD production.

Suitable for PC and Mac users, the book is full of tips, "how to do" topics and illustrations. It's the perfect answer to the question "How do I use my computer to produce my own CD?"

92 pages

Order code PC120

£10.95



### QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh

MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages

Order code PC119

£7.45

### VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115

£10.95 ~~£10.95~~ £5.45

## RADIO BYGONES

We also carry a selection of books aimed at readers of *EPE's* sister magazine on vintage radio *Radio Bygones*. These books include, the four volumes of our own *Wireless For the Warrior* by Louis Meulstee. These are a technical history of radio communication equipment in the British Army and clandestine equipment from pre-war through to the 1960s.

For details see the shop on our UK web site at [www.epemag.com](http://www.epemag.com) or contact us for a list of *Radio Bygones* books.

## PROJECT BUILDING AND TESTING

### ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392

£5.99

### ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different. No doubt many of the projects featured here have practical applications, but they are all worth a try for their interest value alone.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

### PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

### GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

102 pages

Order code BP239

£5.49

## BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £3 per book. Surface mail can take up to 10 weeks to some countries. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **DIRECT BOOK SERVICE** or card details, Visa, Mastercard or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, SEQUOIA HOUSE, 398a RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.  
Tel 01202 873872 Fax 01202 874562. E-mail: [dbs@wimborne.co.uk](mailto:dbs@wimborne.co.uk)

Order from our online shop at: [www.epemag.com](http://www.epemag.com)

## BOOK ORDER FORM

Full name: .....

Address: .....

..... Post code: ..... Telephone No: .....

Signature: .....

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £ .....

☐ Please charge my card £ ..... Card expiry date: .....

Card Number ..... Maestro Issue No. ....

Valid From Date ..... Card Security Code ..... (The last three digits on or just below the signature strip)

Please send book order codes: .....

Please continue on separate sheet of paper if necessary



# PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872; Fax 01202 874562; Email: [orders@epemag.wimborne.co.uk](mailto:orders@epemag.wimborne.co.uk). On-line Shop: [www.epemag.com](http://www.epemag.com).** Cheques should be crossed and made payable to *Everyday Practical Electronics* (**Payment in £ sterling only**).

**NOTE:** While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. **WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.**

Please check price and availability in the latest issue.  
A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

| PROJECT TITLE                                       | ORDER CODE     | COST         |
|---|----------------|--------------|
| <b>JANUARY '09</b>                                  |                |              |
| 20W Class-A Amplifier                               |                |              |
| – Preamplifier and Remote Volume Control            | 696            | £7.93        |
| 1000:1 UHF Prescaler (double-sided)                 | 697            | £12.05       |
| <b>FEBRUARY '09</b>                                 |                |              |
| 1.3V To 22V Regulated Power Supply                  | 698            | £5.39        |
| ★ LED Tachometer                                    |                |              |
| – Control Board                                     | 699            | } set £9.52  |
| – Display Board                                     | 700            |              |
| <b>MARCH '09</b>                                    |                |              |
| Tank Water Level Indicator                          | 701            | £6.34        |
| ★ Digital Stereo VU/Peak Meter                      |                |              |
| – Main Board  | 702            | } set £8.24  |
| – Switch Board                                      | 703            |              |
| <b>APRIL '09</b>                                    |                |              |
| Versatile 4-Input Mixer                             | 704            | £10.31       |
| ★ Oscar Noughts & Crosses Machine                   | 705            | £7.29        |
| ★ GPS-Based Frequency Reference                     |                |              |
| – Main Board  | 706            | } set £11.10 |
| – Display Board                                     | 707            |              |
| <b>MAY '09</b>                                      |                |              |
| Infrared Audio Headphone Link                       | 708            | } set £9.20  |
|   | 709            |              |
| Microstepping Unipolar Stepping Motor Driver        | 710            | £7.49        |
| <b>JUNE '09</b>                                     |                |              |
| ★ Spectacular Bike Wheel POV Display (double-sided) | 711 (set of 3) | £23.73       |
| ★ Remote Volume Control & Preamplifier Module       |                |              |
| – Main Board  | 714            | } set £9.20  |
| – Display Board                                     | 715            |              |
| – Power Supply Board                                | 716            |              |
| <b>JULY '09</b>                                     |                |              |
| ★ Solar Water Heating System Controller             |                |              |
| – Main Board  | 712            | } set £15.00 |
| – Display Board                                     | 713            |              |
| ★ PIC Probe (double-sided)                          | 717            | £9.50        |
| ★ Simple Data-Logging Weather Station               |                |              |
| – Main Board  | 718            | } set £6.66  |
| – RS232 Board                                       | 719            |              |
| <b>AUGUST '09</b>                                   |                |              |
| ★ Fast Charger For NiMH Batteries                   | 720            | £6.66        |
| ★ Rolling Code Keyless Entry System                 |                |              |
| – Main Board  | 721            | £7.29        |
| – Transmitter (2off)                                | 722 (2off)     | £6.18        |
| <b>SEPTEMBER '09</b>                                |                |              |
| PIC Programmer SOIC Converter                       | 723            | £5.07        |
| ★ Random Mains Timer                                | 724            | £9.51        |
| <b>OCTOBER '09</b>                                  |                |              |
| 1pps Driver for Quartz Clocks                       | 725            | £5.71        |
| Minispot 455kHz Modulated Oscillator                | 726            | £5.87        |
| Prog. Ignition System for Cars                      |                |              |
| – Ignition Unit                                     | 727            | } set £11.10 |
| – Ignition Coil Driver                              | 728            |              |
| – LCD Hand Controller                               | 729            |              |
| ★ Guitar-To-MIDI System                             | 730            | £6.66        |

| PROJECT TITLE   | ORDER CODE | COST         |
|---|------------|--------------|
| <b>NOVEMBER '09</b>                                     |            |              |
| Class-A Headphone Amplifier                             |            |              |
| – Main (pair)   | 731        | } set £9.99  |
| – PSU   | 732        |              |
| Emergency 12V Lighting Controller                       | 733        | £7.20        |
| ★ Digital VFO With LCD Graphics Display (doubled sided) | 734        | £13.00       |
| <b>DECEMBER '09</b>                                     |            |              |
| Knock Detector  | 735        | £6.66        |
| ★ 12V/24V High-Current Motor Speed Controller           |            |              |
| – Main  | 736        | } set £10.78 |
| – Display   | 737        |              |
| <b>JANUARY '10</b>                                      |            |              |
| ★ UHF Remote-Controlled Mains Switch                    | 738        | £7.93        |
| ★ UHF Remote Mains Switch Transmitter                   | 739        | £6.00        |
| ★ Playback Adapter For CD-ROM Drives                    | 740        | £7.61        |
| <b>FEBRUARY '10</b>                                     |            |              |
| ★ Charge Controller For 12V Lead-Acid Batteries         | 741        | £6.66        |
| ★ Working Days Alarm Clock                              |            |              |
| – Main (double-sided)                                   | 742        | } set £25.00 |
| – Display (double-sided)                                | 743        |              |
| Low-cost LPT-To-I <sup>2</sup> C Interface              | 744        | £6.30        |
| <b>MARCH '10</b>  |            |              |
| ★ High-Accuracy Digital LC Meter – Main                 | 745        | } set £7.93  |
| – Adaptor   | 746        |              |
| – Shorting Bar  | 747        |              |
| 2-way Stereo Headphone Adaptor                          | 748        | £10.30       |
| ★ Shift Indicator and Rev Limiter For Cars – Main       | 749        | } set £9.04  |
| – Display   | 750        |              |




## EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: [www.epemag.com](http://www.epemag.com)

## PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website ([www.epemag.com](http://www.epemag.com)); go to the 'Library' section.

## EPE PRINTED CIRCUIT BOARD SERVICE

| Order Code   | Project | Quantity               | Price |
|--|---------|------------------------|-------|
| Name .....   |         |                        |       |
| Address .....  |         |                        |       |
| Tel. No. ....  |         |                        |       |
| I enclose payment of £ ..... (cheque/PO in £ sterling only) to:  |         |                        |       |
| <b>Everyday Practical Electronics</b>  |         |                        |       |
|    |         |                        |       |
| Card No. ....  |         |                        |       |
| Valid From .....   |         | Expiry Date .....      |       |
| Card Security No. ....   |         | Maestro Issue No. .... |       |
| Signature .....  |         |                        |       |

**Note:** You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>

## EP<sup>3</sup> EVERYDAY PRACTICAL ELECTRONICS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-four years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Phone: 01202 873872. Fax: 01202 874562. Email: [epads@wimborne.co.uk](mailto:epads@wimborne.co.uk). For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

### SELLWEB LTD

Supplying electronic components to schools, colleges, Private & commercial clients.

No Minimum order. Low package charge.

Buy online: [www.sellweb.co.uk](http://www.sellweb.co.uk)

Tel: 01827 285750

### Versatile Programmable PIC On Screen Display System

Display text over any composite video signal



**PAL - NTSC compatible**  
 • Fully programmable I/O for sensor interfaces  
 • PIC 16F628A micro • User definable fonts  
 Example code for MSF, cash register, 1-wire & GPS data display

[WWW.PIC-OSD.COM](http://WWW.PIC-OSD.COM)

[www.partridgeelectronics.co.uk](http://www.partridgeelectronics.co.uk)

For The Electronic Components & Hardware You Have Been Looking For

[spinvent.co.uk](http://spinvent.co.uk)



...invent with the Propeller microcontroller and Spin programming language from Parallax

### BTEC ELECTRONICS TECHNICIAN TRAINING

NATIONAL ELECTRONICS  
 VCE ADVANCED ICT  
 HNC AND HND ELECTRONICS  
 FOUNDATION DEGREES  
 NVQ ENGINEERING AND IT  
 DESIGN AND TECHNOLOGY

LONDON ELECTRONICS COLLEGE  
 20 PENYVERN ROAD  
 EARLS COURT, LONDON SW5 9SU  
 TEL: (020) 7373 8721  
[www.lec.org.uk](http://www.lec.org.uk)



### CANTERBURY WINDINGS

UK manufacturer of toroidal transformers (10VA to 1kVA)  
 All transformers made to order. No design fees. No minimum order.  
[www.canterburywindings.co.uk](http://www.canterburywindings.co.uk)  
 01227 450810

### BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components  
 Place a secure order on our website or call our sales line  
 All major credit cards accepted  
 Web: [www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)  
 Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield, Derbyshire S40 2QR. Sales: 01246 200222  
 Send 60p stamp for catalogue

**Robot Bits**.co.uk

Robot Kits and Components

0845 5 191 282

### ELECTRONIC COMPONENTS FOR SALE

Large quantity of New/Unused components ideal for enthusiast or small to medium business, includes 4 rack cabinets and 1-2 big boxes (over £5K worth).  
 For more info ring Bob (07757) 651549 (Stevenage Hertfordshire)

### Get rid of your Electrical Gremlins!



For more information visit [www.contralube.com](http://www.contralube.com)  
 In Stock and available at: [maplin](http://www.maplin.co.uk)  
 www.maplin.co.uk Tel: 0844 557 6000

### CPS Solar

Solar panels, solar cells, and many more alternative energy products for battery charging etc, please visit our website for further info or call  
 Tel: 0870 765 2334.  
[www.solarpanelsonline.co.uk](http://www.solarpanelsonline.co.uk)

[www.cstech.co.uk](http://www.cstech.co.uk)



DTMF decoder kit with 6 outputs and morse transpond  
 £14.99

### Miscellaneous

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

KITS, TOOLS, COMPONENTS. S.A.E. Catalogue. SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB, <http://sir-kit.webs.com>

### A TOP FLIGHT GIFT JUST RELEASED

The official DVD of the now annual Bournemouth Air Festival, produced by Hallmark Productions, is now available from [www.hallmarkproductions.com](http://www.hallmarkproductions.com) for £14.99. The DVD is packed with extraordinary footage of the aerobatic displays over the beachfront, plus on-board and in-cockpit action. Festival highlights, display highlights along with exclusive display commentary, pilot interviews, and a photographic gallery are some of the special features included.

A look ahead at the 2010 Air Festival is also included.

Preview the Bournemouth Air Festival DVD by visiting [www.YouTube.com/user/BournemouthAirFest](http://www.YouTube.com/user/BournemouthAirFest) or [www.hallmarkproductions.com](http://www.hallmarkproductions.com).





# Europe's Largest Surplus Store

**20,000,000 Items on line NOW !**  
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

**We Ship Worldwide**

**Surplus Wanted**

**www.distel.co.uk**

**Display Electronics**  
29 / 35 Osborne Road  
Thornton Heath  
Surrey UK CR7 8PD

**Telephone**  
[44] 020 8653 3333  
**Fax** [44] 020 8653 8888

## Rechargeable Batteries With Solder Tags

### NIMH

AA 2000mAh .....£2.82  
C 4Ah .....£4.70  
D 9Ah .....£7.60  
PP3 150mAh .....£4.95

### NICAD


AA 650mAh .....£1.41  
C 2.5Ah .....£3.60  
D 4Ah .....£4.95

### Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.

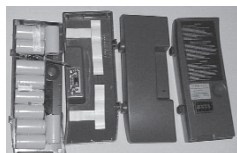866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

**JPG Electronics**

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

**EP E** EVERYDAY PRACTICAL  
**ELECTRONICS**

## NEXT MONTH

### PIC-BASED WATER TANK LEVEL METER

Looking for a water tank level meter that's easy to install, accurate, but doesn't need a complicated in-tank sensor? This PIC-based unit uses a pressure sensor to monitor water level and it displays tank level at the press of a switch. It can even send its readings to a base station with an LCD readout via an RF link.

### USB POWER INJECTOR

A portable USB hard drive is a great way to back up data, but what if your USB ports are unable to supply enough 'juice' to power the drive? This nifty little project will make sure you can get the data flowing.

### ALTERNATIVE 12V 10A POWER SUPPLY

This project is an unusual and useful take on power supplies. There are many instances when you need a 12V 3A power supply, but occasionally the current peaks much higher than this. Normally, you would simply uprate the whole supply to match the peak; but with this circuit, the peaks are met from a battery. It can even keep going if there is a mains failure.

### LM3909 REPLACEMENT MODULE

The venerable, useful and easy-to-use IC the LM3909 was a popular chip used for flashing LEDs, delivering a tone to a speaker or triggering a triac. Sadly, it has been discontinued – but now it has been reborn in this handy little module! It does everything and more that the first version did.

**APRIL '10 ISSUE**  
**ON SALE 11 MARCH**

Content may be subject to change

## ADVERTISERS INDEX

|                                 |             |
|---------------------------------|-------------|
| AUDON ELECTRONICS .....         | 41          |
| BETA LAYOUT .....               | 41          |
| CRICKLEWOOD .....               | 59          |
| DISPLAY ELECTRONICS .....       | 80          |
| ESR ELECTRONIC COMPONENTS ..... | 6           |
| JAYCAR ELECTRONICS .....        | 4/5         |
| JPG ELECTRONICS .....           | 80          |
| LABCENTER .....                 | Cover (iv)  |
| LASER BUSINESS SYSTEMS .....    | 58          |
| MAGENTA ELECTRONICS .....       | 41          |
| NURVE NETWORKS LLC .....        | 41          |
| PEAK ELECTRONIC DESIGN .....    | Cover (iii) |
| PICO TECHNOLOGY .....           | 59          |
| QUASAR ELECTRONICS .....        | 2/3         |
| SHERWOOD ELECTRONICS .....      | 59          |
| STEWART OF READING .....        | Cover (iii) |

### ADVERTISEMENT OFFICES:

Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU

PHONE: 01202 873872 Fax: 01202 874562

EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 7

# Win a Microchip mTouch AR1000 Development Kit!

EPE  
EXCLUSIVE

**E**VERYDAY PRACTICAL ELECTRONICS is offering its readers the chance to win one of four mTouch AR1000 Development Kits from Microchip. The kit provides everything designers need to get started using AR1000 resistive controllers and includes the AR1000 development board, a seven-inch four-wire resistive touch screen, a PICKit Serial Analyzer and all the necessary interface cables, as well as a CD containing technical documentation and all the necessary software. The CD also includes an easy-to-use AR1000 configuration utility, which has a graphical user interface (GUI) that enables designers to test all user-configurable options with the AR1000 controllers.



The AR1000 controllers eliminate trial-and-error engineering by providing sophisticated, proprietary touch-screen decoding algorithms that enable applications to receive fully processed, reliable touch coordinates. Combining Microchip's capabilities in microcontroller manufacturing with the recently acquired Hampshire Company's 15+ years of experience designing resistive touch-screen controllers, the AR1000 controllers enable low-risk product development, lower total system cost and shorter time to market for embedded resistive-touch designs. Popular due to its low cost, acceptance of finger, glove or stylus-pen inputs, and overall ease of manufacturing and integration, resistive touch-sensing technology is suitable for applications such as mobile phones, industrial automation, retail point-of-sale, gaming/entertainment, and automobile navigation systems.

The AR1000 controllers provide universal 4-, 5- and 8-wire support, as well as support for SPI, I<sup>2</sup>C and UART communication interfaces, and are available in 20-pin QFN, SOIC and SSOP packages.

## HOW TO ENTER

For your chance to win a Microchip mTouch AR1000 Development Kit, visit <http://www.microchip-comp.com/epe-mTouchAR1000> and enter your details in the online entry form.

## CLOSING DATE

The closing date for this offer is **30 June 2010**

**WORTH  
\$99.99  
(approx. £60.00)  
EACH**





## GO FASTER WITH PROTEUS PCB DESIGN

The latest version of the Proteus Design Suite harnesses the power of your computer's graphics card to provide lightning fast performance. Together with unique transparency options it's now easier than ever to navigate and understand large, multi-layer boards.

### PROTEUS DESIGN SUITE **Features:**

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++ & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the **Proteus Design Suite** include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

**labcenter**  [www.labcenter.com](http://www.labcenter.com)

**Electronics**

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.  
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: [info@labcenter.com](mailto:info@labcenter.com)

Visit our website or  
phone 01756 753440  
for more details